

Tutorial - 6

Oza Dheiryer M.

Page No.:	1
Date:	YOUVA

- ① What will be gain factor for a non-invert closed loop of amp.

$$\rightarrow A_{(V)} = \frac{V_{out}}{V_{in}}$$


$$= \frac{R_2 + R_f}{R_2}$$

$$= 1 + \frac{R_f}{R_2}$$

→ from the equation we can see that gain factor is always greater but never less than one (unity), its positive in nature and determined by the ratio of R_f and R_2 .

- ② How many op-amps are required to implement this equation.
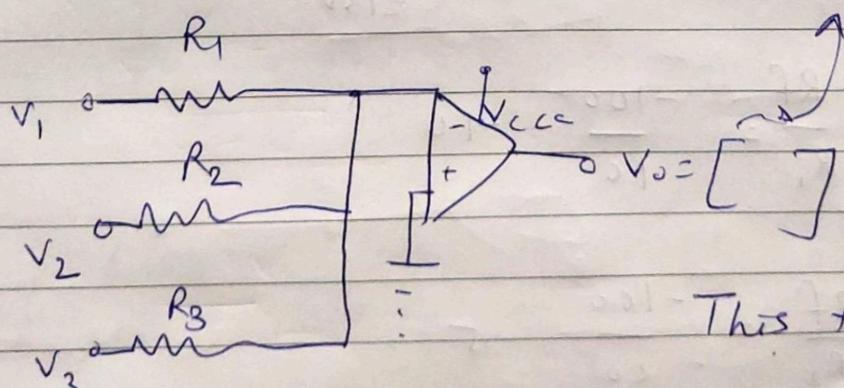
$$\rightarrow V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$




This topology

→ So basically only one op-amp is required.

③ How many op-amps are required to implement this equation $V_o = V_i$,


→ $V_o = V_i$

- Basically Voltage follower

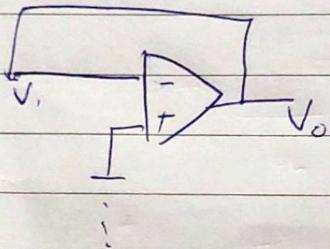

→ So, Only one op-amp is required for $V_o = V_i$, too.

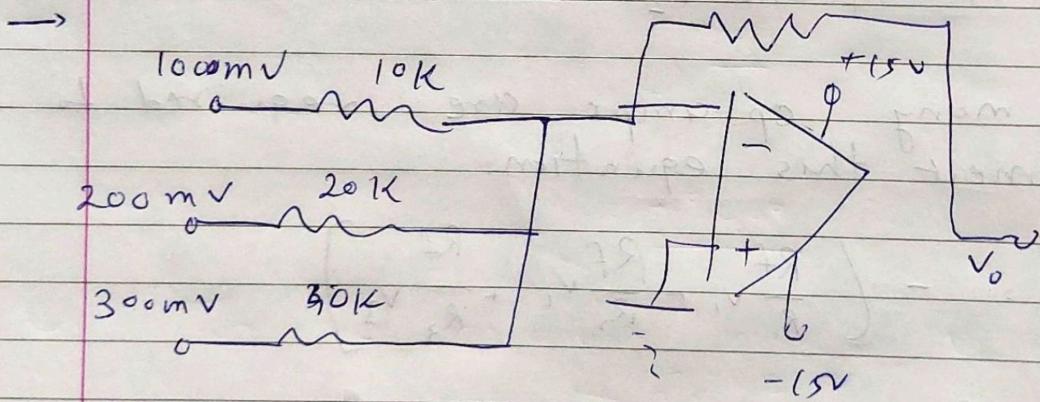④ The loop gain that is considered as closed loop gain can be calculated as.



$$A_1 = -\frac{R_f}{R_1} = \frac{-100}{10} = -10$$

$$A_2 = -\frac{R_f}{R_2} = \frac{-100}{20} = -5$$

$$A_3 = -\frac{R_f}{R_3}$$

$$= -100$$

$\frac{1}{40}$

$$= -2.5$$

$V_{out} =$

$$[A_1 V_1 + A_2 V_2 + A_3 V_3]$$

$$= -10(0.1) + -5(0.2) + -2.5(0)$$


$$= -1 - 1 - 0.75$$

$$= -2.75 \text{ V}_0 +$$

Q

The inverting op-amp shown, loop gain ≈ 100
The closed loop gain $\frac{V_o}{V_s} \approx$

$$R_2 / 10k\Omega$$

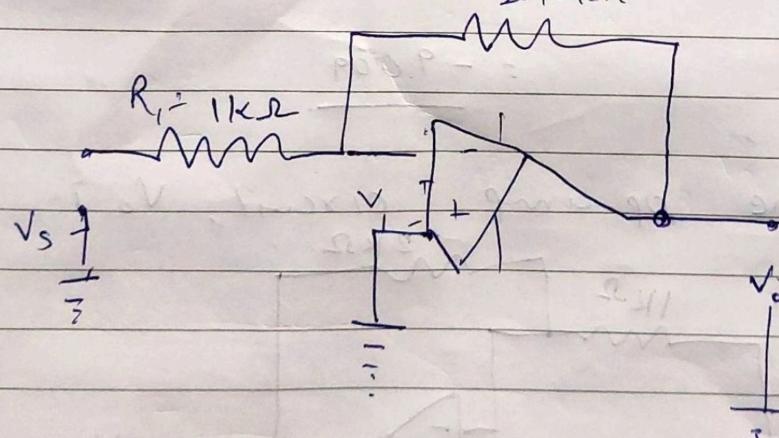

$$R_1 = 1 k\Omega$$

$$R_2 = 10 k\Omega$$

$$A_{OL} = 100$$

It's Inverting op-amp, so

Closed loop gain

$$A_{OL} = \frac{V_o}{V_s}$$

$$= \frac{-R_2}{R_1} \cdot \frac{1 + \frac{R_2}{R_1}}{1 + \frac{A_{OL}}{1 + \frac{R_2}{R_1}}}$$


$$\frac{V_o}{V_s} = \frac{-10}{1 + \frac{(1 + 10)}{100}}$$

$$= \frac{-10}{1 + \frac{11}{100}} = \frac{-1000}{100 + 11}$$

$$= \frac{-1000}{111}$$

$$= -9.009$$

⑥ For the op-amp circuit, V_o is

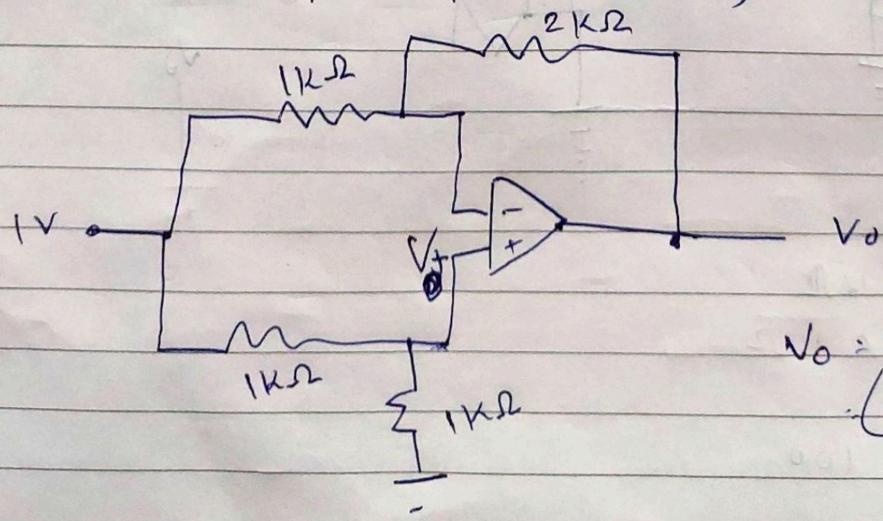

$$V_o = V_{o1} + V_{o2}$$

$$= (a_{v+}) V_{+} + (a_{v-}) V_{-}$$

$$V_{O1} = \left(-\frac{R_2}{R_1} \right) V_{in} \quad (\text{Inverting})$$

$$= -2 \frac{1}{1+1}$$

$$= -2 \text{ Volts}$$

$$V_{O2} = \left(1 + \frac{R_2}{R_1} \right) V_{in} \quad (\text{Non-Inverting})$$

$$= \left(1 + \frac{R_2}{R_1} \right) V_{in} +$$

$$= \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R_3}{R_2 + R_3} \right) V_{in}$$


$$= \left(1 + \frac{2}{1} \right) \left(\frac{1}{1+1} \right) V_{in}$$

$$= 3 \cdot \frac{1}{2}$$

$$\approx 1.5 \text{ Volts}$$

$$\therefore V_o = 1.5 + (-2) = -0.5 \text{ Volts}$$

(7) In this circuit show, V_{out}

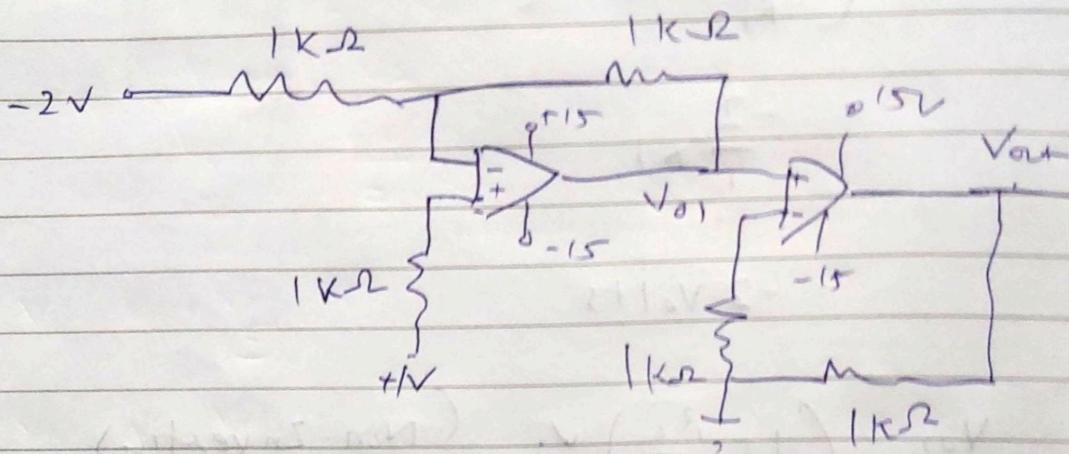

→ w.r.t op-amp-2
Non Inverting op-amp

$$V_{out} = \left(1 + \frac{R_f}{R_1}\right) V_{o1}$$

$$V_{out} = \left(1 + \frac{1}{1}\right) V_{o1}$$

$$V_{out} = 2V_{o1} \quad \text{--- (1)}$$

$$\rightarrow V_{o1} \rightarrow V_{o1} = V_{o1\ -2} + V_{o1\ r1} \quad (\text{Superposition})$$

V_{o1} due to -2 Volt

op-amp act as Inverting op-amp

$$V_{o1\ -2} = -\frac{R_f}{R_1} \Rightarrow V_{in} = (-1)(-2) = 2V_{o1\ t}.$$

V_o , due to +

→ Non Inverting op-amp.

$$V_o = \left(1 + \frac{R_f}{R_i}\right) V_{in}$$

$$\therefore (2)(1)$$

$$= 2$$

$$\therefore V_o = 2 + 2 \\ = 4 \text{ V}$$


$$\therefore V_{out} = 2V_o$$

$$= 2(4)$$

$$= 8 \text{ Volt}$$

⑧

Calculate CMRR.

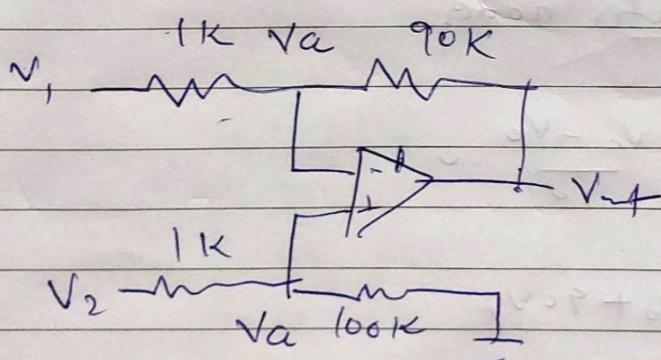

→

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|$$

$$V_o = A_d V_d + A_c V_c$$

$$\textcircled{A} \quad V_d = V_1 - V_2$$

$$V_c = V_1 + \frac{V_2}{2}$$

$$V_1 = V_c + \frac{V_d}{2}$$

$$V_2 = V_c - \frac{V_d}{2}$$

→ V_o In terms of V_1 & V_2

KCL at Non Invertor node,

$$\frac{V_a - V_2}{1} + \frac{V_a}{100} = 0$$

$$\therefore V_a = \frac{100}{101} V_2 \quad \textcircled{1}$$

KCL at Invertor node

$$\frac{V_a - V_1}{1} + \frac{V_c - V_o}{90} = 0$$

$$91V_a = V_o + 90V_c$$

$$91\left(\frac{100}{101}V_2\right) = V_o + 90V_c$$

$$91\left(\frac{100}{101}\left(V_c - \frac{V_d}{2}\right)\right) = V_o + 90\left(V_c + \frac{V_d}{2}\right)$$

$$\therefore V_o = \left(\frac{91(100)}{101} - 90 \right) V_c - \left(\frac{\frac{50}{91(100)}}{(101)(2)} - 45 \right) V_d$$

$$\therefore \left(\frac{9100 - 9090}{101} \right) V_c - \left(\frac{9100/29 - \frac{91(50) - 45}{(101)}}{101} \right) V_d$$

$$= \left(\frac{10}{101} \right) V_c + \left(-\frac{9095}{101} \right) V_d$$

$$V_o = A_d V_d + A_c V_c$$

$$A_d = -\frac{9095}{101}$$

$$A_c = \frac{10}{101}$$

$$(MRE) = \left| \frac{A_d}{A_c} \right|$$

$$= \left| \frac{-\frac{9095}{101}}{\frac{10}{101}} \right|$$

$$= \underline{909.5}$$

Q) An OPAMP has slew rate of $5 \text{ V}/\mu\text{s}$.
The largest sine wave output voltage possible at 1 MHz

$$\rightarrow \text{Slew-rate} = \frac{2\pi f \times V_m}{10^6} \text{ V}/\mu\text{s}$$

$$\begin{aligned} \text{SR} &= 5 \text{ V}/\mu\text{s} \\ f &= 1 \text{ MHz} \end{aligned}$$

$$\therefore \text{SR} = \frac{2\pi f V_m}{10^6}$$

$$5 = \frac{2\pi \times 1 \times 10^6}{10^6} \times V_m$$

$$\therefore V_m = \frac{5}{2\pi} \text{ Volts}$$

$$= \underline{0.79577 \text{ Volts.}}$$