

- ① Calculate the cut-off or breakpoint ( $f_c$ ) for a simple passive high pass filter consisting of an 82 pf capacitor in  $240\text{ k}\Omega R$

$$\rightarrow f_c = \frac{1}{2\pi \times R \times C}$$

$$= \frac{1}{2 \times 3.14 \times 82 \times 10^{-12} \times 240 \times 10^3}$$

$$= \frac{10^9}{2 \times 3.14 \times 82 \times 240}$$

$$= \underline{8.091 \text{ kHz}}$$

- ② For the 1<sup>st</sup> order butter worth HPF Calculate R if  $C = 0.0047 \mu\text{F}$ ,  $f_c = 10 \text{ kHz}$

$$\rightarrow f_c = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi f_c C}$$

$$= \frac{1}{2 \times 3.14 \times 10 \times 10^3 \times 0.0047 \times 10^{-6}}$$

$$= \frac{10^3}{2 \times 3.14 \times 10 \times 0.0047}$$

$$= 3.3879 \text{ k}\Omega$$

③ Design a HPF circuit for 10kHz cut-off frequency.

$$\rightarrow f_c = 10 \text{ kHz}$$


- R can vary from 1-10 kΩ

④ Let's take 10 kΩ

$$\begin{aligned} C &= \frac{1}{2\pi R f_c} \\ &= \frac{1}{2 \times 3.14 \times 10 \times 10^3 \times 10 \times 10^3} \\ &= 1.59 \text{nF} \end{aligned}$$


Now, Reverse
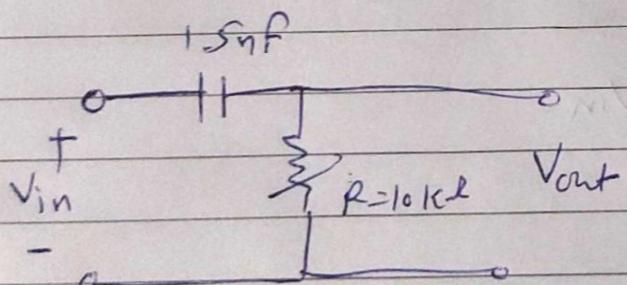
$$f_c = \frac{1}{2\pi R C} = \frac{1}{2 \times 3.14 \times 10^4 \times 1.5 \times 10^{-9}} = 10.61 \text{ k}\Omega$$



② Let's take 5 kΩ
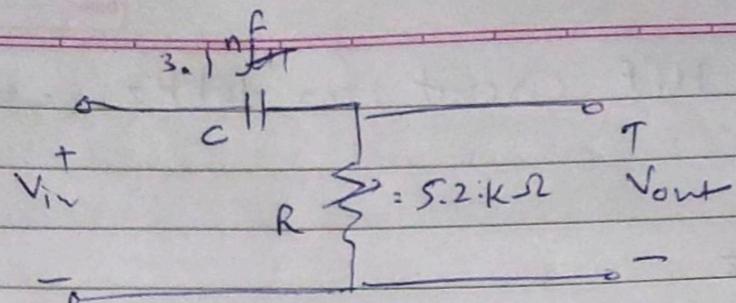
$$\therefore C = \frac{1}{2\pi R f_c} = 3.18 \text{nF} \quad \therefore \text{Reverse } f_c = 5.2 \text{ k}\Omega$$




$\Sigma \rightarrow$  Variable Resistance

$$\text{for } 10 \text{ k}\Omega \rightarrow 3.18 \text{ nF} \rightarrow 10.61 \text{ k}\Omega$$

$$5 \text{ k}\Omega \rightarrow 3.18 \text{ nF} \rightarrow 5.21 \text{ k}\Omega$$

- (i) A Low pass filter circuit consr. of A resistor of  $4.7 \text{ k}\Omega$  in series with a Capacitor of  $47 \text{ nF}$  is connected across  $10\text{V}$ .  $V_{out} = (?)$

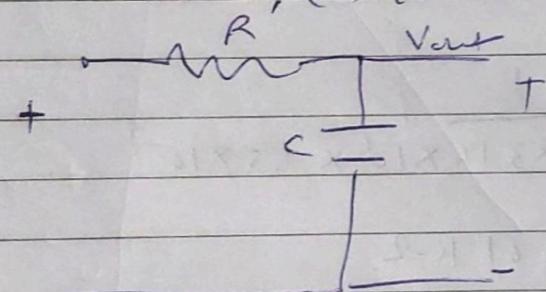(i)  $f = 100 \text{ Hz}$ , (ii)  $10000 \text{ Hz}$  (~~101~~)



$$\rightarrow V_{out} = \frac{X_C}{\sqrt{X_C^2 + R^2}} \times V_{in}$$

$$\text{Now. } X_C = \frac{1}{\omega C}$$

$$= \frac{1}{2 \times 3.14 \times 100 \times 47 \times 10^{-9}}$$

$$= \frac{10^7}{2 \times 3.14 \times 47} = 33.879 \text{ k}\Omega$$

$$V_{out} = 10 \times \frac{33.879 \times 10^3}{\sqrt{(33.879)^2 + (4.7)^2} \times 10^3}$$

$$= \underline{9.9 \text{ Volt}}$$

(ii)  $f = 10 \text{ kHz}$


$$X_C = \frac{1}{2 \times 3.14 \times 10 \times 10^3 \times 4.7 \times 10^{-7}}$$

$$= 0.338 \text{ k}\Omega$$

$$\therefore V_{out} = 10 \times \frac{0.338 \times 10^3}{\sqrt{(0.338)^2 + (4.7)^2}}$$

$$= \underline{0.718 \text{ Volt}}$$

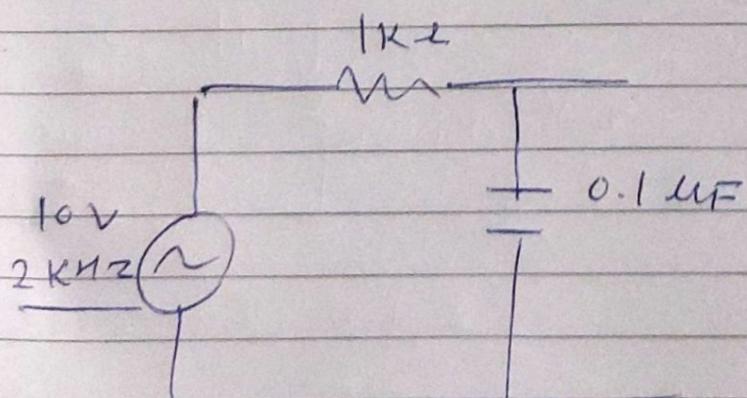
⑤ For the given LPF find the -3 dB frequency &  $V_{out}$  at 2 kHz.  
Also plot the frequency response characteristics for the given LPF.




$$f_c = \frac{1}{2\pi R C} = \frac{1}{2 \times 3.14 \times 1 \times 0.1 \text{ MF}} \\ = 1.59 \text{ KHz}$$

$$V_{out} = V_{in} \times \frac{X_C}{\sqrt{R^2 + X_C^2}} \quad X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 1.59 \times 0.1 \text{ MF}} \\ = 10 \times \frac{7.96178 \times 10^5}{\sqrt{(7.96178 \times 10^5)^2 + (10^3)^2}} \\ = 6.22 \text{ Volt}$$


$\approx 0.796178 \times 10^6 \Omega$

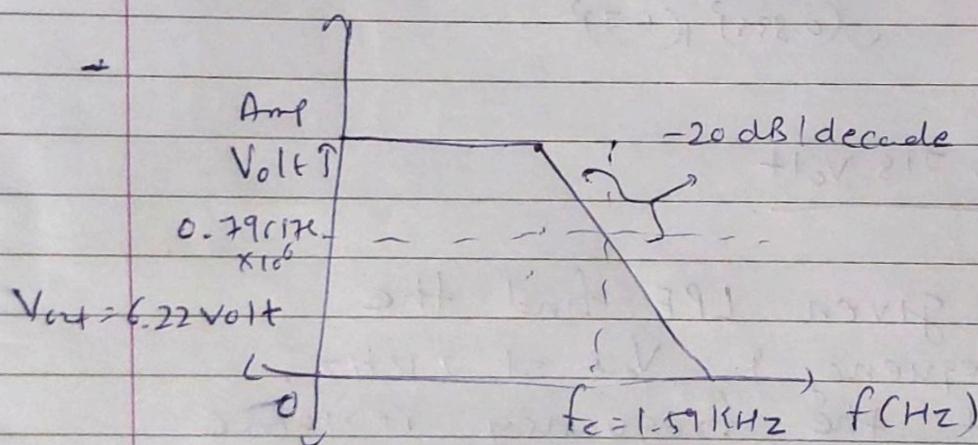

(6)

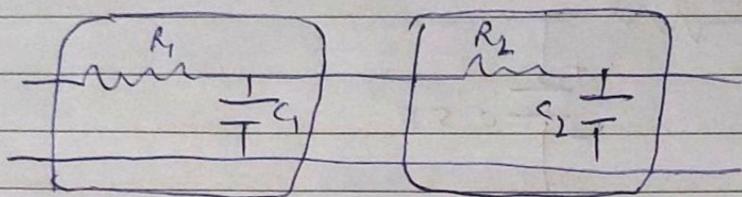
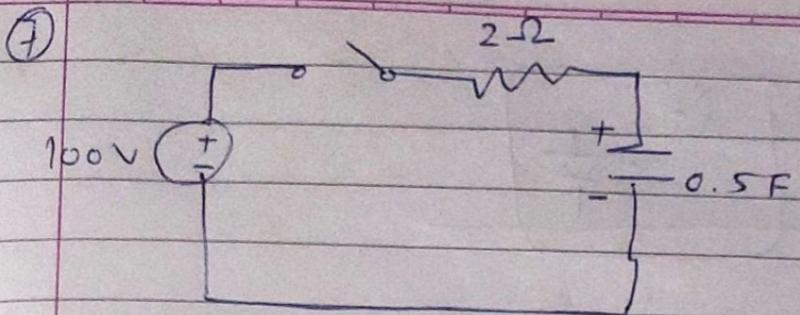
$$f_c = \frac{1}{2\pi\sqrt{R_1 C_1 R_2 C_2}} = \frac{1}{2\pi R_1 C_1}$$



$$\rightarrow Q = 10 \text{ C} \quad i_{\text{sec}} = (?)$$

Now, Initially  $V = \frac{Q}{C}$

$$= \frac{10}{0.5}$$

$$= 20 \text{ V}$$

$$\text{So } I_0 = \frac{100 - 20}{2} \\ = 40 \text{ A}$$

$$\text{Now, } I(t) = i_0 e^{-t/RC}$$

$$RC = 2 \times 0.5 = 1 \Omega$$

$$\therefore I = 40 - e^{-t/1}$$

$$= \underline{14.71 \text{ A}}$$