



Expt. No:

2

Date:

Diode Clipper Circuits

U20CS100_ADITYA_RAJ

AIM: To implement various diode clamper circuits and verify its performance using Multi-Sim software

SOFTWARE TOOLS / OTHER REQUIREMENTS:

1. Multisim Simulator/Circuit Simulator
-

THEORY:

A clamper is a network constructed of a diode, a resistor, and a capacitor that shifts a waveform to a different dc level without changing the appearance of the applied signal.

Additional shifts can also be obtained by introducing a dc supply to the basic structure. The resistor and capacitor of the network must be chosen such that the time constant determined by $\tau=RC$ is sufficiently large to ensure that the voltage across the capacitor does not discharge significantly during the interval the diode is not conducting. Throughout the analysis we assume that for all practical purposes the capacitor fully charges or discharges in five-time constants. The simplest of clamper networks is shown in figure below.

Clamping networks have a capacitor connected directly from input to output with a resistive element in parallel with the output signal. The diode is also in parallel with the output signal but may or may not have a series dc supply as an added element.


Six type of clamper circuits are as follows:




1. POSITIVE CLAMPER
2. POSITIVE CLAMPER WITH POSITIVE V_T
3. POSITIVE CLAMPER WITH NEGATIVE V_T
4. NEGATIVE CLAMPER
5. NEGATIVE CLAMPER WITH POSITIVE V_T
6. NEGATIVE CLAMPER WITH NEGATIVE V_T

CIRCUIT DIAGRAMS


1. POSITIVE CLAMPER CIRCUIT:

 


2. POSITIVE CLAMPER WITH POSITIVE V_T

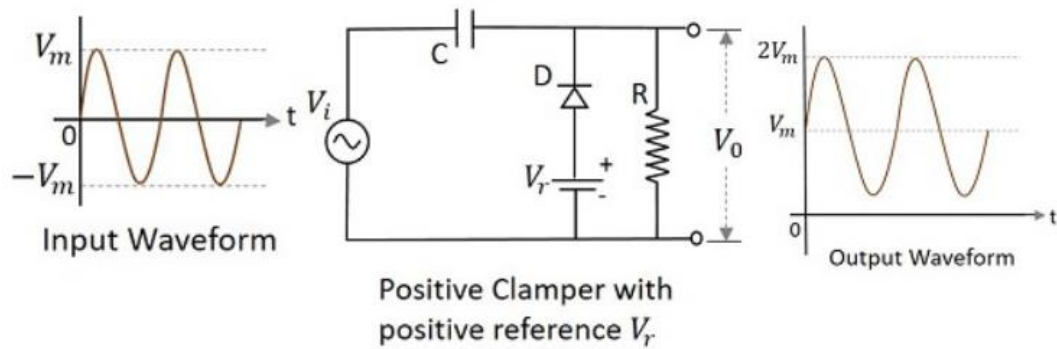


3. POSITIVE CLAMPER WITH NEGATIVE VT

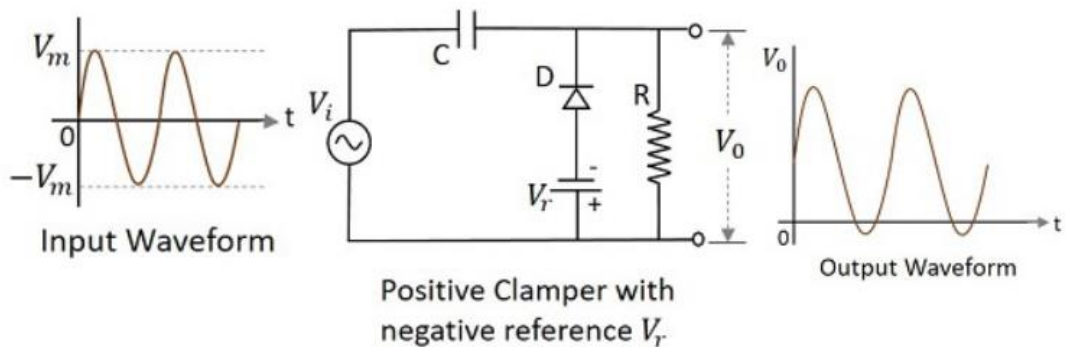


4. NEGATIVE CLAMPER

 

5 NEGATIVE CLAMPER WITH POSITIVE VT

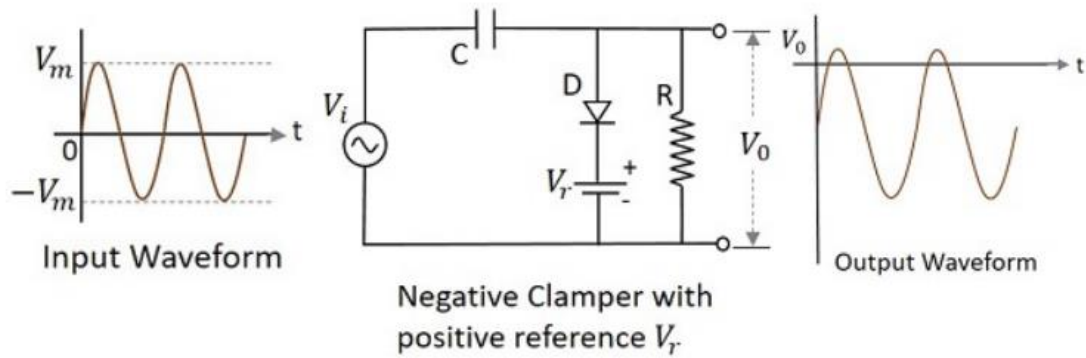


6 NEGATIVE CLAMPER WITH NEGATIVE V_r

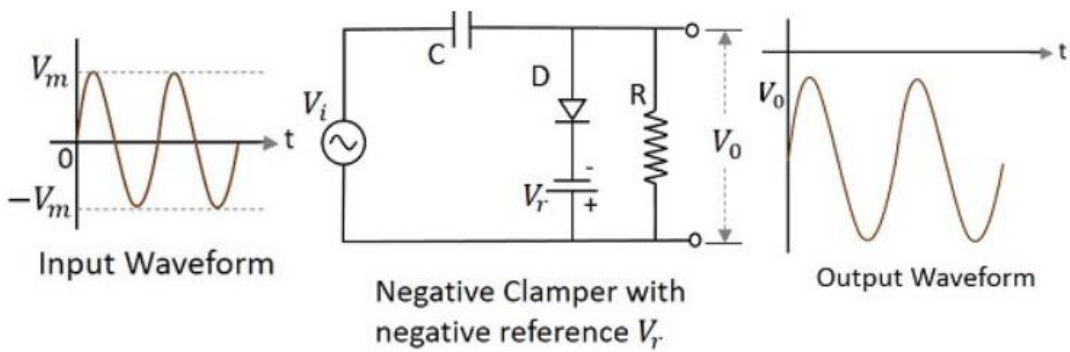

 1) POSITIVE CLAMPER

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)





CALCULATIONS:

Let V_c be the voltage of capacitor:

CASE 1: For interval $0 < t < T/2$

Diode is reversed biased, so it will act like open circuit in ideal condition.

By applying Kirchhoff's voltage law:

$$V_i + V_c - V_o = 0$$

$$V_o = V_i + V_c$$

$$V_o = 2V_i = 30V$$

CASE 2: For interval $T/2 < t < T$

Diode is forward biased, so it will act like short circuit in ideal condition.


By applying Kirchhoff's voltage law:

$$-V_i + V_c - V_o = 0$$

$$V_c = 15V$$

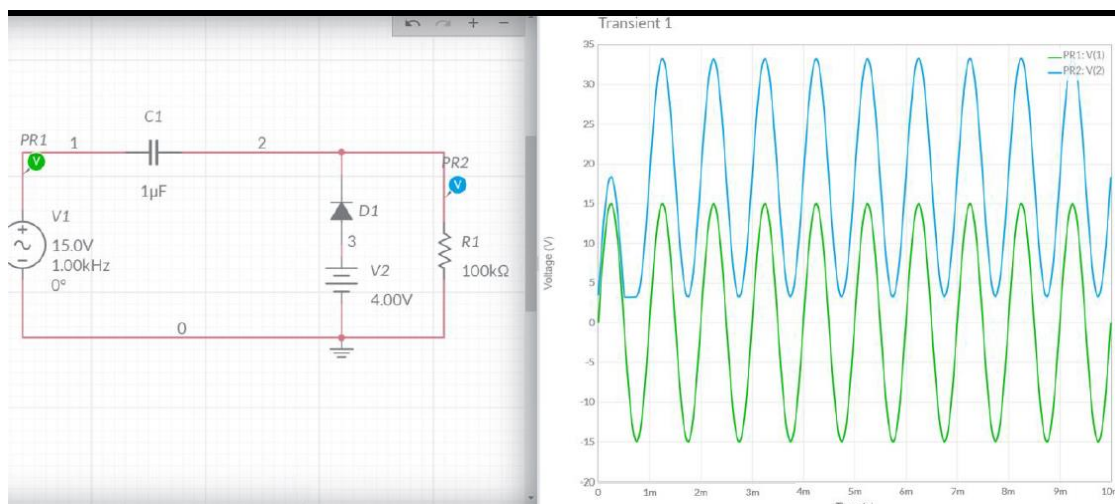2) POSITIVE CLAMPER CIRCUIT WITH POSITIVE REFERENCE

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)





CALCULATIONS

CASE 1: For interval $0 < t < T/2$

Diode is reversed biased, so it will act like open circuit in ideal condition.

By applying Kirchhoff's voltage law:

$$V_i + V_c - V_o = 0$$

$$V_o = V_c + V_i$$

$$= 15V + 19V = 34V$$

CASE 2: For interval $T/2 < t < T$

Diode is forward biased, so it will act like short circuit in ideal condition.


Assume that capacitor will charge p instantaneously to a voltage level determined by the surrounding network. As diode is short circuited $V_o = V_r = 4V$

Applying KVL: $-V_i + V_c - V_o = 0$

$$V_c = 19V$$

 3) POSITIVE CLAMPER CIRCUIT WITH NEGATIVE REFERENCE

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)





CALCULATIONS:

CASE 1: For interval $0 < t < T/2$

Diode is reversed biased so will act as open circuit.

Applying KVL:

$$V_i + V_c - V_o = 0$$

$$V_o = 15V + 11V = 26V$$

CASE 2: For interval $0 < t < T/2$

Diode is forward biased.


Assume that capacitor will charge p instantaneously to a voltage level determined by the surrounding network. As diode is short circuited $V_o = V_r = -4V$

Applying KVL: $-V_i + V_c - V_o = 0$

$$V_c = 11V$$

 4) NEGATIVE CLAMPER

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)





CALCULATIONS:

Case-1: For interval $0 < t < T$

Assume that capacitor will charge p instantaneously to a voltage level determined by the surrounding network. As diode is short circuited $V_o = 0$

Voltage across capacitor V_c : Applying KVL: $V_i - V_c - V_o = 0$

$$V_c = -15V$$

Case-2) For interval $T/2 < t$

Diode is reverse bias.

As diode is open circuited


Applying KVL : $-V_i - V_c - V_o = 0$

$$V_o = -V_i - V_i$$

$$V_o = -2V_i = -30V$$

 5) NEGATIVE CLAMPER CIRCUIT WITH POSITIVE REFERENCE

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)



CALCULATIONS:



Case-1) For interval $0 < t < T/2$

Diode is forward bias. Assume that capacitor will charge p instantaneously to a voltage level determined by the surrounding network.

As diode is short circuited $V_o = V_r = 4V$

Voltage across capacitor V_c :

Applying KVL: $V_i - V_c - V_o = 0$

$V_c = 11V$

Case2: For interval $T/2 < t < T$

Diode is reversed biased.

As diode is open circuited.


Applying KVL: $V_i - V_c - V_o = 0$

$V_o = -V_c - V_i$

$V_o = -11V - 15V = -26V$

 6) NEGATIVE CLAMPER CIRCUIT WITH NEGATIVE REFERENCE

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)





CALCULATIONS:

Case-1) For interval $0 < t < T/2$

Diode is forward bias. Assume that capacitor will charge p instantaneously to a voltage level determined by the surrounding network

As diode is short circuited $V_o = V_r = -4V$

Voltage across capacitor V_c :

Applying KVL: $V_i - V_c - V_o = 0$

$$V_c = 19V$$

Case-2) For interval $T/2 < t < T$:

Diode is reverse bias.

As diode is open circuited

Applying KVL : $-V_i - V_c - V_o = 0$

$$V_o = -V_c - V_i$$

$$V_o = -19V - 15V = -34V$$


CONCLUSIONS

Here, the practical and theoretical characteristics of various negative and positive clamper (with and without bias) are same. Hence verified.

ASSIGNMENT


QUESTION 1:

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)

 


QUESTION 2:

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)

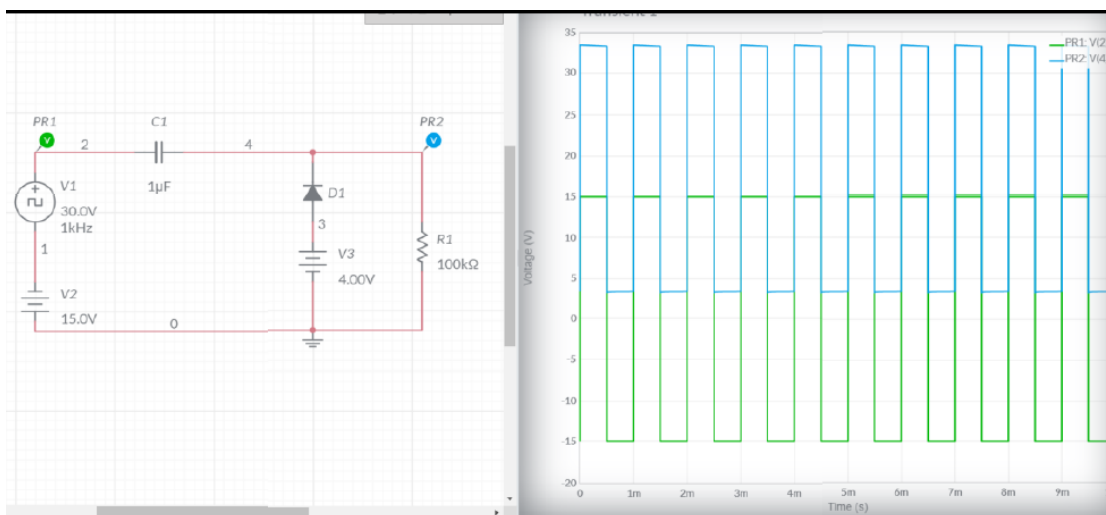

QUESTION 3:


CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)

 




QUESTION 4:

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)

 

QUESTION 5:

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)

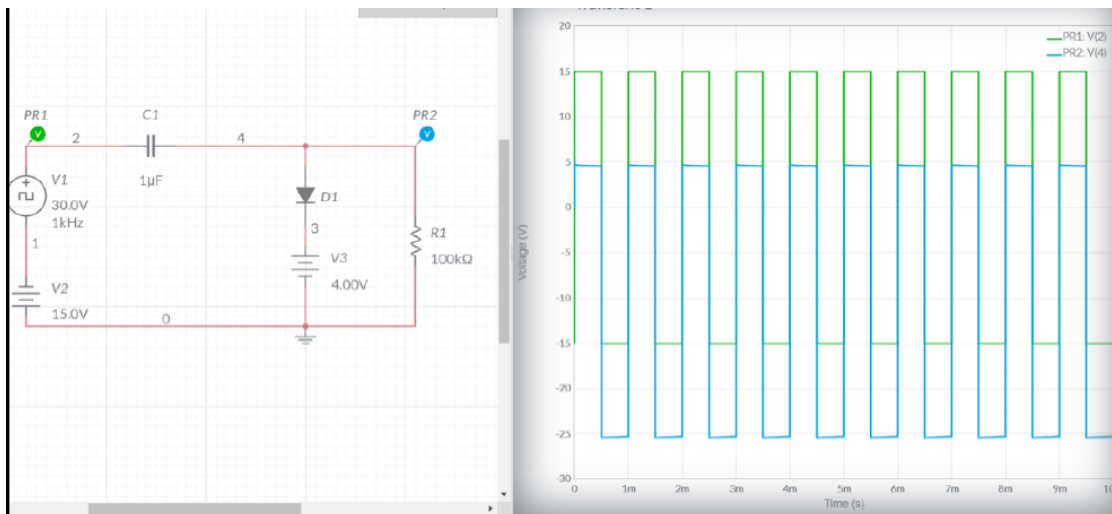

QUESTION 6:

CIRCUIT/CONNECTION DIAGRAMS (FROM MULTISIM)

