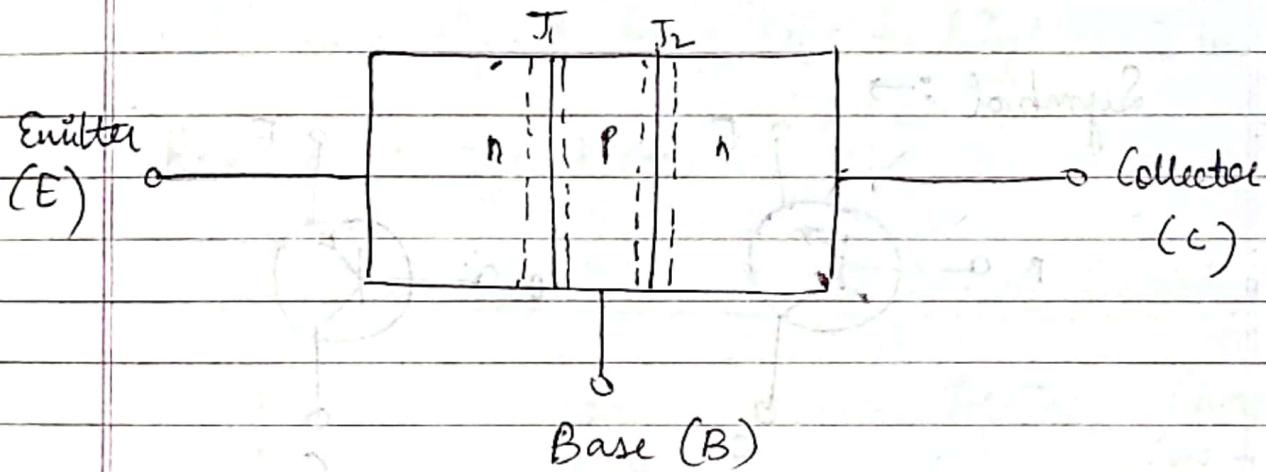



TRANSISTOR

- Three layer semiconductor device, either with two n and one P material, or two p type and one n-type material.
- Former is npn, latter is pnp
- There are 3 terminals, one taken from each semiconductor
- Middle layer is thin as compared to the other two.



$J_1 \rightarrow$ Emitter - Base junction

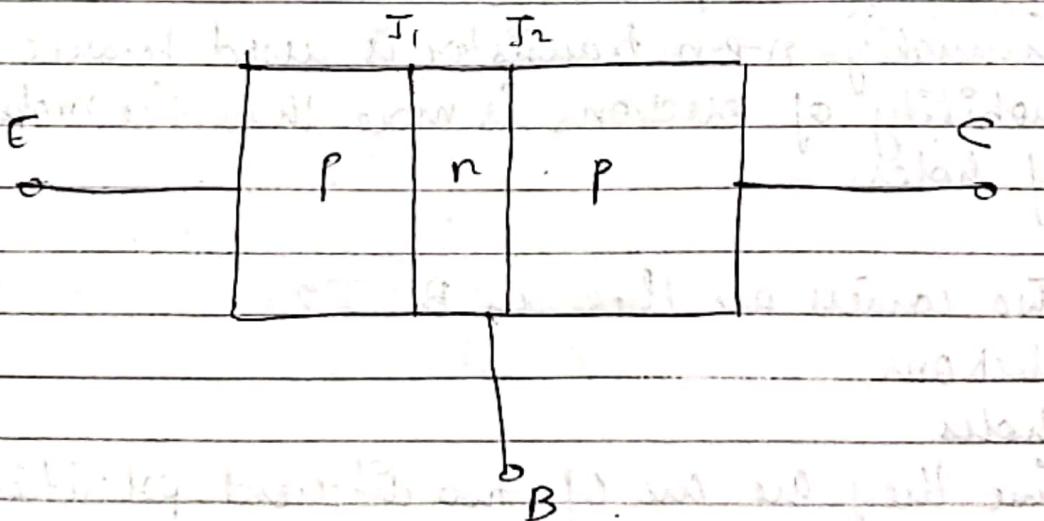
$J_2 \rightarrow$ Base - Collector junction




Width: $C > E > B$

Doping: $E > C > B$

Cross Section View $B \rightarrow$

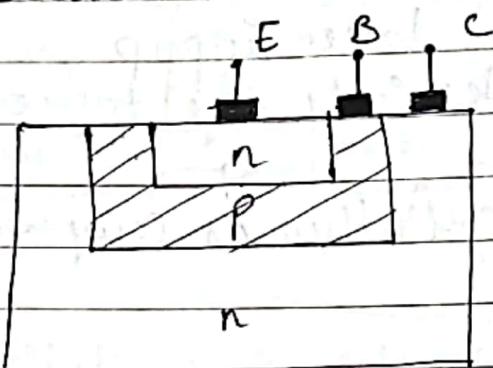

Symbol: \rightarrow

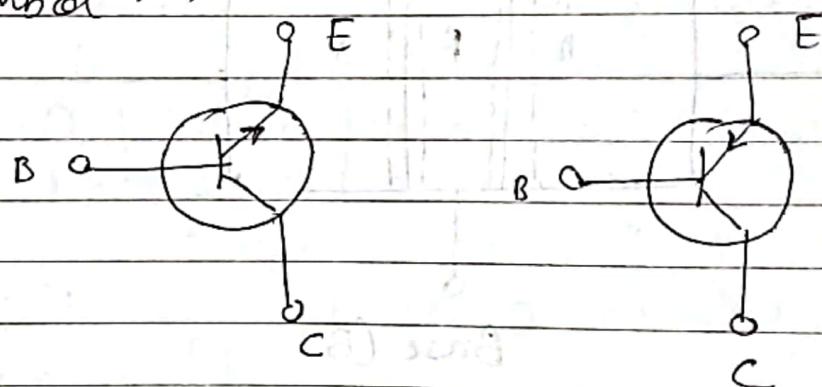

- Transistor can be considered as two diodes connected back to back.
- Generally n-p-n transistor is used because the mobility of electrons is more than the mobility of holes.

Two carriers are there in BJT:

- electrons
- holes

Since they are one of two different polarities

transistors are called Bipolar.

Also;

$$\text{TRANSISTOR} = \text{TRANSFER} + \text{RESISTOR}$$

If J_1 is \rightarrow Forward Bias

\rightarrow It offers low resistance

J_2 is \rightarrow Reverse Bias

\rightarrow It offers high resistance

Weak signal is introduced at low resistance & output is taken at high resistance. Thus BJT transfers signal from low to high resistance.

Regions of operation:

J_1

J_2

Region of Operation

F.B R.B

F.B F.B

R.B R.B

R.B F.B

Active (Amplifier)

Saturation (ON - closed switch)

Cut-off (OFF \rightarrow open circuit)

Inverted (rarely used)


J_1, J_2 reverse
their roles.

Active mode:

Ideal Condition \rightarrow


- $J_1 \rightarrow F.B$ Resistance = 0

- $J_2 \rightarrow R.B$ $R = \infty$

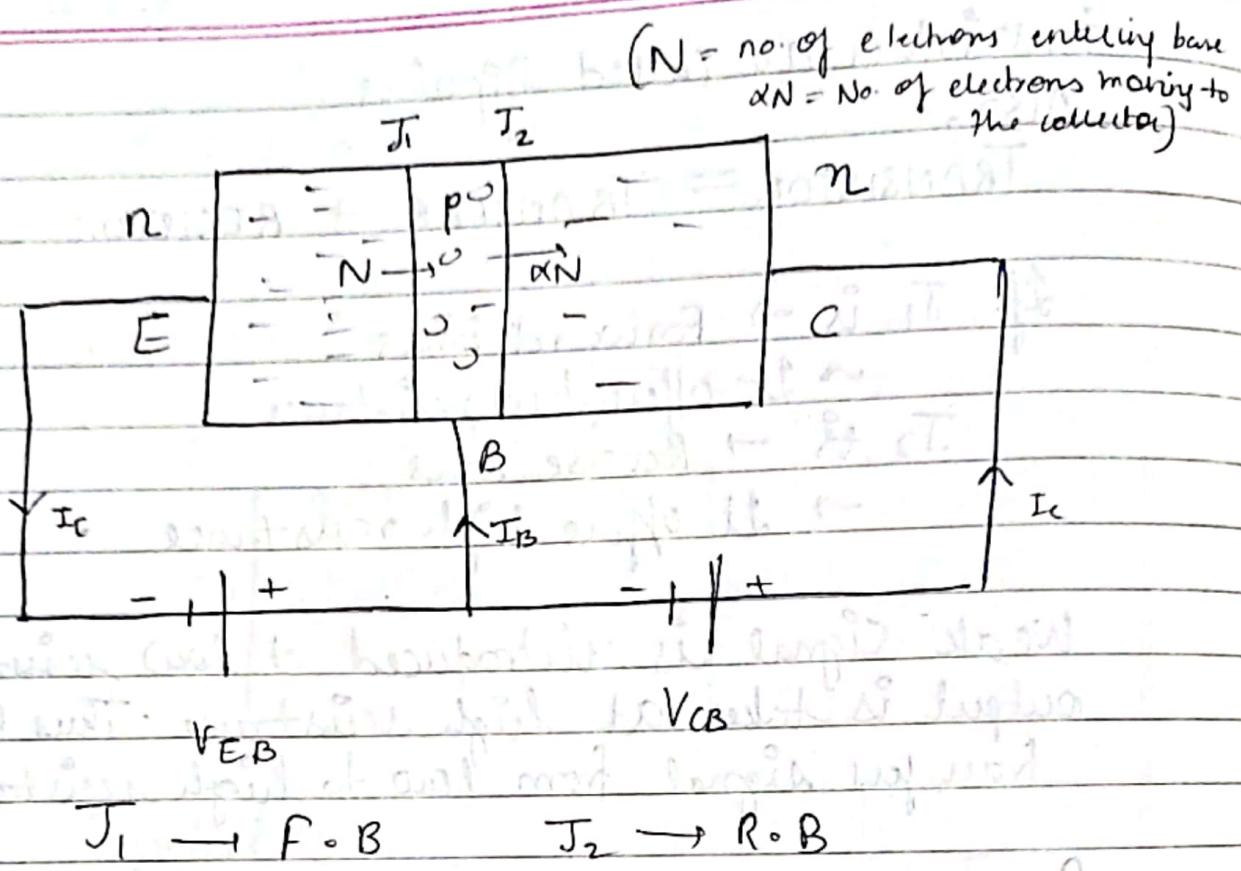

Initially before biasing, the barrier potential of junction J_1, J_2 was V_b .

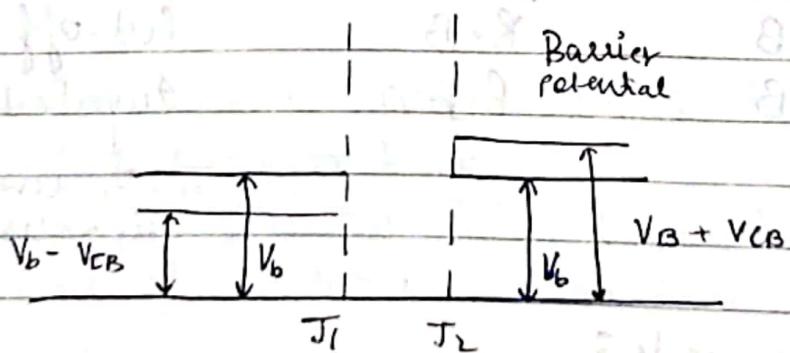After biasing : As J_1 is in F-B, its barrier potential decreases while that of J_2 increases.



Because of the reduced barrier potential of J_1 , electrons at emitter side will move to the base and recombine with holes in base.

Base → very small, lightly doped

Since base is very small and lightly doped there is very little recombination here. So most e⁻ will cross junction J₂ and they have high velocity, high kinetic energy. Only 2-5% e⁻ recombine in the base and 95-98% move to the collector.

Also since J₂ is reverse biased, there must be reverse saturation current. In collector minority charge carriers is holes, on p side electrons. So holes move towards base and get pulled to collector. This reverse saturation current is also known as leakage current when J₂ is R.B.

I_{Co} = leakage current

(We measure this current when emitter terminal is open circuited)

$$I_c = \alpha I_E + I_{Co}$$

By KCL:


$$I_E = I_B + I_C$$

Configurations:

- i) Common Base
- ii) Common Emitter
- iii) Common Collector

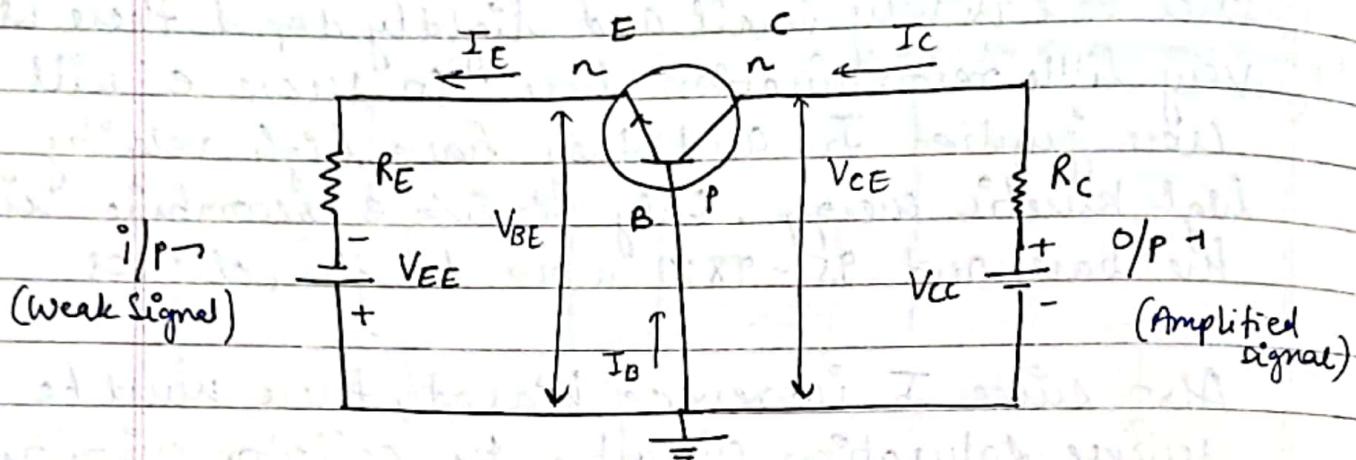- i) Common Base:

Base is common in CB config. and it is grounded.



→ There is amplification of weak signal in active mode

$J_1 \rightarrow F.B$

$J_2 \rightarrow R.B$

I/p characteristics: I_E vs V_{BE}

O/p characteristics: I_C vs V_{CE}

- If we neglect $R_C \rightarrow V_{CE} = V_{BE}$

- If we neglect $R_E \rightarrow V_{CE} = V_{CC}$

{
 $V_{BE} \rightarrow$ Emitter at lower potential
 ↑
 Base at higher potential }
 $V_{CE} X$

By KCL:

$$I_E = I_B + I_C \quad \text{--- (1)}$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E \gg I_{CBO}$$

$$\therefore I_C = \alpha I_E \quad \text{--- (2)}$$

$$\boxed{\alpha = \frac{I_C}{I_E}}$$

$\alpha \Rightarrow$ Common base current gain / Amplification factor
 Range of $\alpha \Rightarrow 0.95$ to 0.95

From ①, ②


$$I_B = (1-\alpha) I_E$$

Input Characteristics

i/p current $\Rightarrow I_E$ i/p voltage $\Rightarrow V_{BE}$

o/p current $\Rightarrow I_C$ o/p voltage $\Rightarrow V_{CB}$

I_E (mA)

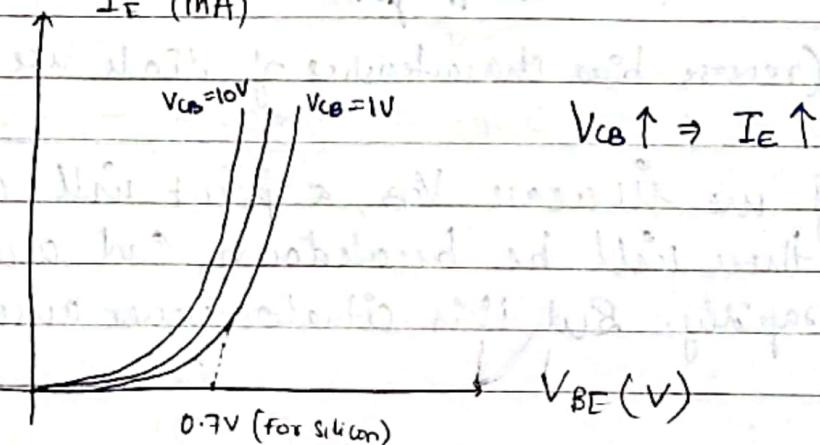

Early Effect:

$$W_B = W_{eff} + W$$

$$W_{eff} = W_B - W$$

On increasing V_{CB} , reverse bias


will increase so penetration of

depletion layer in base will increase &
 hence W will increase.

$$W \uparrow \Rightarrow W_{eff} \downarrow$$


$W_{eff} \rightarrow$ Region where recombination takes place.

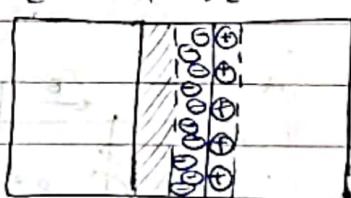Chance of recombination reduces, $I_E \uparrow$



$$\text{So } V_{CB} \uparrow \Rightarrow I_E \uparrow$$


Output Characteristics

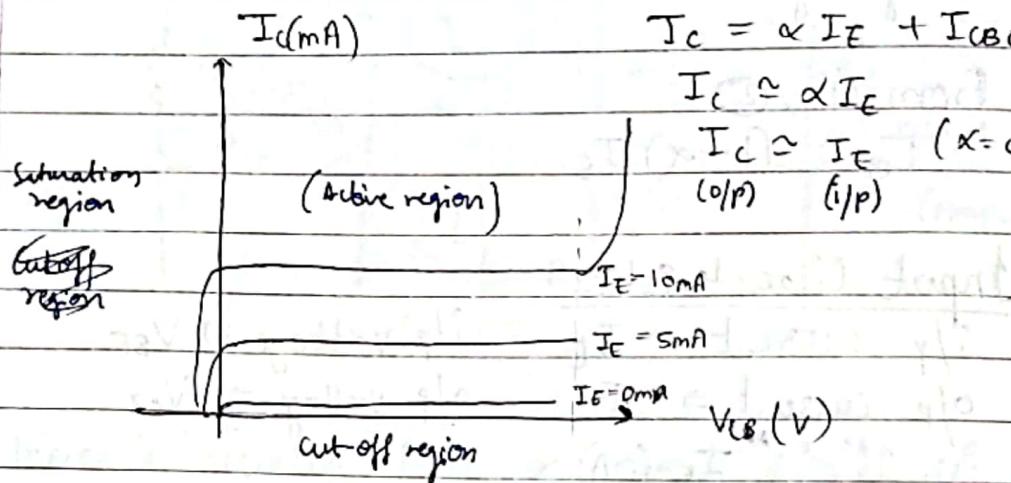

(reverse bias characteristics of diode like graph)

- ~ If we increase V_{CE} , a point will come where there will be breakdown and current will increase rapidly. But this situation never arises in transistor.

Amplifying Actions

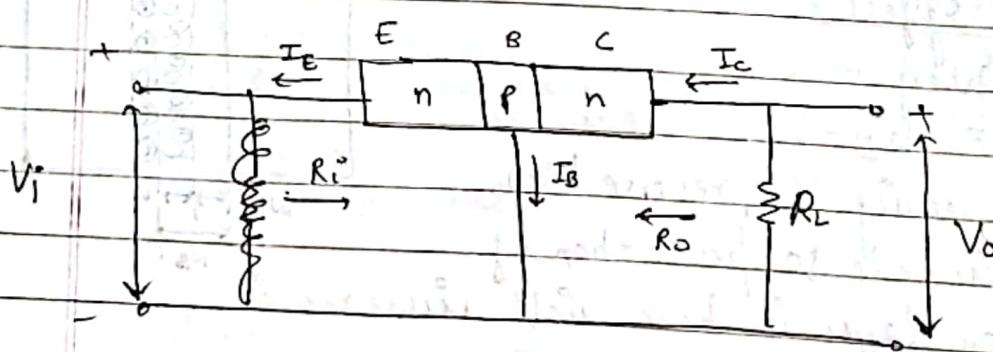

I/P Chanc \Rightarrow

$$\text{Slope} = \frac{1}{R_p} \quad (R_i = \text{very small})$$

O/P Charact. =)

$$\text{Slope} = \frac{1}{R_o} \quad (\text{very large } R_o)$$

Taking $V_i = 200\text{mV}$, $R_L = 5\text{k}\Omega$, $R_i = 20\Omega$,
 $R_o = 100\text{k}\Omega$, $V_o = ?$

$$V_i = I_E R_i \Rightarrow I_E = \frac{V_i}{R_i}$$

$$I_E = \frac{200\text{mV}}{20\Omega} = 10\text{mA}$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_C \approx \alpha I_E$$

$$I_C \approx I_E$$

$$I_C = 10\text{mA}$$

$$V_o = I_C R_L$$

$$= 10\text{mA} \times 5\text{k}\Omega$$

$$V_o = 50\text{V}$$

$$V_i = 200\text{mV} \quad V_o = 50\text{V}$$

Amplification

$$A_v = \frac{V_o}{V_i}$$


$$A_v = \frac{50\text{V}}{200\text{mV}} = 50$$

→ Input voltage is amplified 50 times

→ Range of A_v : 50 - 300

→ Range α : 0.95 - 0.99

Common Emitter (Mostly used)

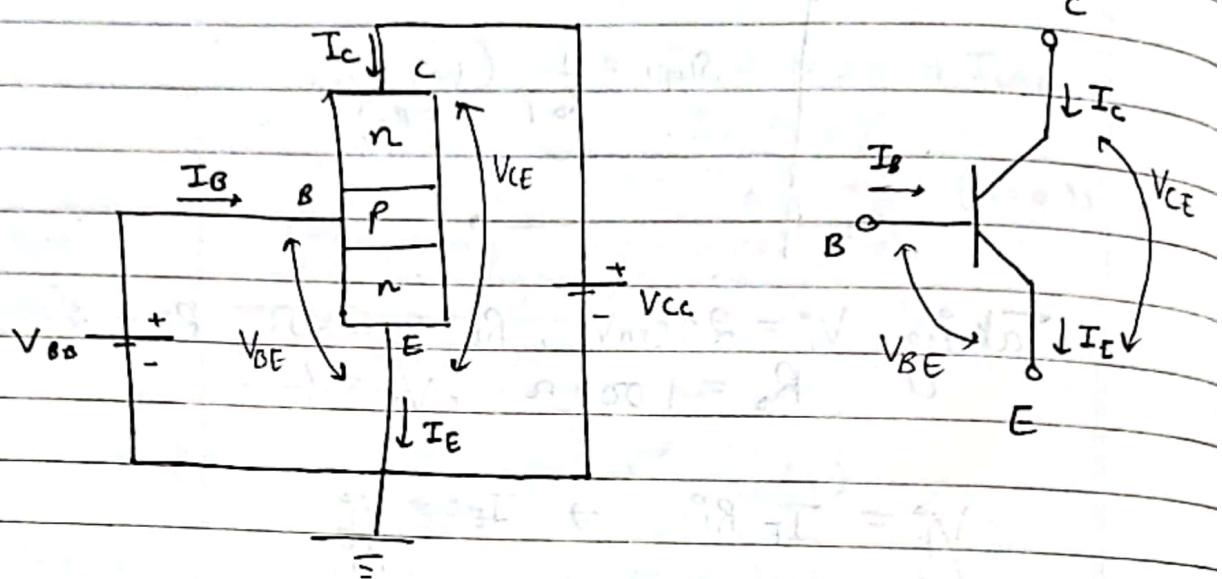

i/p current $\rightarrow I_B$

i/p volt $\rightarrow V_{BE}$

o/p current $\rightarrow I_C$

o/p volt $\rightarrow V_{CE}$

KCL:

$$I_E = I_C + I_B \quad \text{--- (1)}$$

$$I_C = \alpha I_E + I_{CBO} \quad \text{--- (2)}$$

{ These 2 relations are true for any transistor connection }

$$I_C = \alpha (I_C + I_B) + I_{CBO}$$

$$I_C = \alpha I_C + \alpha I_B + I_{CBO}$$

$$(1 - \alpha) I_C = \alpha I_B + I_{CBO}$$

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CBO}$$

$$\boxed{\frac{\alpha}{1 - \alpha} = \beta}$$

$$\beta + 1 = \frac{\alpha}{1 - \alpha} + 1$$

$$\boxed{\beta + 1 = \frac{1}{1 - \alpha}}$$

$$I_c = \beta I_B + (\beta + 1) I_{CBO}$$

$$\left. \begin{aligned} &\Rightarrow \alpha < 1 \\ &\Rightarrow \beta \text{ range} \Rightarrow 50 \text{ to } 400 \end{aligned} \right\}$$

$$(\beta + 1) I_{CBO} = I_{CEO}$$

$$I_c = \beta I_B + I_{CEO}$$

$$I_{CEO} \ll \beta I_B$$


$$I_c = \beta I_B$$

$$\boxed{\beta = \frac{I_c}{I_B}}$$

$\beta \rightarrow$ Current amplification factor


- \Rightarrow CE Configuration works as current amplifier
- \Rightarrow leakage current (I_{CBO}) has more contribution in CE Config and less contribution in CB Config.
- \Rightarrow Used as CURRENT BUFFER

Input Characteristics:

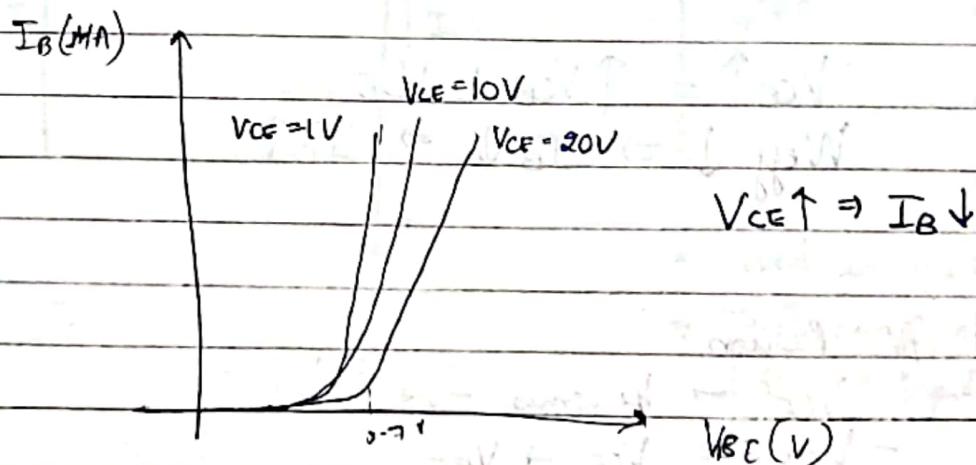

Early effect: $V_{CE} \uparrow \Rightarrow V_{CB} \uparrow \Rightarrow W_{eff} \downarrow \Rightarrow W \uparrow \Rightarrow \underline{\underline{I_B \downarrow}}$

Output Characteristics

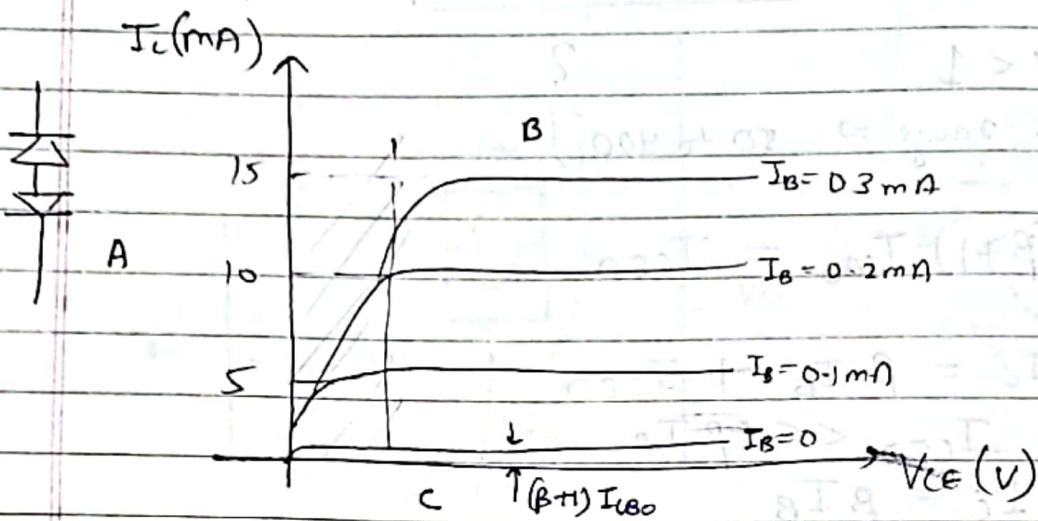

$$I_c = \beta I_B + (\beta + 1) I_{CBO}$$

(when $I_B = 0$)

$$I_c = (\beta + 1) I_{CBO}$$

$$I_B = 0.1 \text{ mA} \rightarrow I_c = 5 \text{ mA}$$

$$I_B = 0.2 \text{ mA} \rightarrow I_c = 10 \text{ mA}$$

$$\beta = \frac{\Delta I_c}{\Delta I_B} = \frac{10 - 5}{0.2 - 0.1} = 50$$

$$V_{CE} \uparrow = \uparrow V_{CB} + V_{BE}$$

$$\text{Weg } \downarrow \Rightarrow I_B \downarrow \Rightarrow I_c \uparrow$$

A Region:

$V_{CE} \rightarrow$ becomes -ve

$$-V_{CE} = V_{CB} + V_{BE}$$

$$V_{CB} = -V_{CE} - V_{BE}$$

V_{CB} is now (-ve) which means V_{CB} is

now it is forward bias and direction of I_C will change. A is saturation region. Some of the shaded region is also a part of this because $V_{CE} > 0$ but it is very small so V_{CB} is still (-ve).


Region B :

It is active region because there is amplification of input signal.

Region C :

$I_B < 0 \Rightarrow$ So the direction Base current changes. Both diodes are reverse biased. This happens in cut-off region.

Common Collector

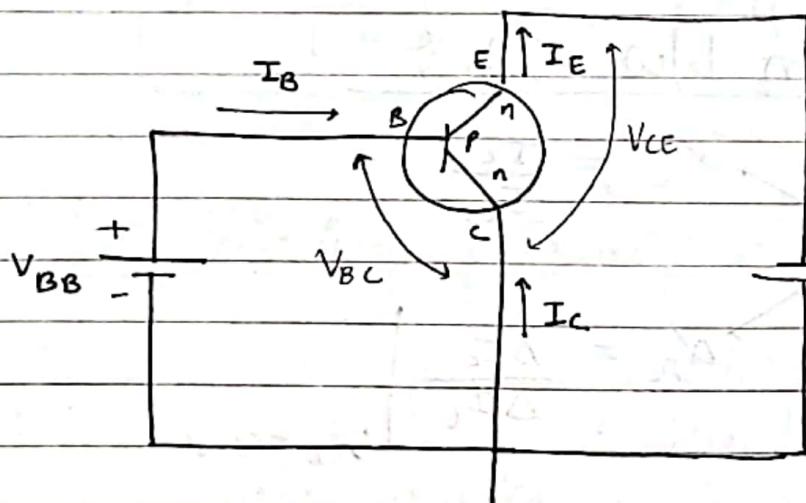

$$\text{O/P Current} = I_C$$

$$\text{O/P voltage} = V_{CE}$$

$$\text{I/P current} = I_B$$

$$-\text{i/P voltage} = V_{BE}$$

- Used as voltage Buffer
- This configuration has highest input impedance

$$I_C = \alpha I_E$$

$$\alpha = 0.95 \text{ to } 0.98$$

$$I_C \approx I_E$$

$$V_{CE} = V_B + V_{BE}$$

c/p characteristics of CE = o/p of CC
as ($I_C \approx I_E$)

ϑ = current amplification

$$\boxed{\vartheta = \frac{\Delta I_E}{\Delta I_B}}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = \alpha I_E + I_B + I_{CBO}$$

$$(1 - \alpha) I_E = I_B + I_{CBO}$$

$$I_E = \frac{1}{1-\alpha} I_B + \frac{1}{1-\alpha} I_{CBO}$$

$$(I_E = \vartheta I_B + \vartheta I_{CBO})$$

Relation b/w α, β, ϑ

$$\alpha_{DC} = \frac{I_C}{I_E}$$

$$\alpha_{AC} = \frac{\Delta I_C}{\Delta I_E} \quad | V_{CB} = \text{const}$$

$$\beta_{DC} = \frac{I_C}{I_B}$$

$$\beta_{AC} = \frac{\Delta I_C}{\Delta I_B} \quad | V_{CE} = \text{const}$$

$$V_A = \frac{I_E}{I_B}$$

$$V_m = \frac{\Delta I_E}{\Delta I_B} \quad |_{V_{CC} = \text{const}}$$

$$I_C = I_C + I_B$$

$$\frac{I_E}{I_B} = \frac{I_C}{I_B} + \frac{I_B}{I_B}$$

$$V = \beta + 1$$

$$\beta = \frac{\alpha}{1-\alpha}$$


$$V = \frac{1}{1-\alpha}$$

$$V = \beta + 1$$

DC Biasing of Transistors


Biasing is the process in which we apply external DC voltages to establish the desired operation point. These networks are biasing networks.

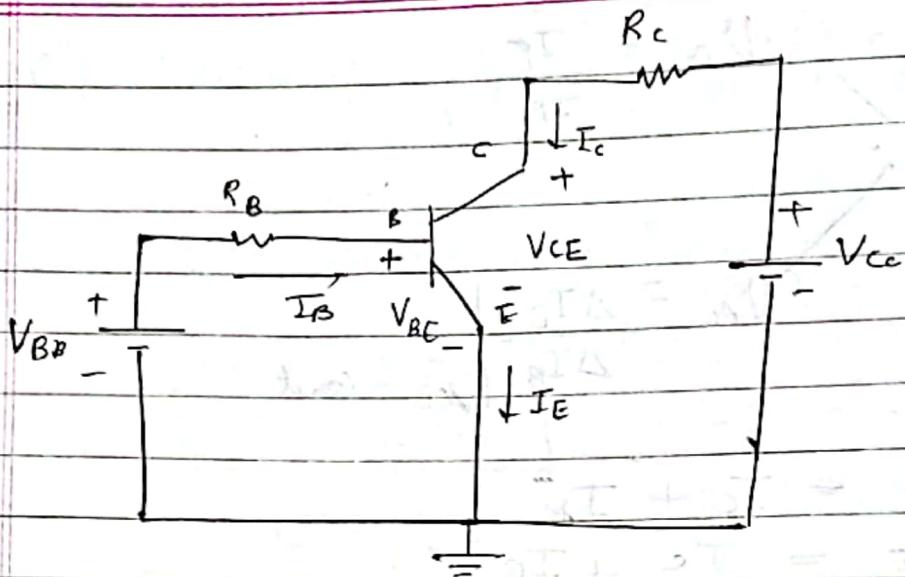- Active Region
- Saturation Region
- Cut-off region
(npr C_E)



→ If we apply an input signal, we want the output signal without any distortion. We do not want any portion of output waveform to be clipped this is faithful amplification of input signal.

i/p operating pt →

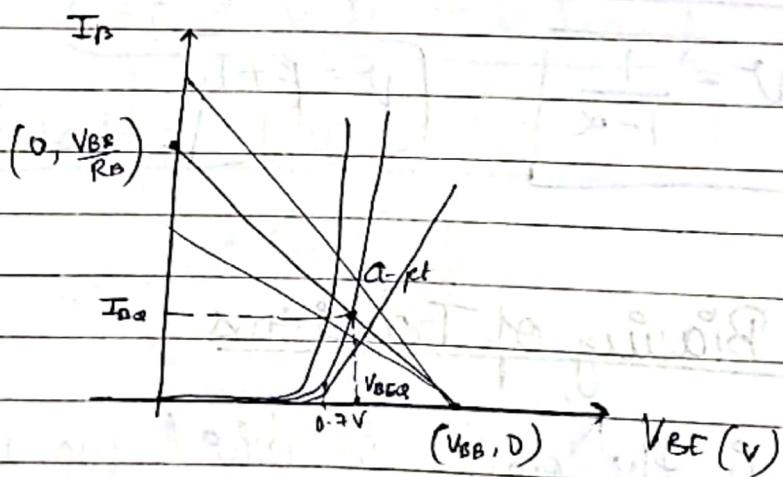

KVL :


$$V_{BB} - I_B R_B - V_{BE} = 0$$

when $V_{BE} = 0$, $I_B = V_{BB} / R_B$

$$I_B = 0, V_{BE} \neq V_{BB}$$

$$\text{Slope} = -1/R_B$$

o/p operating pt :-

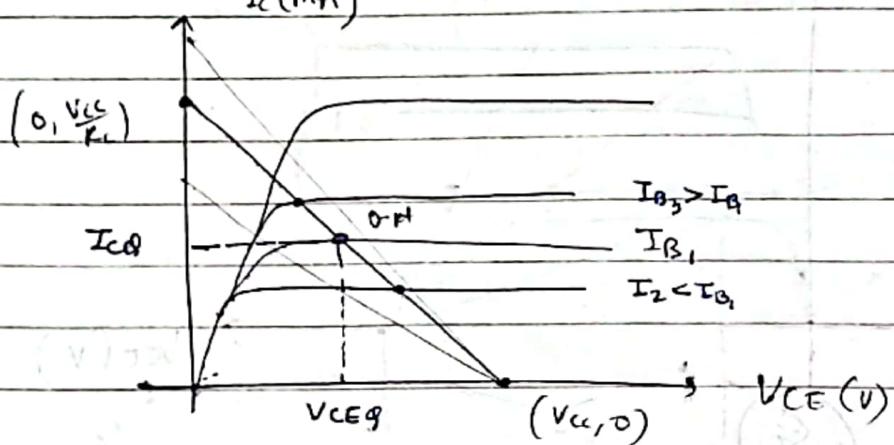

KVL :


$$V_{CC} - I_c R_C - V_{CE} = 0$$

$$\text{when } V_{CE} = 0 \quad I_c = V_{CC}/R_C$$

$$I_c = 0 \quad V_{CE} = V_{CC}$$

$$\text{slope} = -1/R_C$$

- ⇒ Setting of operating point is basic thing for amplification of weak signal because
- ⇒ Operating pt. should be in the middle of load line, if not have distortionless output signal.
- ⇒ When operating point is near the cut-off region the positive part of waveform is clipped.
- ⇒ When operating point is near the saturation region the negative portion of the waveform is clipped. Or swing (strength) is reduced.
- ⇒ This is why operating pt. should be selected in the middle of active region for max. swing & min. distortion otherwise it results in UNFAITHFUL AMPLIFICATION.

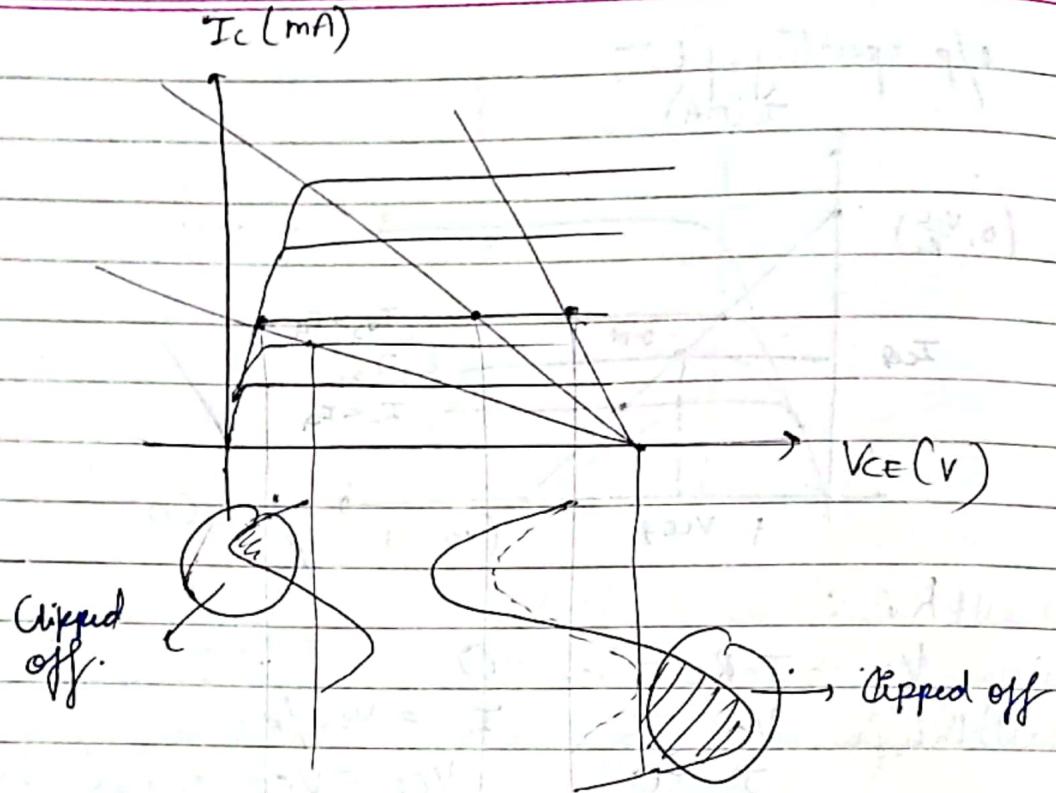

→ Once O-point is fixed, it should not change with Collector current.

I_c may change

→ Change in β

(No two ~~same~~ transistors have same β)

$$I_c = \beta I_B$$


→ Change in T

$$I_c = \beta I_B + (\beta + 1) I_{B0}$$


T changes, sat current changes
due to effect on minority charge carriers

$$T \uparrow \Rightarrow I_{B0} \uparrow \Rightarrow I_c \uparrow$$

FIXED-BIAS CONFIG (Base bias config)

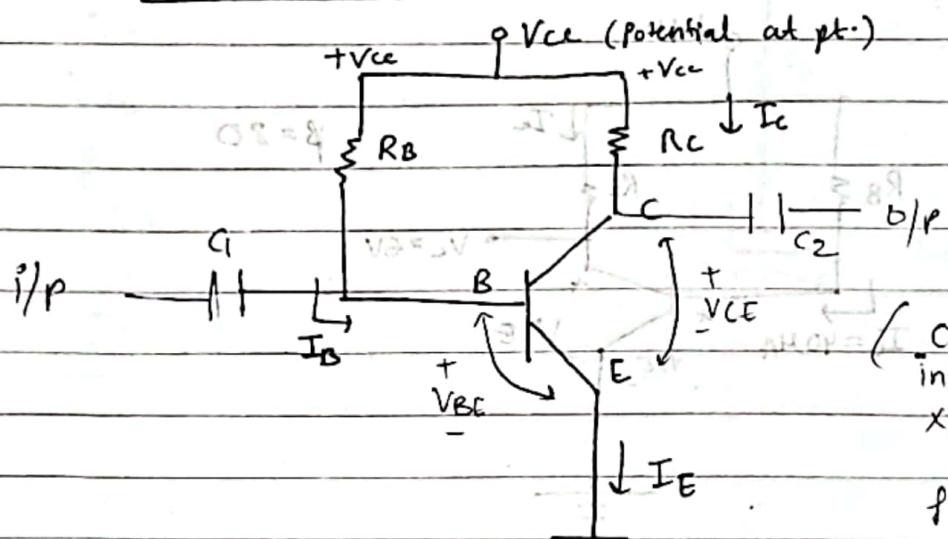

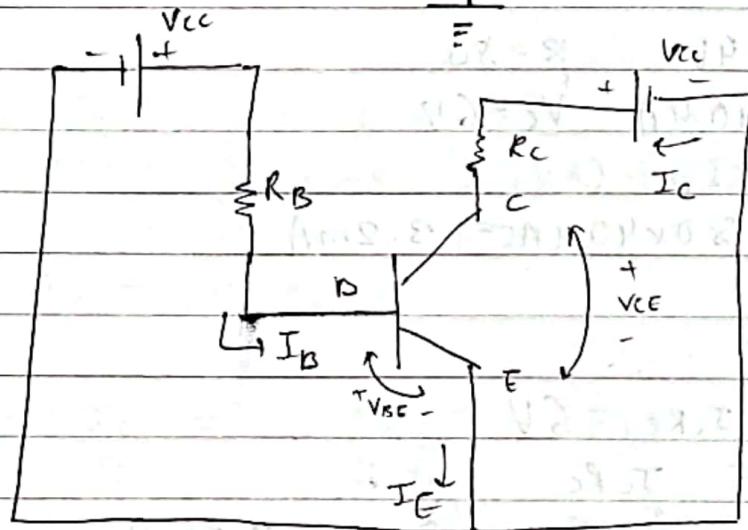C_1 & C_2 are ignored
in DC analysis because
 $X_C = \frac{1}{2\pi f C}$
 $f = 0$ in DC



$X_C = \infty$, so it would
make the capacitor
open circuit

(i/p) KVL:

$$V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$


$$I_C = \beta I_B = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

(o/p) KVL:

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

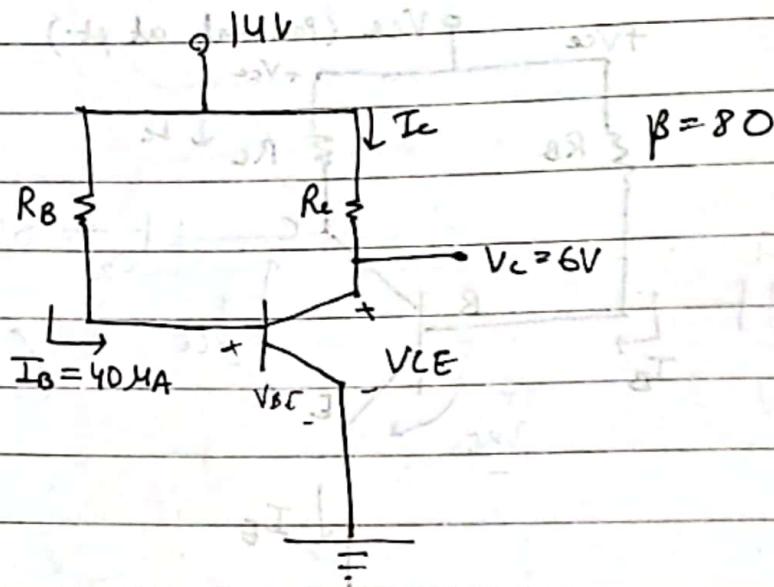Q. Find i) I_c ii) R_c iii) R_B iv) V_{CE}



$$V_{CC} = 14V \quad \beta = 80$$

$$I_B = 40\text{mA} \quad V_C = 6V$$

$$\begin{aligned} \text{i) } I_C &= \beta I_B \\ &= 80 \times 40\text{mA} = 3.2\text{mA} \end{aligned}$$

$$\text{ii) } \cancel{R_C = ?}$$

$$14V - I_C R_C = 6V$$

$$8 = I_C R_C$$

$$R_C = \frac{14V - 6V}{I_C} = \frac{8}{3.2\text{mA}} = 2.5k\Omega$$

$$\text{iii) } 14 - I_B R_B - V_{BE} = 0$$

$$R_B = \frac{14 - V_{BE}}{I_B} = \frac{13.3}{40\text{mA}} = 332.5\Omega$$


$$\text{iv) } V_{CE} = V_C - V_E = 6 - 0 = 6V$$

Q. Determine
 a) I_c

b) V_{CC}

c) β

d) R_B

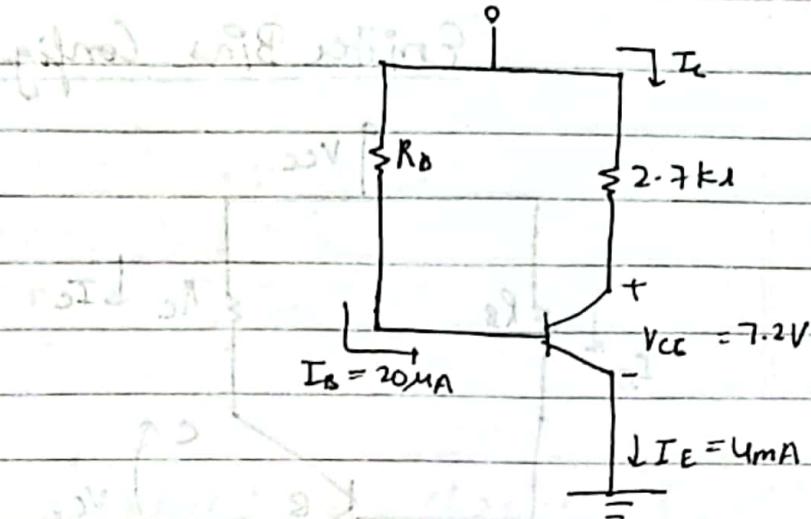

$$I_E = I_C + I_B$$

$$I_C = I_E - I_B \\ = 4\text{mA} - 20\mu\text{A}$$

$$I_C = 3.98\text{mA}$$

$$V_{CC} - I_C(2.7\text{k}\Omega) - 7.2V = 0$$

$$V_{CC} = (3.98\text{mA})(2.7\text{k}\Omega) + 7.2V \\ = 10.746V + 7.2V$$

$$V_{CC} = 17.946V$$


$$\text{iii) } \beta = \frac{I_C}{I_B} = \frac{3.98\text{mA}}{20\mu\text{A}} = 199$$

$$\text{iv) KVL: } V_{CC} - I_B R_B - V_{BE} = 0 \\ 17.946V - 20\text{mA} \times R_B - 0.7V = 0$$

$$R_B = \frac{17.946V - 0.7V}{20\text{mA}}$$

$$R_B = 862.3\text{k}\Omega$$

Emitter Bias Config

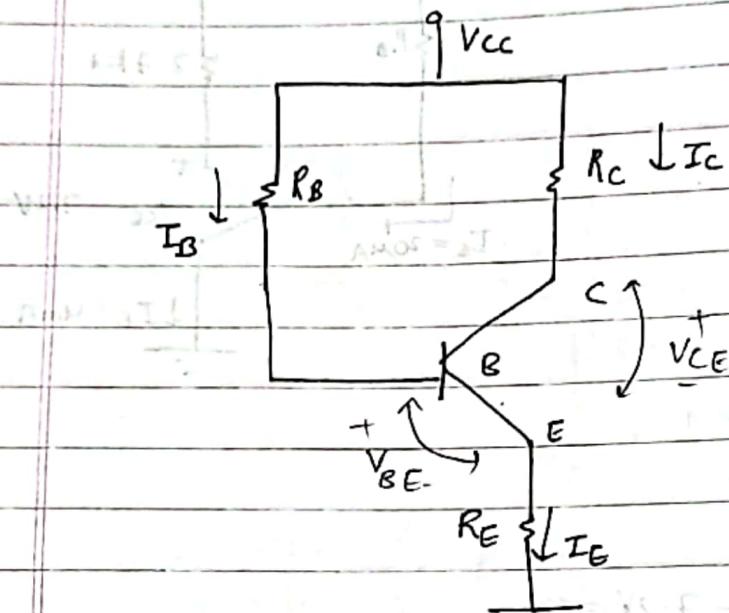

$$V_{CC} - I_B R_B - V_{BE} - I_C R_E = 0 \quad = 9V$$

$$I_E = I_C + I_B$$

$$= \beta I_B + I_B$$

$$I_E = (\beta + 1) I_B$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1) I_B R_E$$

$$V_{CC} - I_B (R_B + [\beta + 1] R_E) - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$R_B + (\beta + 1) R_E$$

$$I_C = \beta I_B$$

$$I_C = \frac{\beta (V_{CC} - V_{BE})}{R_B + (\beta + 1) R_E}$$

6/r loop:

$$V_{CC} - I_C R_C - V_{CE} - J_E R_E = 0$$

$$V_{CC} - I_C (R_C + R_E) - V_{CE} = 0$$


$$\boxed{V_{CE} = V_{CC} - (R_C + R_E) I_C}$$

Why to use R_E :

We do not want operating point change. If we take $I_C \neq 0$ it will change.

Q.

Find: R_C , R_E , R_B , V_{CE} , V_B

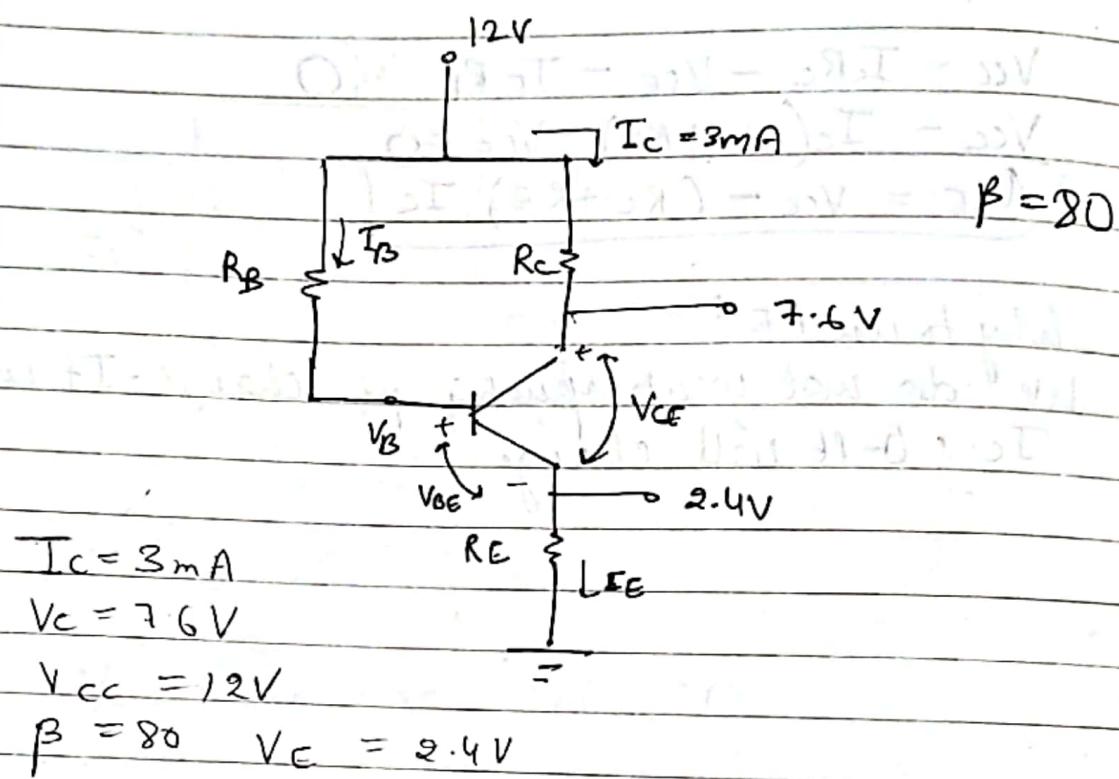

$$\Rightarrow V_{BE} = 0.7 \text{ V (Si)}$$

$$V_B - V_E = 0.7$$

$$V_B = 2.4 + 0.7$$

$$V_B = 3.1 \text{ V}$$

$$\Rightarrow V_{CE} = V_C - V_E$$

$$= 7.6 - 2.4$$

$$V_{CE} = 5.2 \text{ V}$$

$$\Rightarrow 12 - I_B R_B = 3.1$$

$$I_B = I_C / \beta = \frac{3 \text{ mA}}{80} = 37.5 \mu\text{A}$$

$$R_B = \frac{12 - 3.1}{37.5 \times 10^{-6}} = 237.4 \text{ k}\Omega$$

$$\Rightarrow 2.4 - I_E R_E = 0$$

$$I_E \approx I_C$$

$$\frac{2.4V}{3mA} = R_E$$


$$R_E = 0.8k\Omega$$

$$\Rightarrow 12 - I_C R_C = 7.6$$

$$\frac{12 - 7.6}{3mA} = R_C$$

$$R_C = 1.47k\Omega$$

Collector feedback Biasing

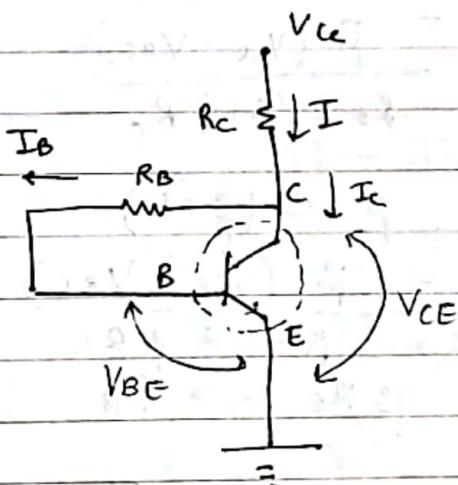

$$I = I_C + I_B$$

$$V_{CC} - (I_C + I_B) R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} - (\beta I_B + I_B) R_C - I_B R_B - V_{BE} = 0$$

$$V_{CC} - [(\beta + 1) R_C + R_B] I_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + R_B}$$

$$I_C = \beta I_B = \frac{\beta (V_{CC} - V_{BE})}{(\beta + 1) R_C + R_B}$$

KVL o/p:

$$V_{CC} - IR_C - V_{CE} = 0$$

~~EB~~

$$V_{CC} - (I_C + I_B)R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - (I_C + I_B)R_C$$

Advantages:-

- It stabilises the Q-point
- 1) Against the variation of Temperature (T)
- 2) Against the variation of biasing voltage V_{CC}
- 3) Against the variation of β

$$\text{as } I_C = \frac{\beta(V_{CC} - V_{BE})}{R_B + (\beta+1)R_C}$$

$$\text{Now } \beta \approx (\beta+1)$$

$$I_C = \frac{\beta(V_{CC} - V_{BE})}{R_B + \beta R_C}$$

$$\text{also } \beta R_C \gg R_B$$

$$I_C = \frac{\beta(V_{CC} - V_{BE})}{\beta R_C}$$

(So it's independent of β)

Disadvantages:


For iii) advantage $\beta R_C \gg R_B$ - Many times

we don't know value of β so, we have

to make $R_C \uparrow$ or $R_B \downarrow$. If $R_C \uparrow$, V_{CC} should be also \uparrow which means cost

increases & precautions also increase. \Rightarrow Also Reverse Bias of Collect - Base junction \downarrow .

Q. Determine the Operating point:

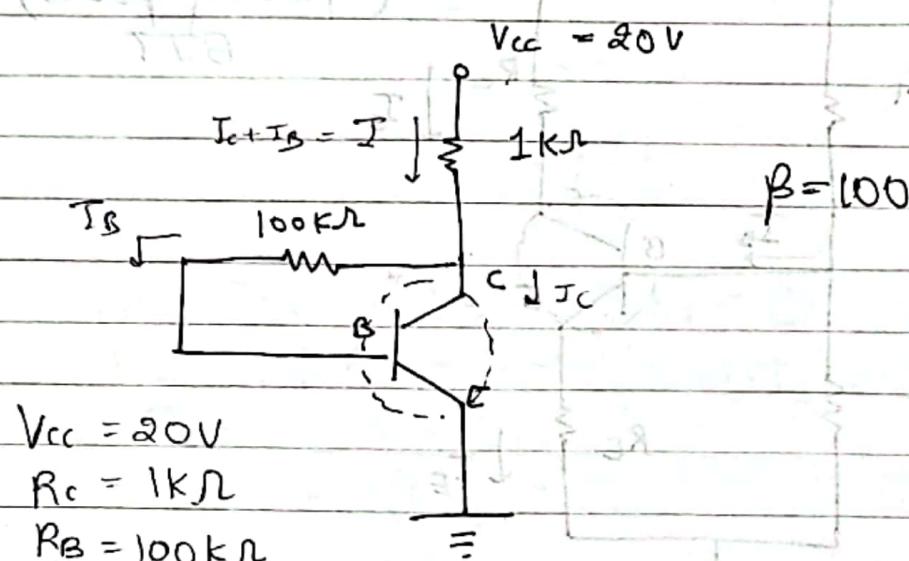

$$Q_{pt} = (I_C, V_{CE})$$

$$V_{CC} - (I_C + I_B)(1k\Omega) - I_B(100k\Omega) = 0.9V = 0$$

$$I_C = \beta I_B$$

$$I_B = \frac{V_{CC} - 0.7}{(\beta + 1)(1k\Omega) + 100k\Omega}$$

$$I_B = \frac{20 - 0.7}{(100)(1k\Omega) + 100k\Omega} = \frac{19.3}{201k\Omega} V$$

$$I_B = 0.096mA$$

$$I_B = 96mA$$


$$I_C = \beta I_B = 9.6mA$$

$$\text{Now, } 20V - (I_C + I_B)(1k\Omega) - V_{CE} = 0$$

$$V_{CE} = 10.364V$$


$$Q_{pt} = (9.6mA, 10.364V)$$

VOLTAGE DIVIDER BIAS

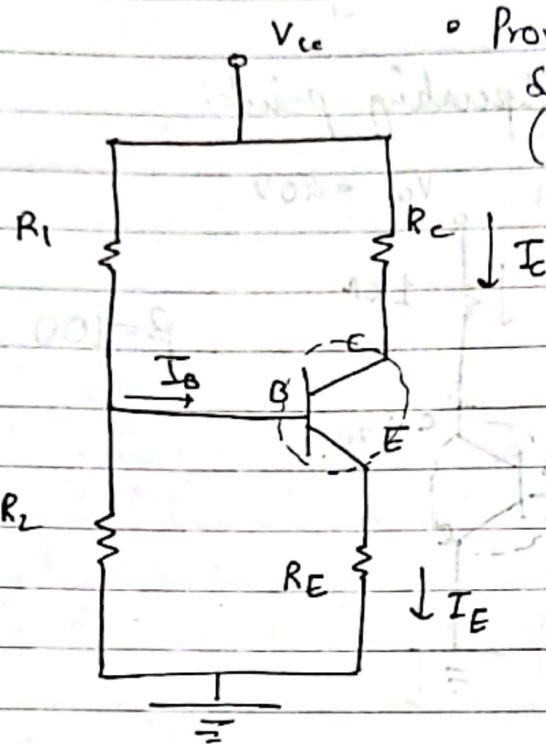

- Provides the best stabilisation of Q-point (Operating point) for BJT


Using Thevenin's theorem:-

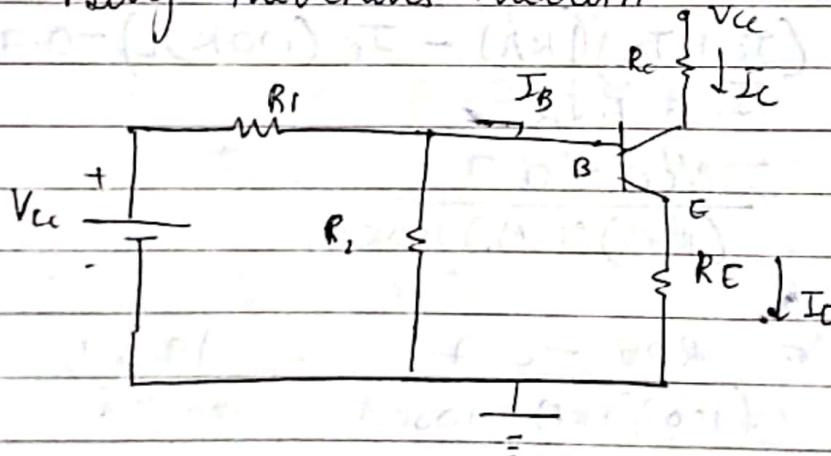


$$R_{Th} = (R_1 || R_2) = \frac{R_1 R_2}{R_1 + R_2}$$

$$I = \frac{V_{cc}}{R_1 + R_2}$$
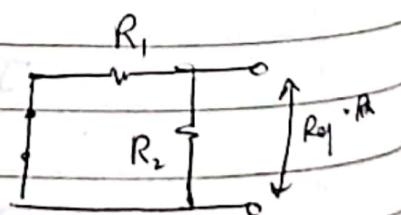
$$V_{Th} = I R_2 = \frac{R_2 V_{cc}}{R_1 + R_2}$$


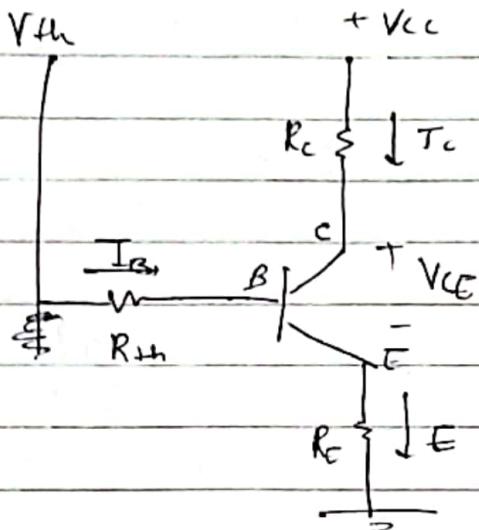
$$V_{Th} = I R_2 = \frac{R_2 V_{cc}}{R_1 + R_2}$$



$$V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$$

$$V_{th} - I_B R_{th} - V_{BE} - (\beta + 1) I_E R_E = 0$$

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} + (\beta + 1) R_E}$$

$$I_C = \beta I_B = \frac{\beta (V_{th} - V_{BE})}{R_{th} + (\beta + 1) R_E}$$

$$R_{th} \ll (\beta + 1) R_E$$

Now,

$$V_{cc} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$I_E \approx I_C$$

$$V_{cc} - I_C (R_C + R_E) - V_{CE}$$

$$\Rightarrow V_{CE} = V_{cc} - I_C (R_C + R_E)$$

ADVANTAGES :

- Mostly Used Bias Config.
 $R_{th} \ll (\beta + 1) R_E$ and since $R_{th} = R_1 || R_2$ it is already small