

## Experiment No.: 7

### Applications of OP-AMP

ADITYA RAJ  
U20CS100

**Aim:** To study various applications of operational amplifiers.


#### SOFTWARE TOOLS / OTHER REQUIREMENTS:

Multisim Simulator/Circuit Simulator


#### Theory:
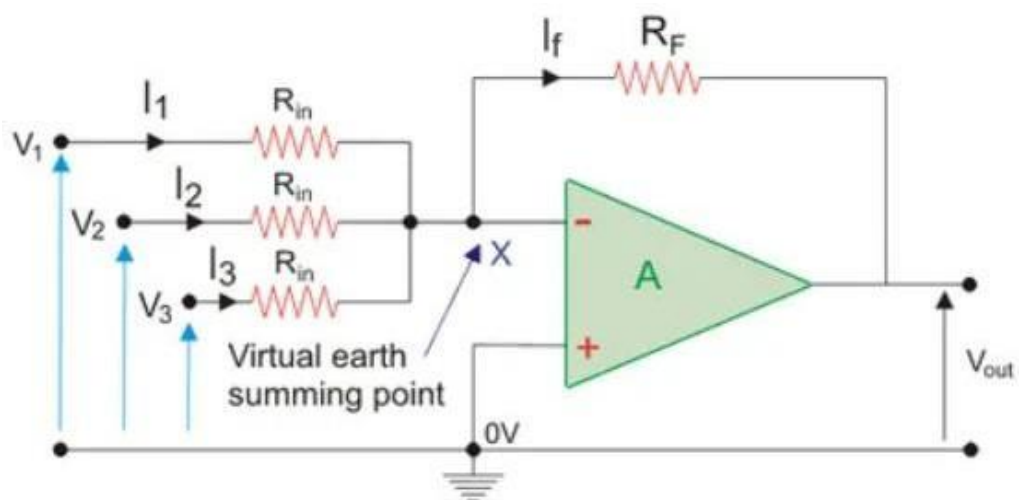
##### OP-AMP Applications as Adder or Summing Amplifier:

Op-amp can be used to sum the input voltage of two or more sources into a single output voltage. Below is a circuit diagram depicting the application of an op-amp as an adder or summing amplifier. The input voltages are applied to the inverting terminal of the op-amp. The inverting terminal is grounded. The output voltage is proportional to the sum of the input voltages.


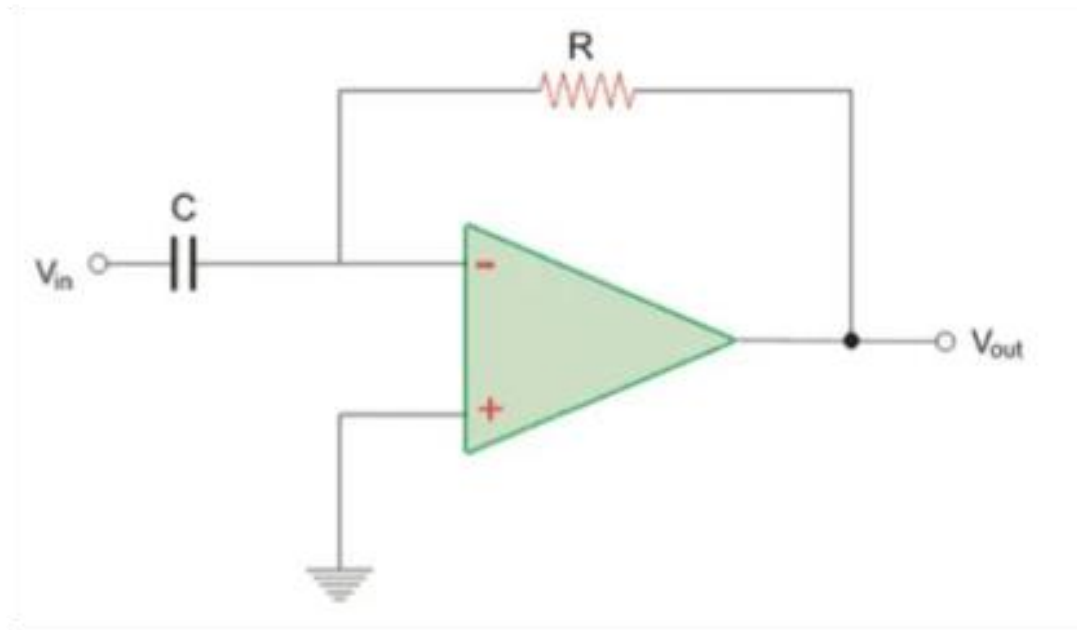
##### OP-AMP Application as a Differentiator:




Op-amp can be used as a differentiator where the output is the first derivative of the input signal. The following equation gives the relation between the input signal and the output signal.

$$V_{OUT} = -R_F C \frac{dV_{IN}}{dt}$$
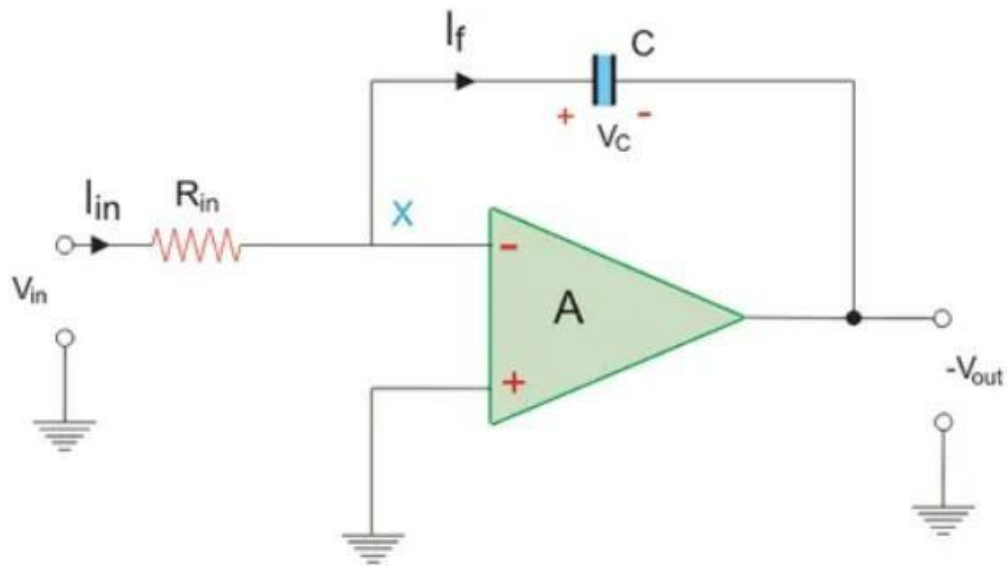
### OP-AMP Application as an Integrator:

Op-amp is used as an integrator also. The integrator op-amp produces an output that is proportional to the amplitude of the input signal as well as the duration of the input signal. Instead of a resistor in the feedback loop, we have a capacitor. It is able to perform the mathematical operation of integration as the output varies with the input and duration of the signal.




### OP-AMP Application as a Comparator:

Operational amplifier compares the voltage applied at one input to the voltage applied at the other input. Any difference between the voltages even if it is small drives the op-amp into saturation. When the voltages supplied to both the inputs are of the same magnitude and the same polarity, then the op-amp output is 0Volts.

A comparator produces limited output voltages which can easily interface with digital logic, even though compatibility needs to be verified.

### **CIRCUIT DIAGRAM (FROM MULTISIM)**

### **ADDER**

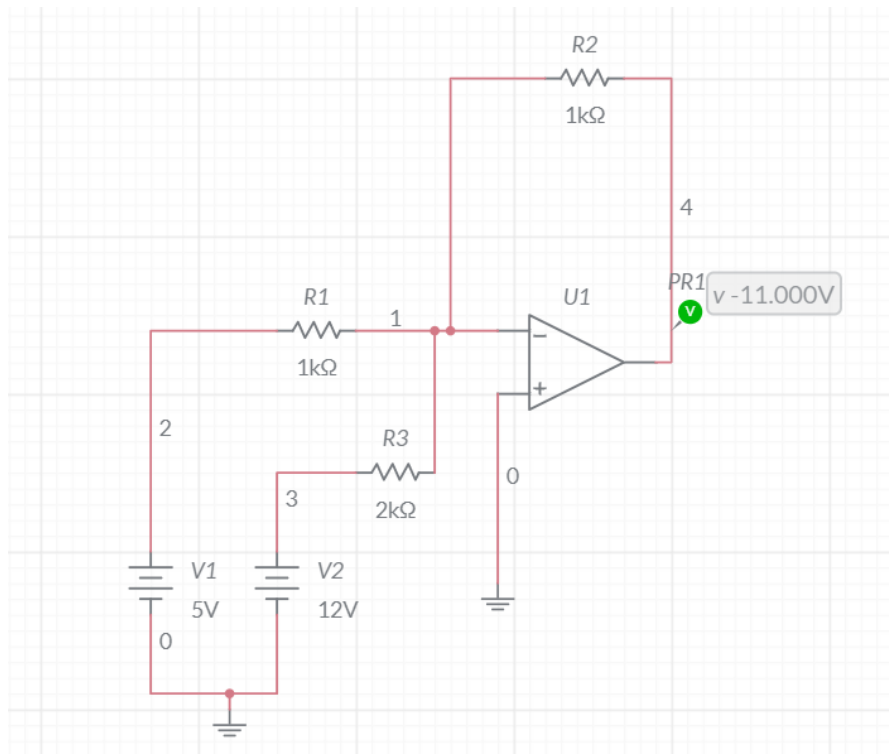

1) Adder


$$\rightarrow I = \frac{5}{1} + \frac{12}{2}$$

$$= 11 \text{ mA}$$

$$V_{out} = 11 \times 10^{-3} \times 1 \times 10^3$$

$$= -11 \text{ V}$$

## SUBTRACTOR

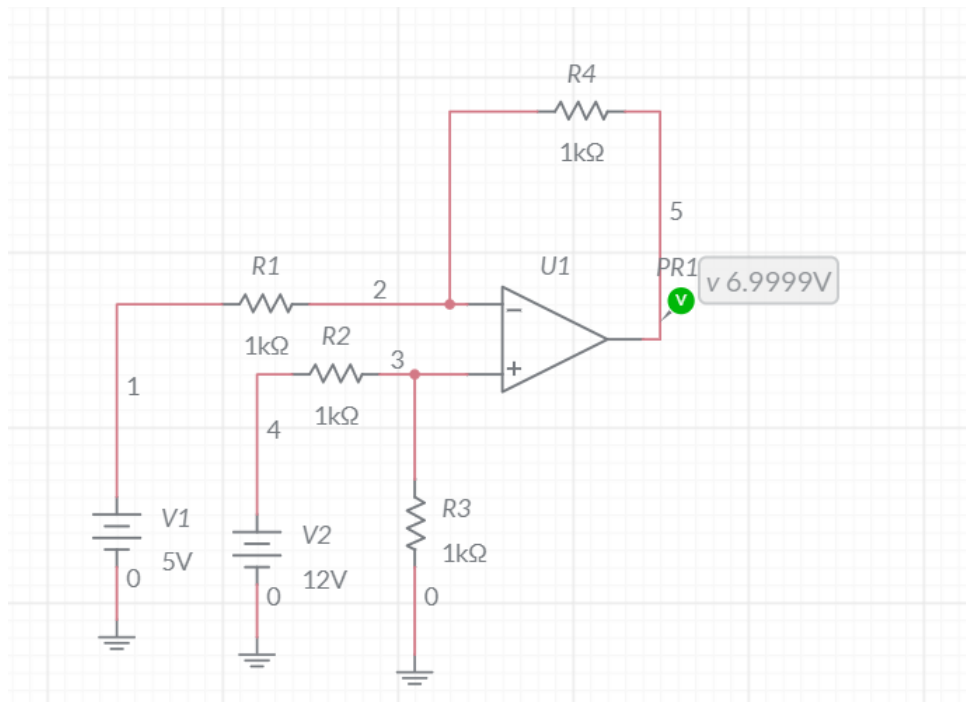


a) Subtractor

$$\frac{5 - 6}{1k\Omega} = \frac{6 - V_{out}}{1k\Omega}$$

$$V_{out} = 7V$$

## SUMMING AMPLIFIER

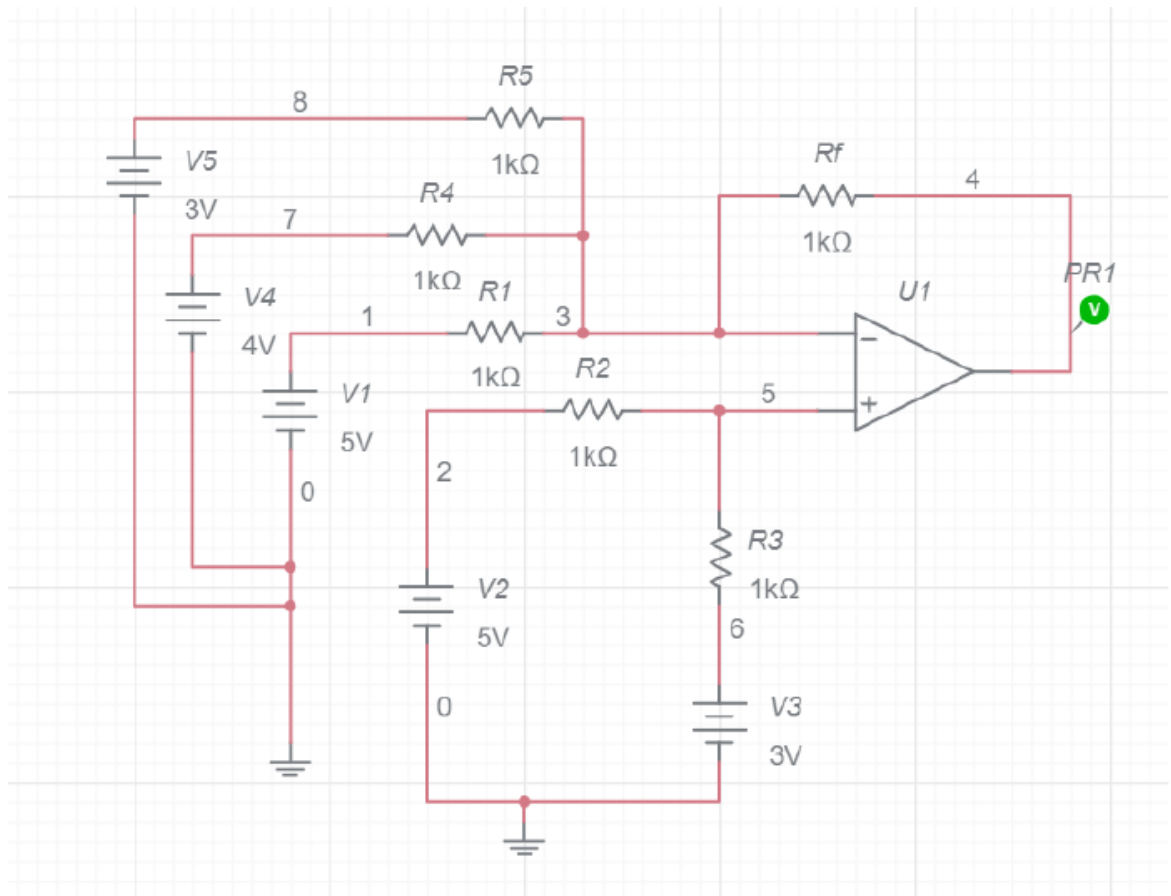

### 3) Summing Amplifier.

→ Take inverting terminal & non inverting ground.

$$V_{out 1} = -K \left( \frac{V_1}{R_3} + \frac{V_2}{R_4} + \frac{V_3}{R_5} \right)$$

$$= -1 \left( \frac{5}{1} + \frac{4}{1} + \frac{3}{1} \right)$$

$$= -12V$$

Take non-inverting terminal & inverting ground

$$V_{out 2} = -12 + 4$$

$$= -16V$$

Current through  $R_3$ ,  $R_4$  &  $R_5 = 4mA$ .

$$I_{total} = 3 \times 4 = 12mA$$

$$12 = \frac{V_{out 2} - 4}{1}$$


$$V_{out 2} = 16V$$

$$V = V_{out 1} + V_{out 2}$$

$$= (-12) + 16$$

$$= 4V$$

## COMPARATOR

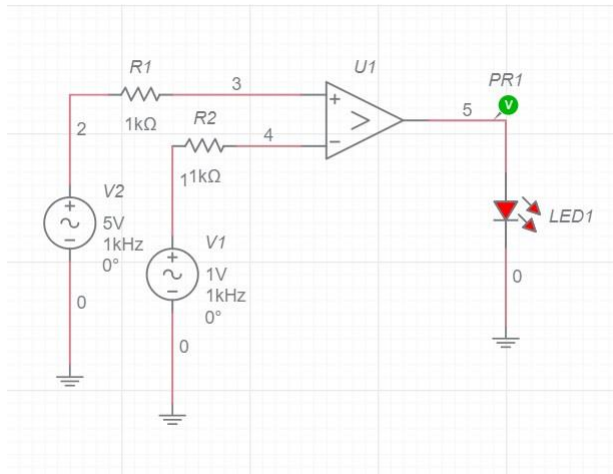



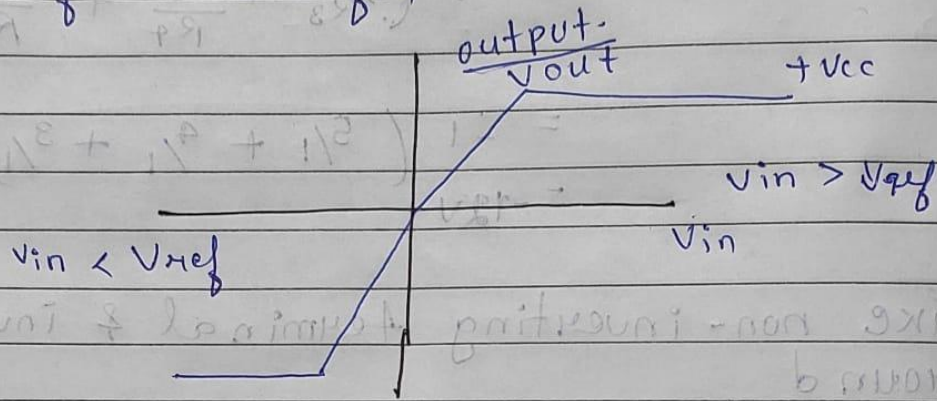
#### 4) Comparator


if  $V_{in} > V_{ref}$ , then  $V_{out} = +V_{cc}$

if  $V_{in} < V_{ref}$ , then  $V_{out} = -V_{cc}$




Sudden change from  $-V_{cc}$  to  $+V_{cc}$  is not allowed, that's why, we get linear region.

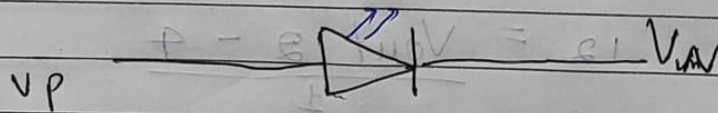LED will glow only when it goes into forward biased region.




$V_P > V_N \rightarrow$  LED glows.  
(forward bias)

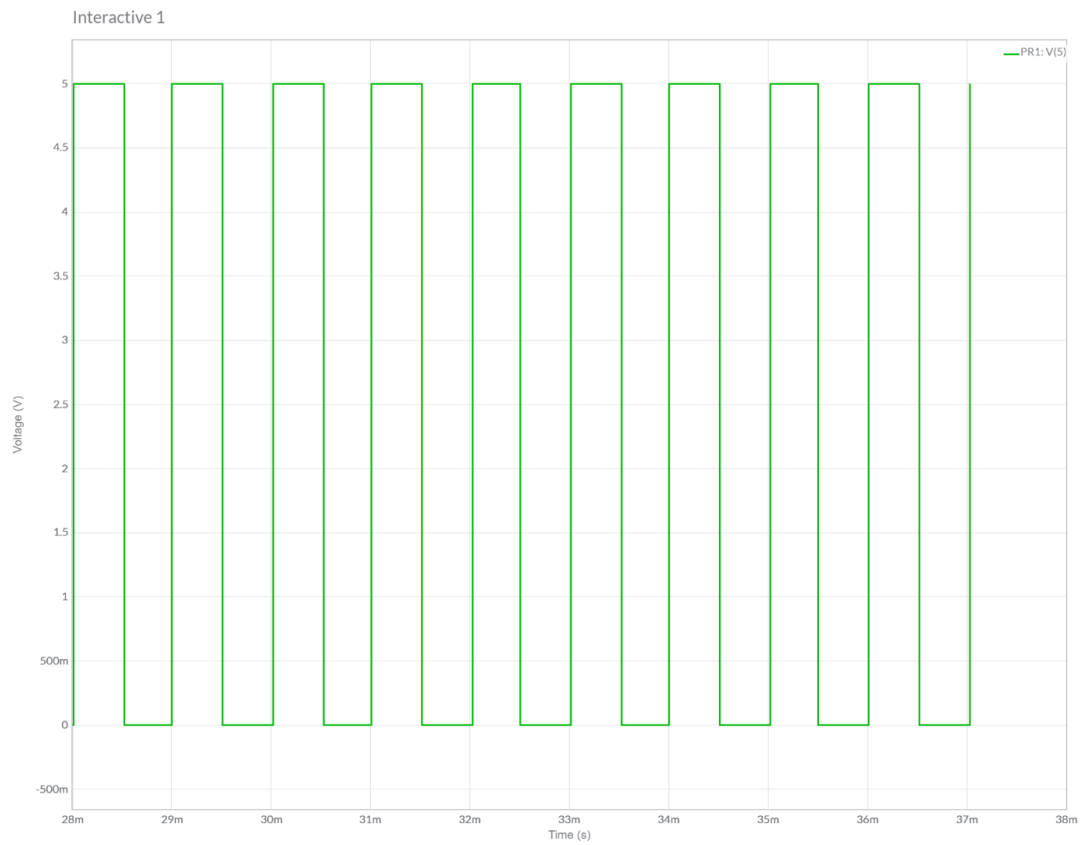$V_P < V_N \rightarrow$  LED does not glow  
(reverse bias)



## OP-AMP INTEGRATOR

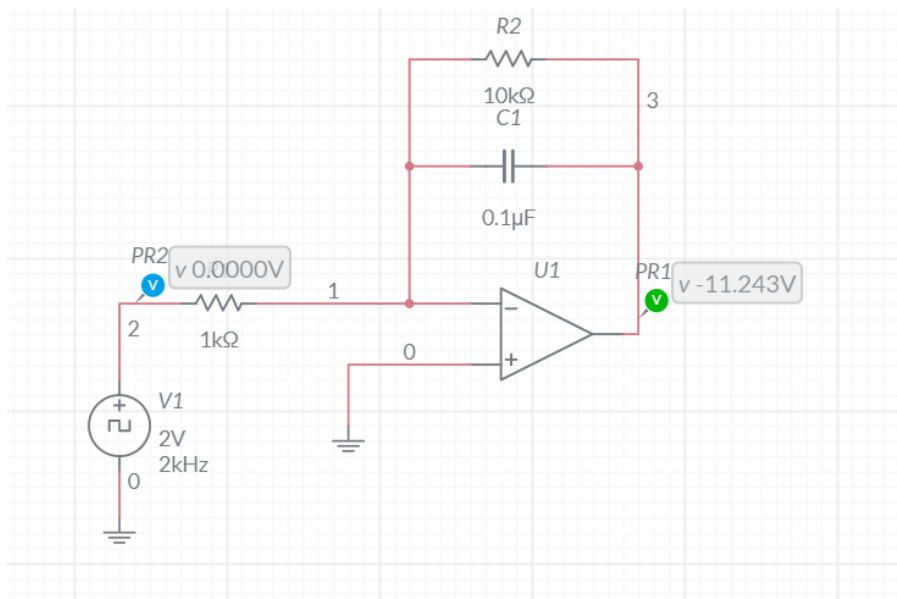

5) Integrator.


$$\begin{aligned} \text{For } V_{out} &= -\frac{1}{RC} \int V_{in} dt \\ &= \frac{1}{RC} \left[ \frac{T}{2} \int_0^{T/2} 1 dt + \int_{T/2}^T 0 dt \right] \\ &= -\frac{T}{RC} \times \frac{T}{2} \end{aligned}$$

$$\text{at } T = RC$$


$$V_{out} = -2V$$

for (+ve) half cycle, slope is (-ve) & vice-versa.

## GRAPH

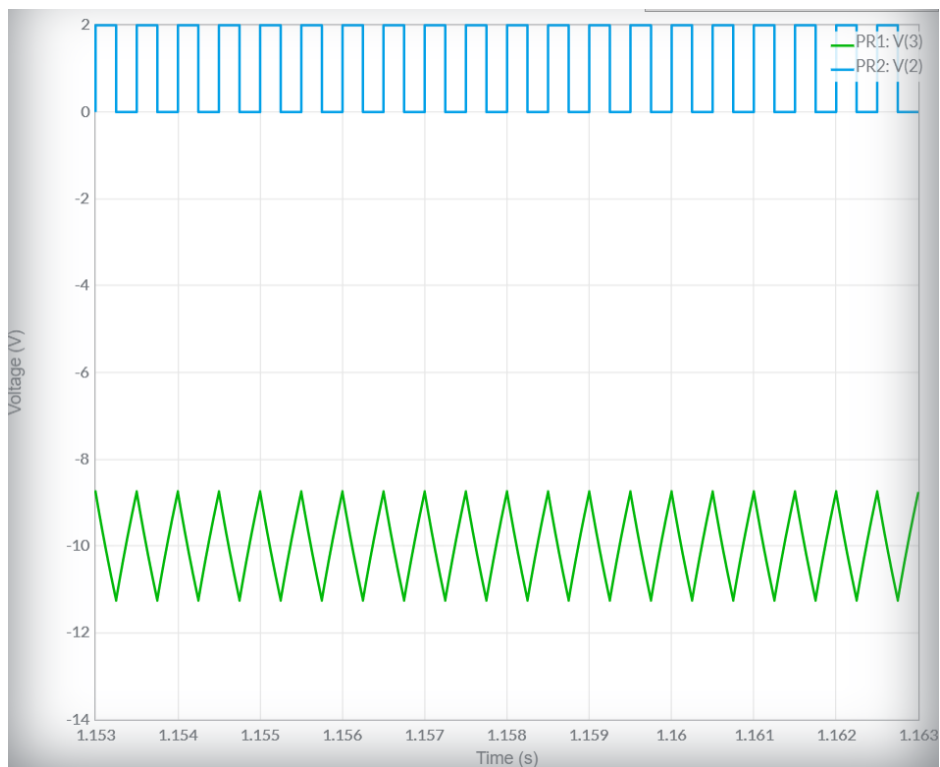

## OP-AMP DIFFERENTIATOR

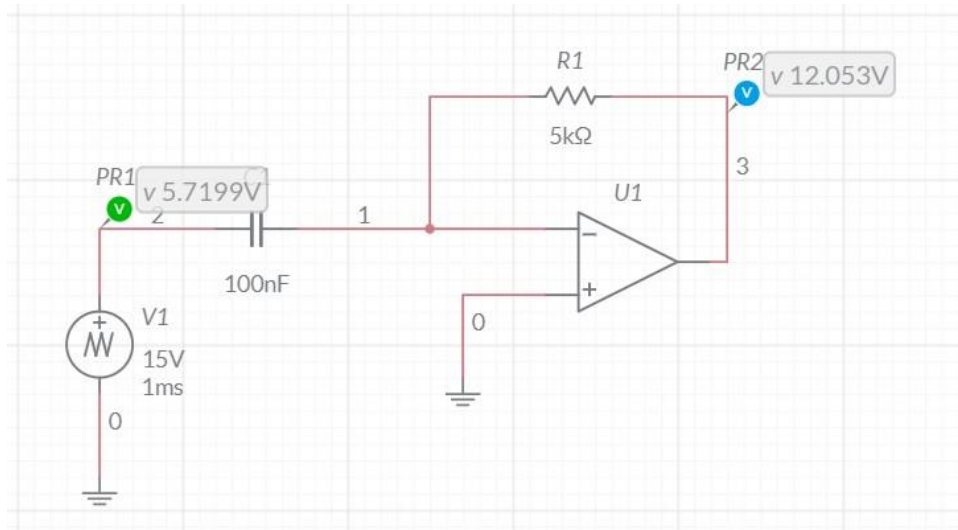

6) Differentiator.

$$I = C \cdot \frac{d}{dt} (V_{in})$$


$$I = \frac{0 - V_{out}}{R_f}$$

$$\frac{-V_{out}}{R_f} = \frac{C \frac{d(V_{in})}{dt}}{dt}$$


$$V_o = -R_f \left( C \cdot \frac{d(V_{in})}{dt} \right)$$


diff of input voltage

**GRAPH**

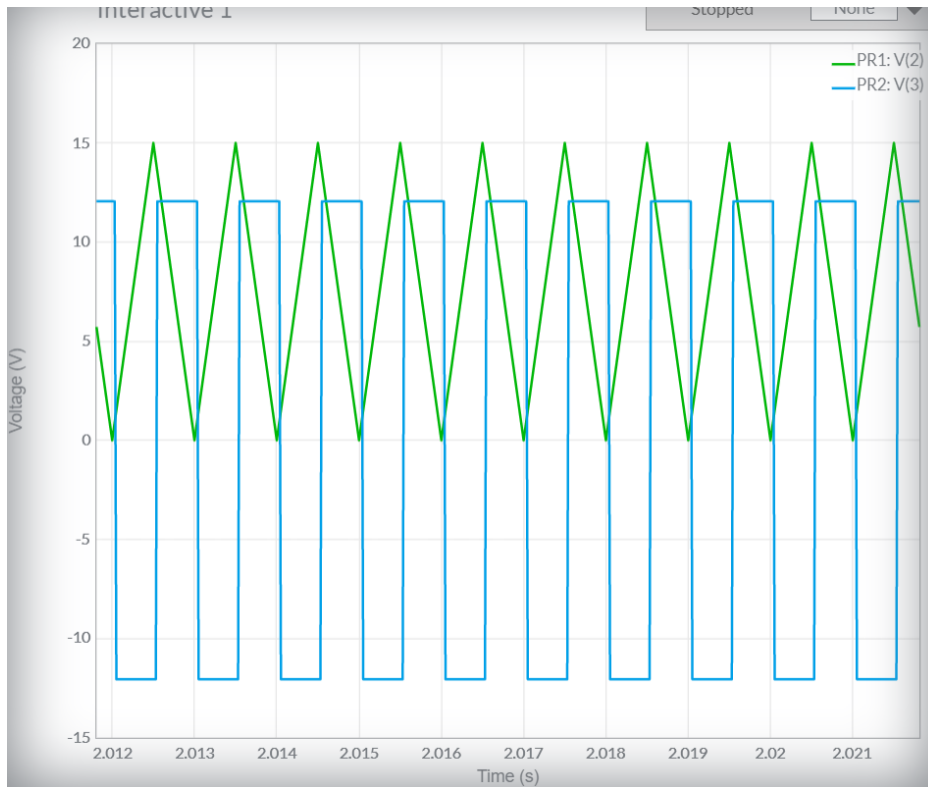


## **FREQUENCY RESPONSE OF INTEGRATOR**

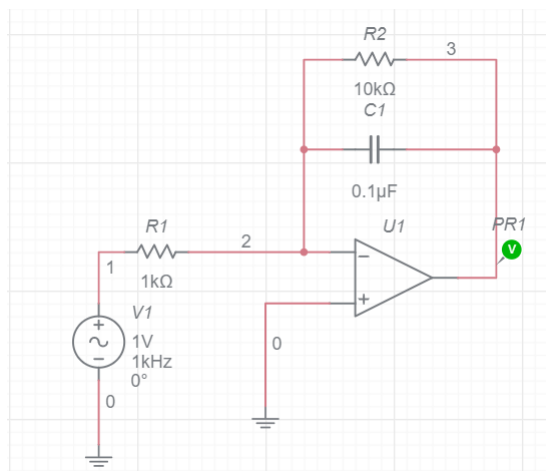


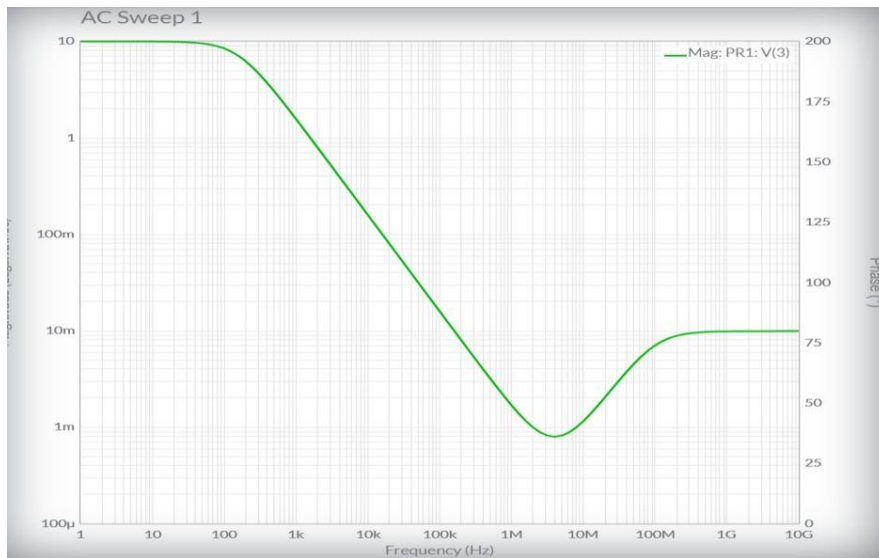
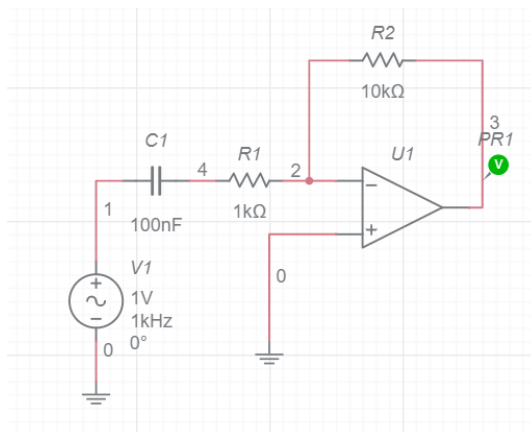
## **FREQUENCY RESPONSE OF DIFFERENTIATOR**





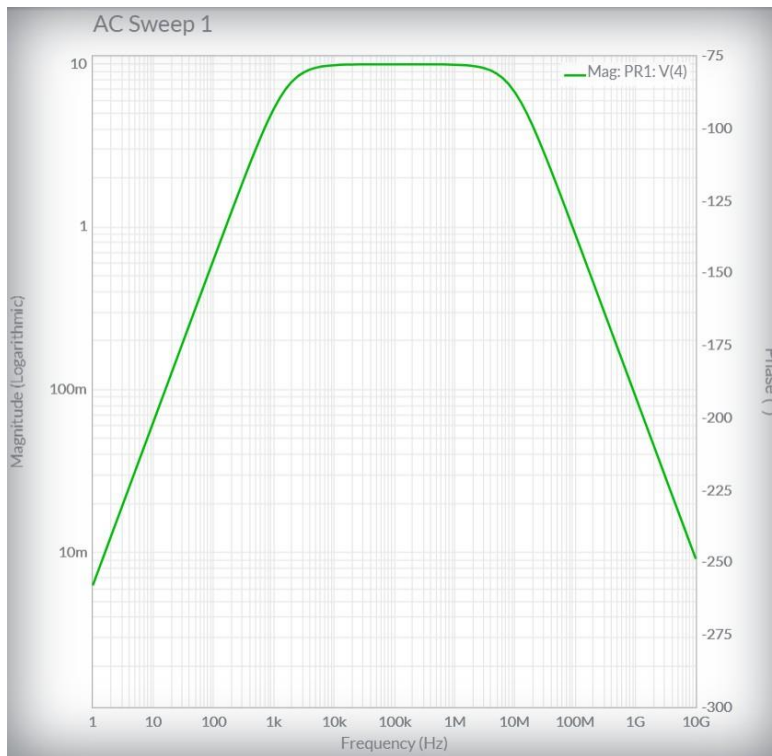

## Conclusion

**THROUGH THIS EXPERIMENT, WE OBSERVED AND VERIFIED VARIOUS APPLICATIONS OF OPERATIONAL AMPLIFIERS.**

**IT CAN BE USED AS ADDER, SUBTRACTOR, SUMMING AMPLIFIER, COMPARATOR, INTEGRATOR, DIFFERENTIATOR AND MANY MORE APPLICATIONS.**