

Name – Aditya Raj
Admission no. – U20CS100

Expt. No:	1	Diode Clipper Circuits
Date:	16/8/2021	

AIM: To implement various Diode clipper circuits and verify its performance using Multi - Sim simulator

SOFTWARE TOOLS / OTHER REQUIREMENTS:

1. Multisim Simulator/Circuit Simulator
-

THEORY:


We know that when a diode is forward biased it allows current to pass through itself clamping the voltage across it to 0.7 volts (Practical Silicon Diode). While, when it is reverse biased, no current flows through it and the voltage across its terminals is unaffected, and this is the basic operation of the diode clipping circuit.

Clippers are networks that employ diodes to "clip" away a portion of an input signal without distorting the remaining part of the applied waveform.

There are two general categories of clippers: **Series** and **Parallel**. The series configuration is defined as the one where the diode is in series with the load, whereas the parallel variety has the diode in a branch parallel to the load.

SERIES CONFIGURATIONS

NEGATIVE CLIPPER :

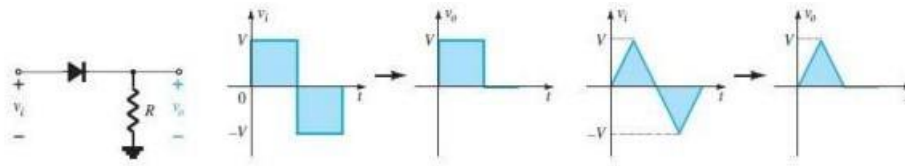


As shown above, when the positive half cycle appears, the diode being forward biased, acts as short circuit and allows the input voltage to appear across the load resistor. During the negative half cycle, the diode is reverse biased, acts as open circuit and hence we see that there is no connection between the output and input node, thereby the output voltage level remains at zero. Since the negative cycle of the input is getting clipped-off, the configuration in the above circuit is known as negative clipper.

Like-wise when the polarity of the diode is reversed, we can clipper-off the positive half of the input cycle. In this case, during the positive half cycle, the diode remains reverse biased thereby disconnecting the output node from input node and the output voltage level remains at zero. But when the negative half cycle appears, the diode gets forward biased and allows the entire input to appear across the output load resistance.

SHUNT CONFIGURATIONS

SHUNT POSITIVE CLIPPER

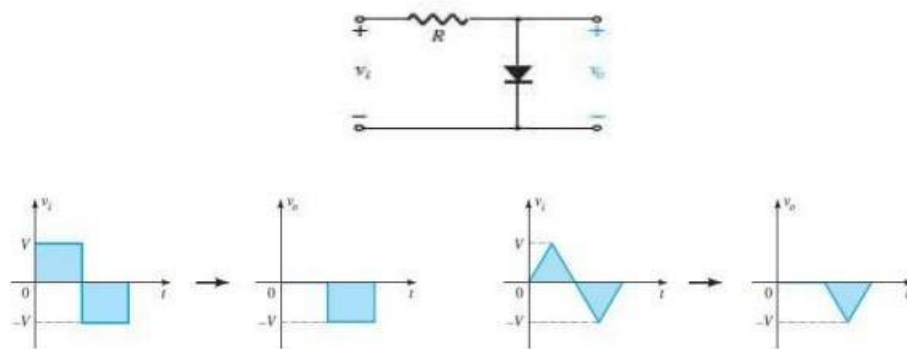


As shown above, when the positive half cycle appears, the diode being forward biased, acts as short circuit and thus the output voltage remains at zero level. During the negative half

cycle, the diode is reverse biased, acts as open circuit and hence we see that the output node comes into direct contact with the input node, thereby the output follows the input. Since the positive cycle of the input is getting clipped-off, the configuration in the above circuit is known as shunt positive clipper.


Likewise if the polarity of the diode is reversed; we can clip-off the negative half of the input cycle. In this case, during the positive half cycle, the diode remains reverse biased thereby connecting the output node with input node and the output voltage follows the input. But when the negative half cycle appears, the diode gets forward biased creating a short across the output nodes resulting into a zero voltage at the output. The level will be 0.7 if a silicon diode is considered instead of an non-ideal diode.

FEW SHUNT DIODE CLIPPER CONFIGURATIONS

POSITIVE

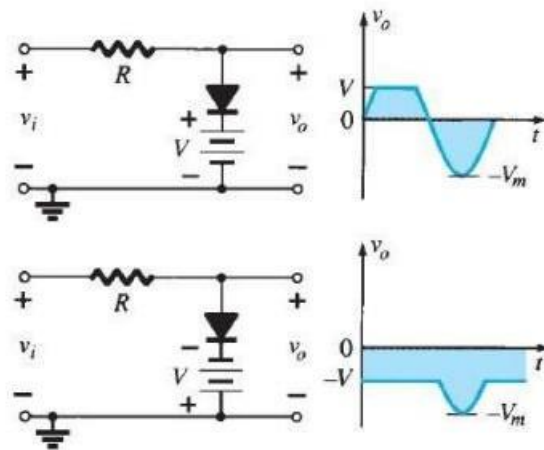


NEGATIVE

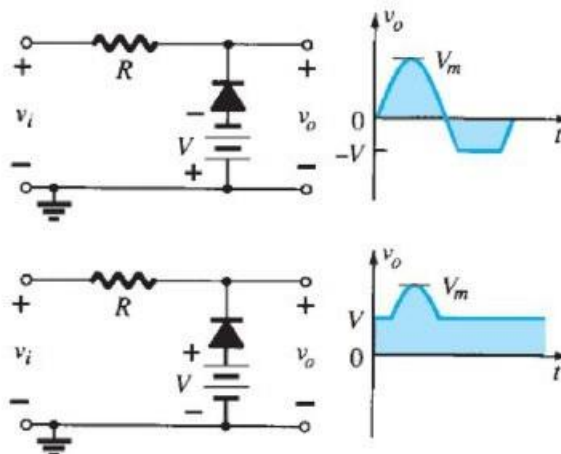


TWO LEVEL CLIPPERS

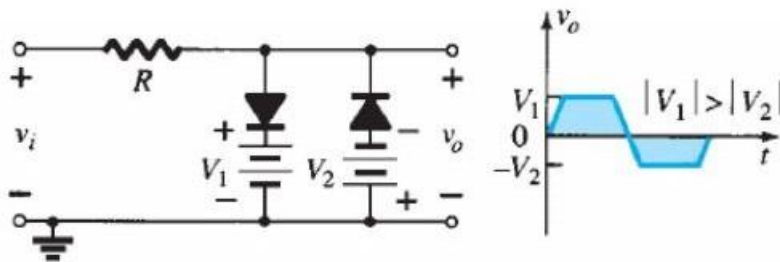These circuits employ clipping in both the directions (Positive as well as Negative Half Cycles) as shown in figure below:




FEW SERIES DIODE CLIPPER CONFIGURATIONS




POSITIVE :

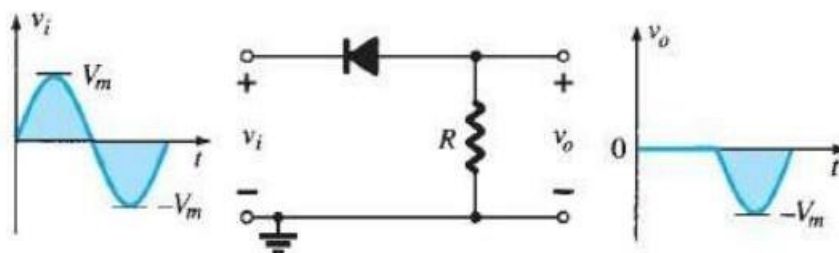

Biased Series Clippers (Ideal Diodes)

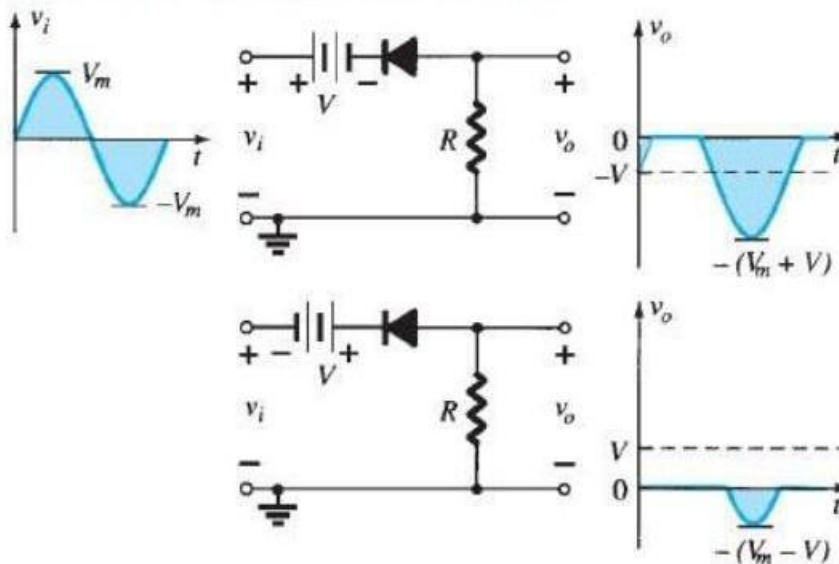


NEGATIVE :

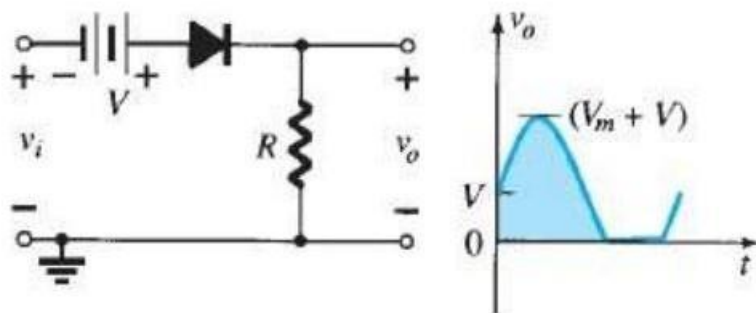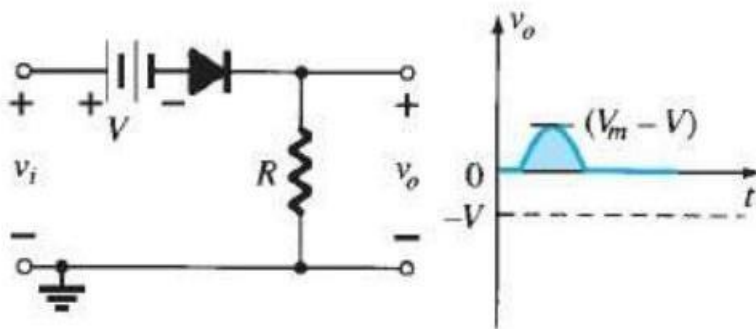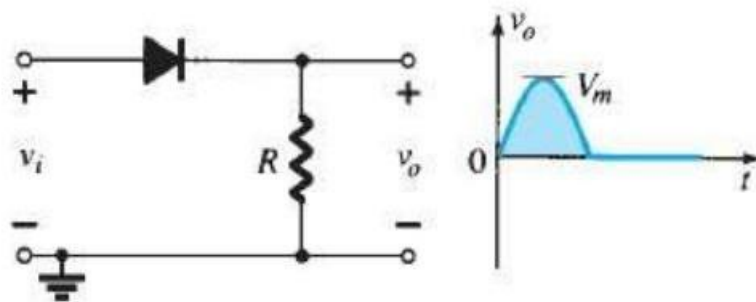


CIRCUIT/CONNECTION AND WAVEFORMS DIAGRAMS (FROM MULTISIM):


SIMPLE SERIES CLIPPERS (IDEAL DIODES):

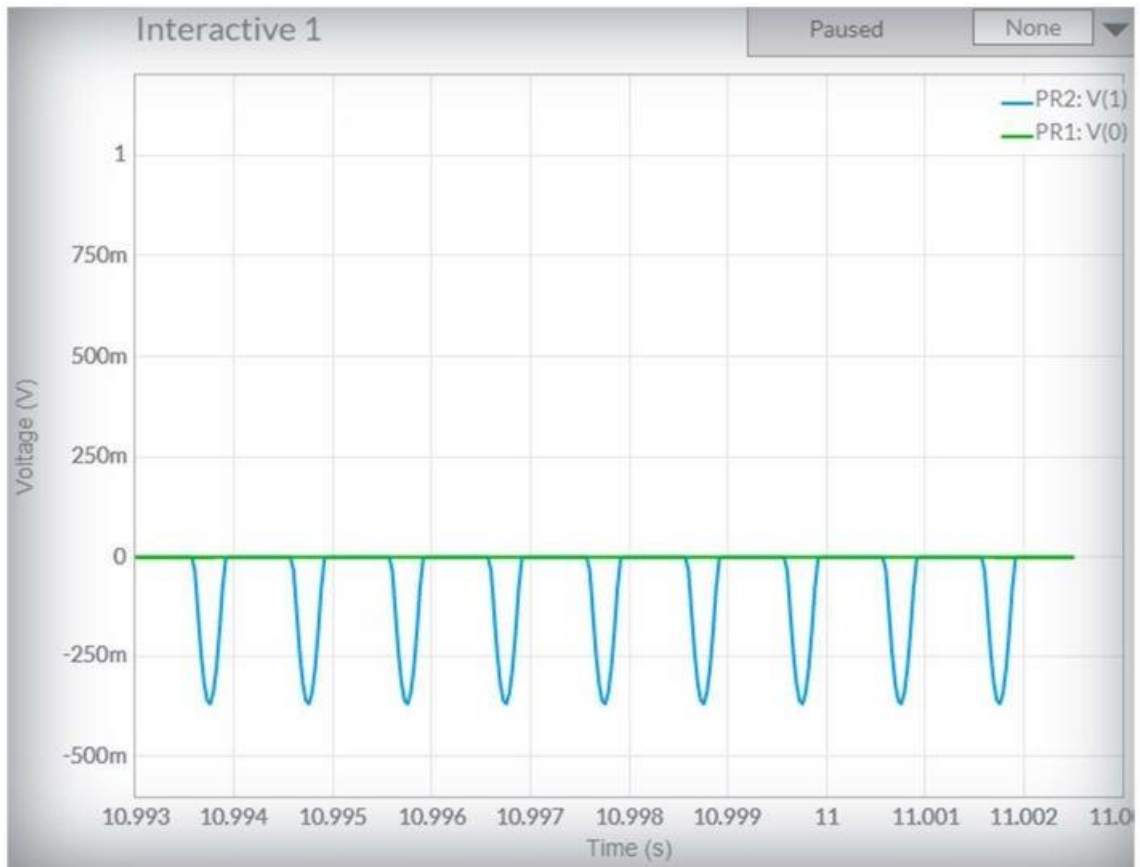



NEGATIVE:



POSITIVE:

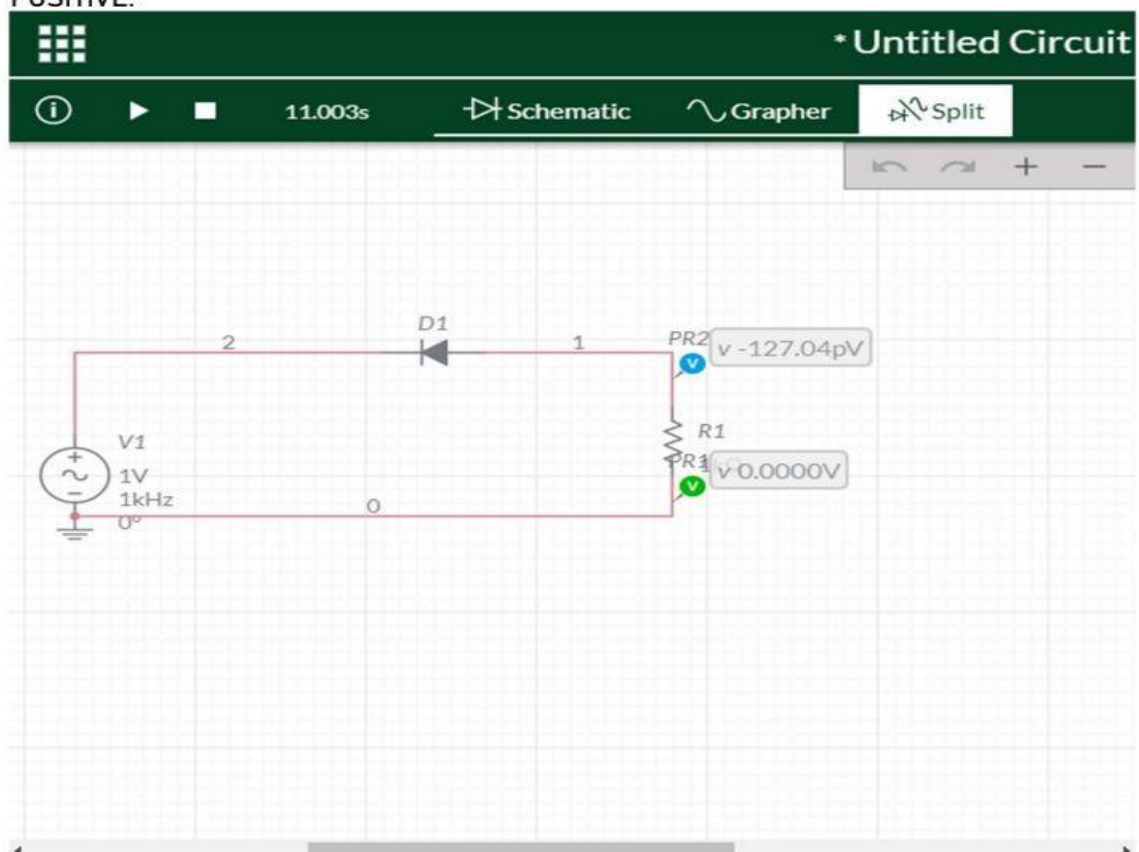

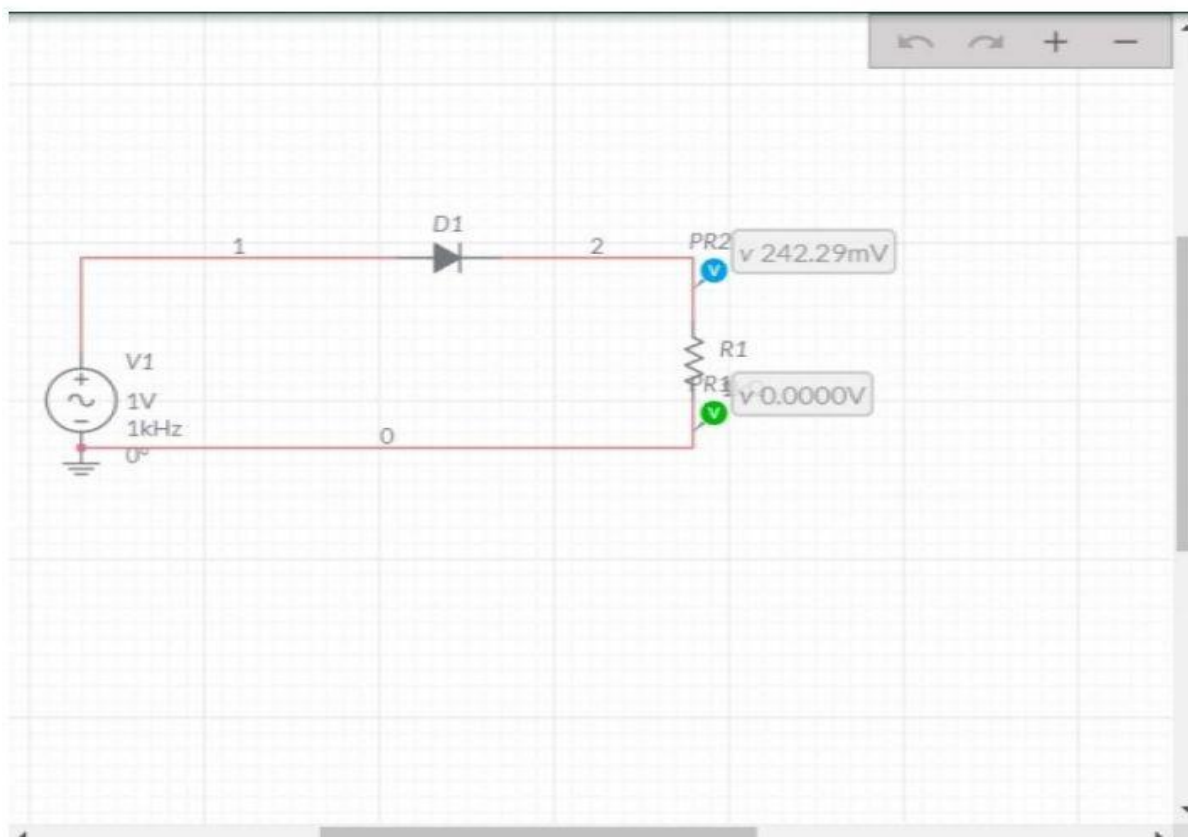


BIASED SERIES CLIPPERS (IDEAL DIODES):

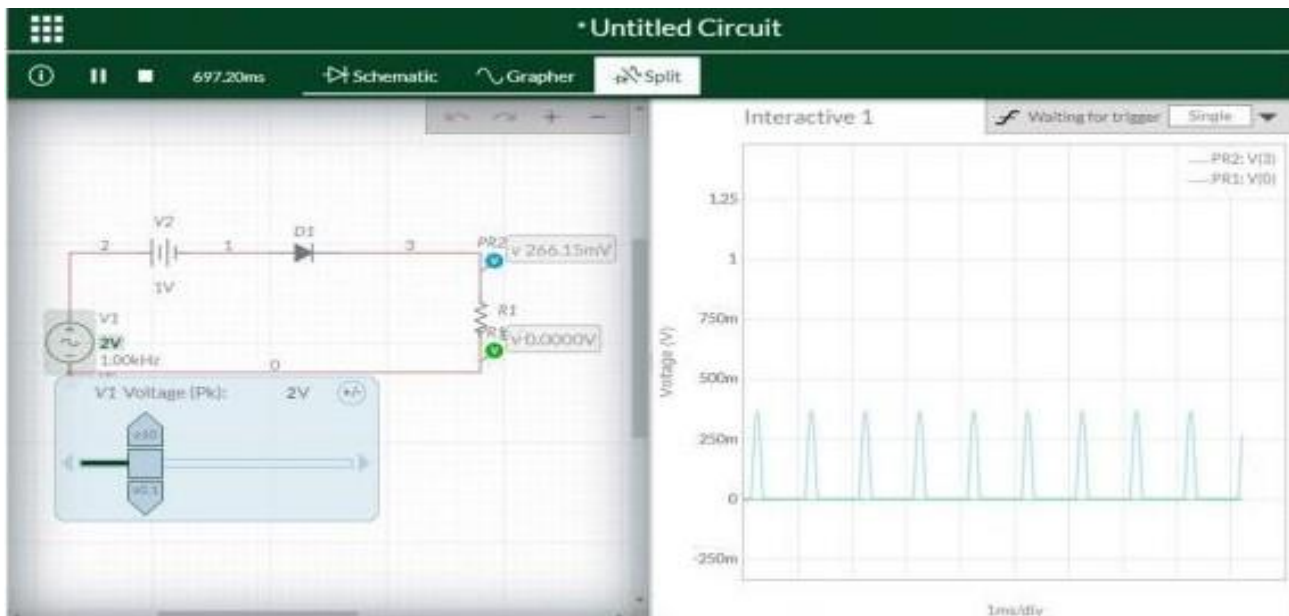
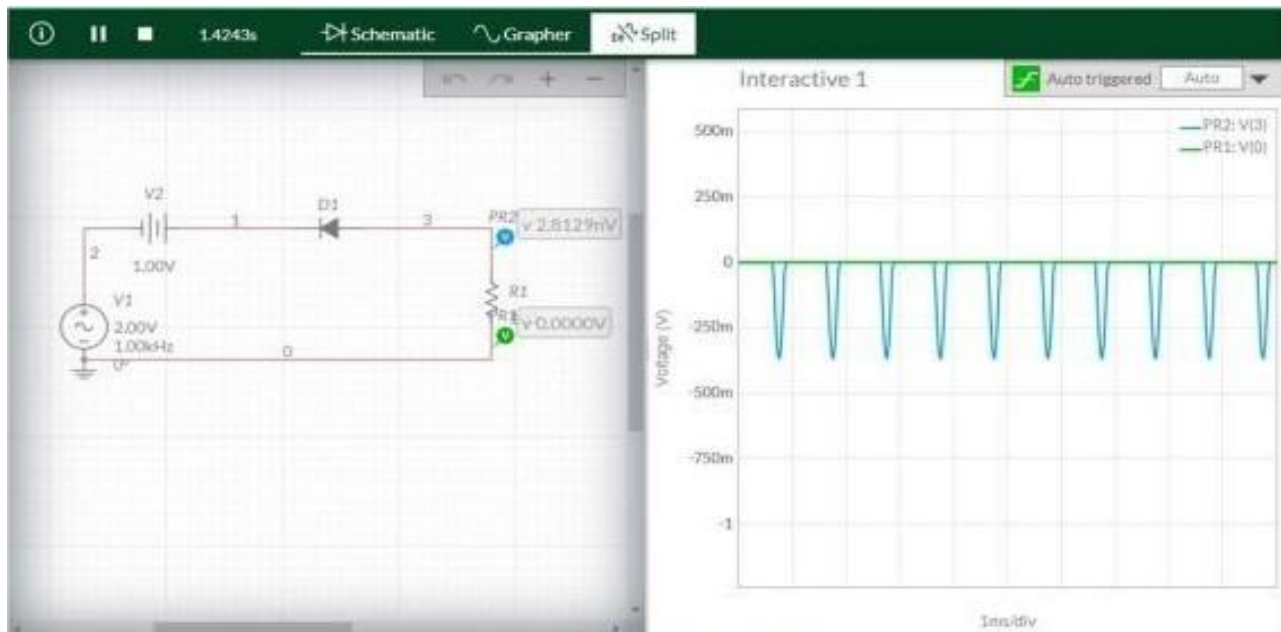


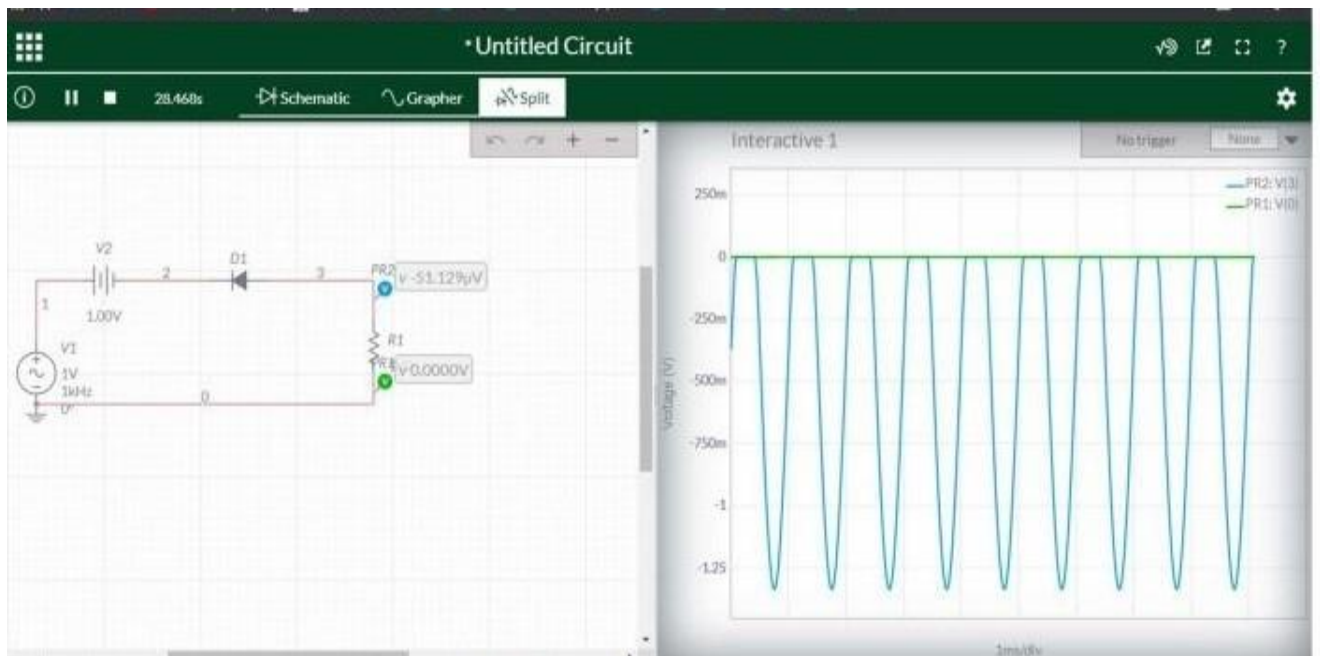
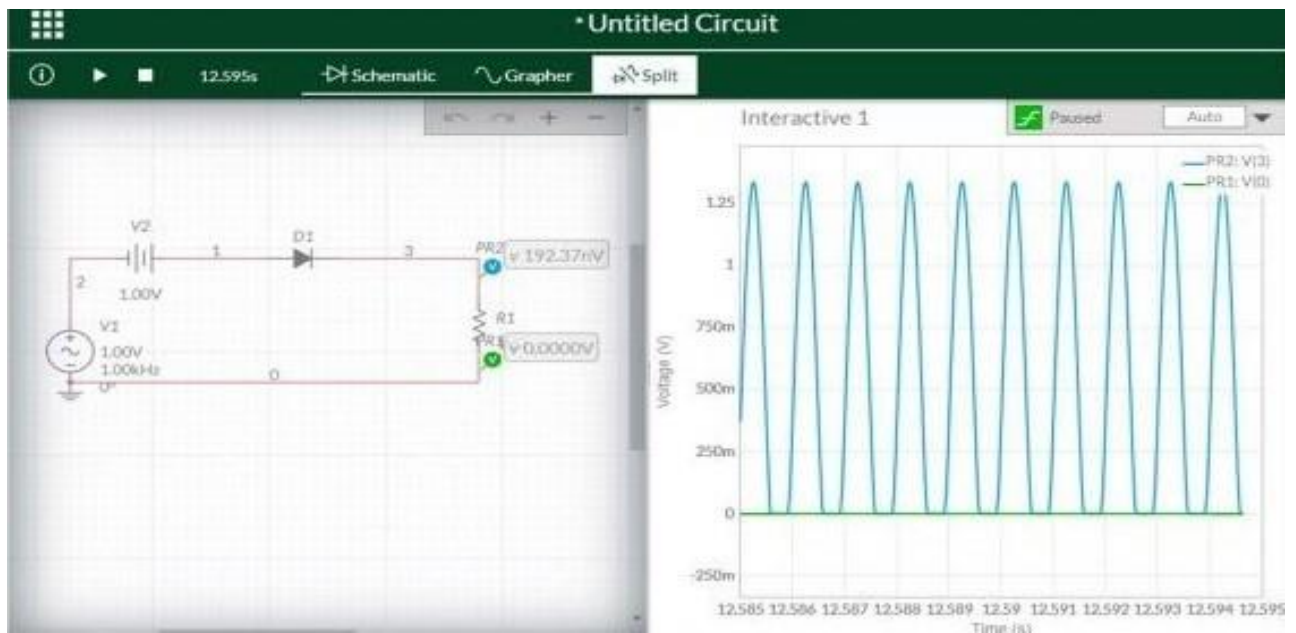



SIMPLE PARALLEL CLIPPERS (IDEAL DIODE)

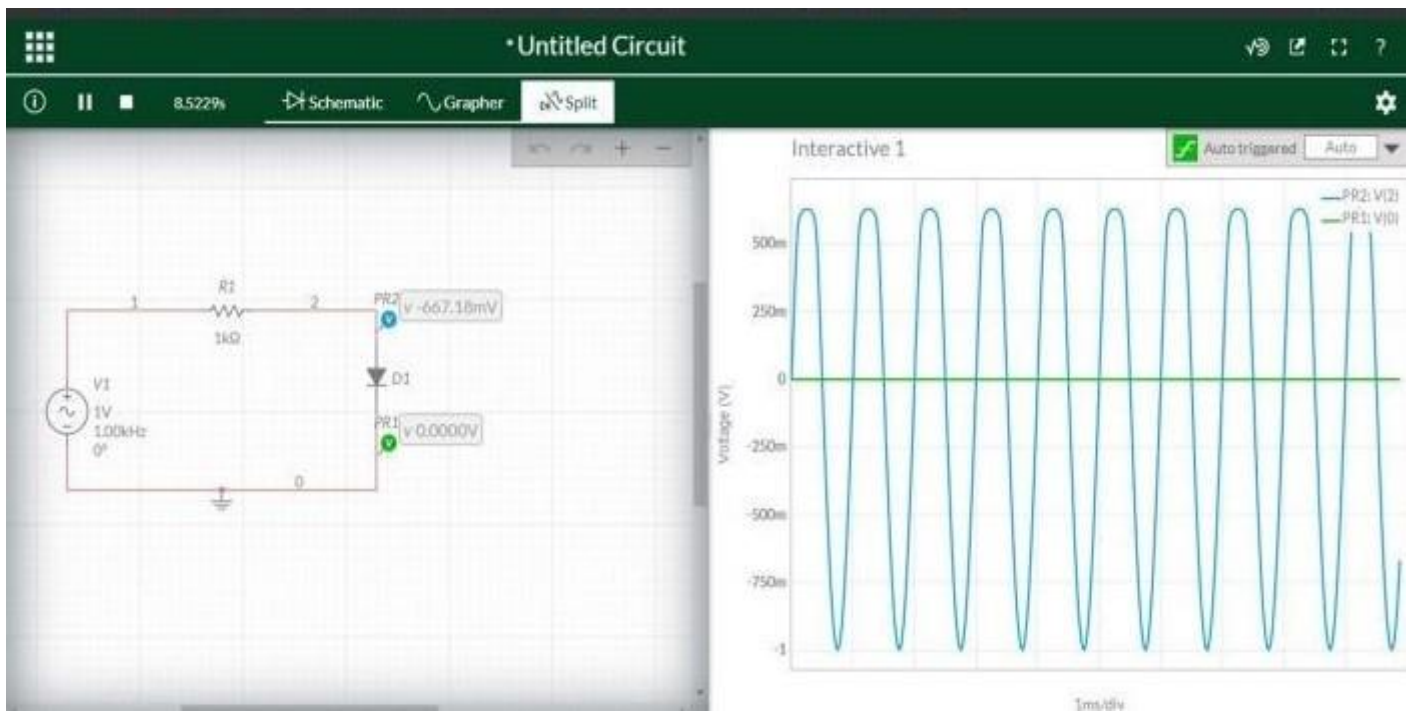

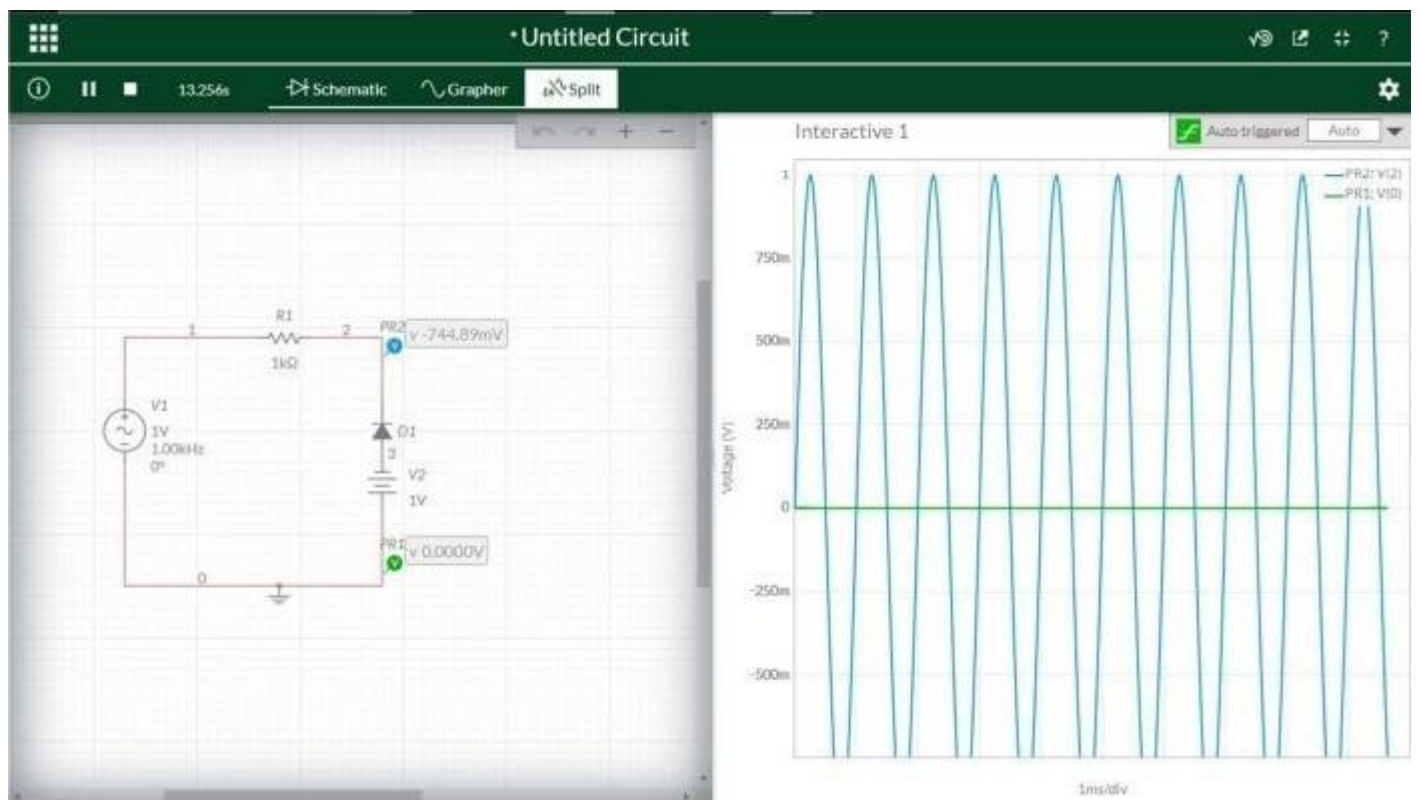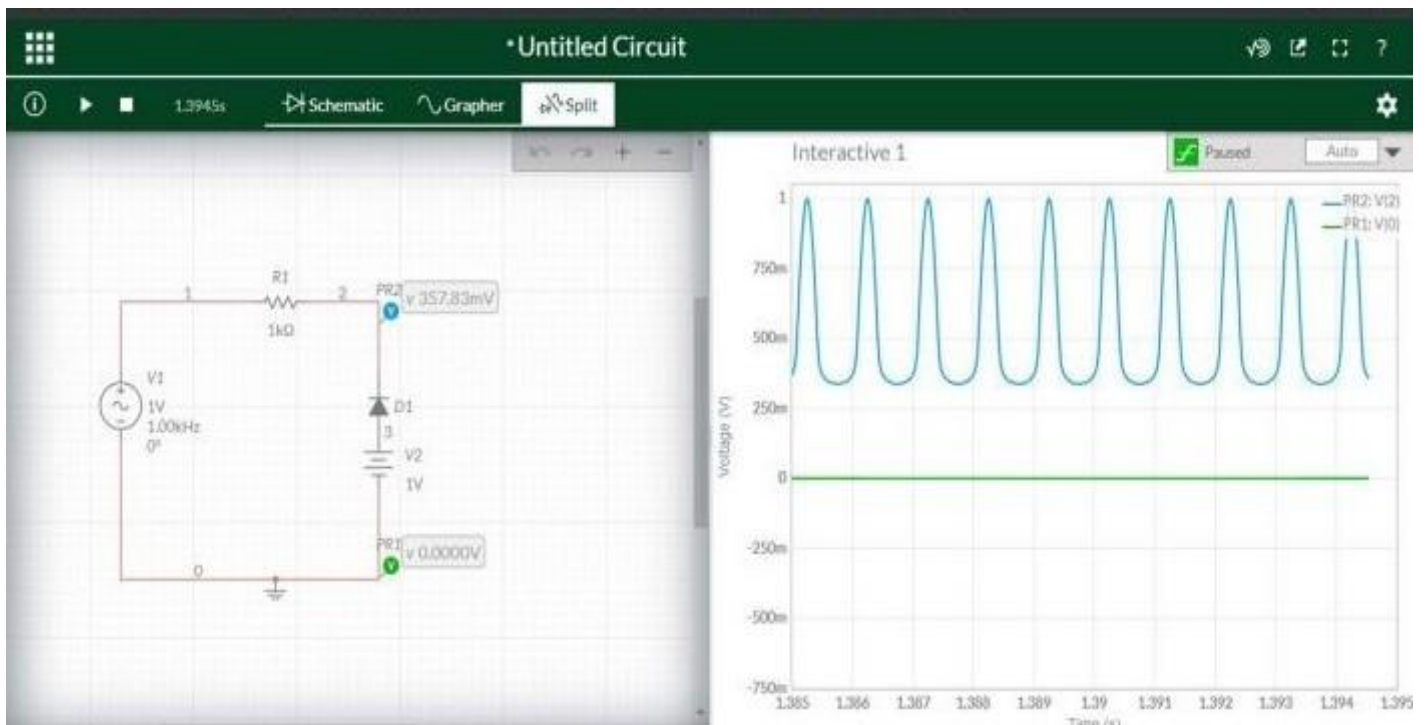BIASED PARALLEL CLIPPER CIRCUITS (IDEAL DIODES):



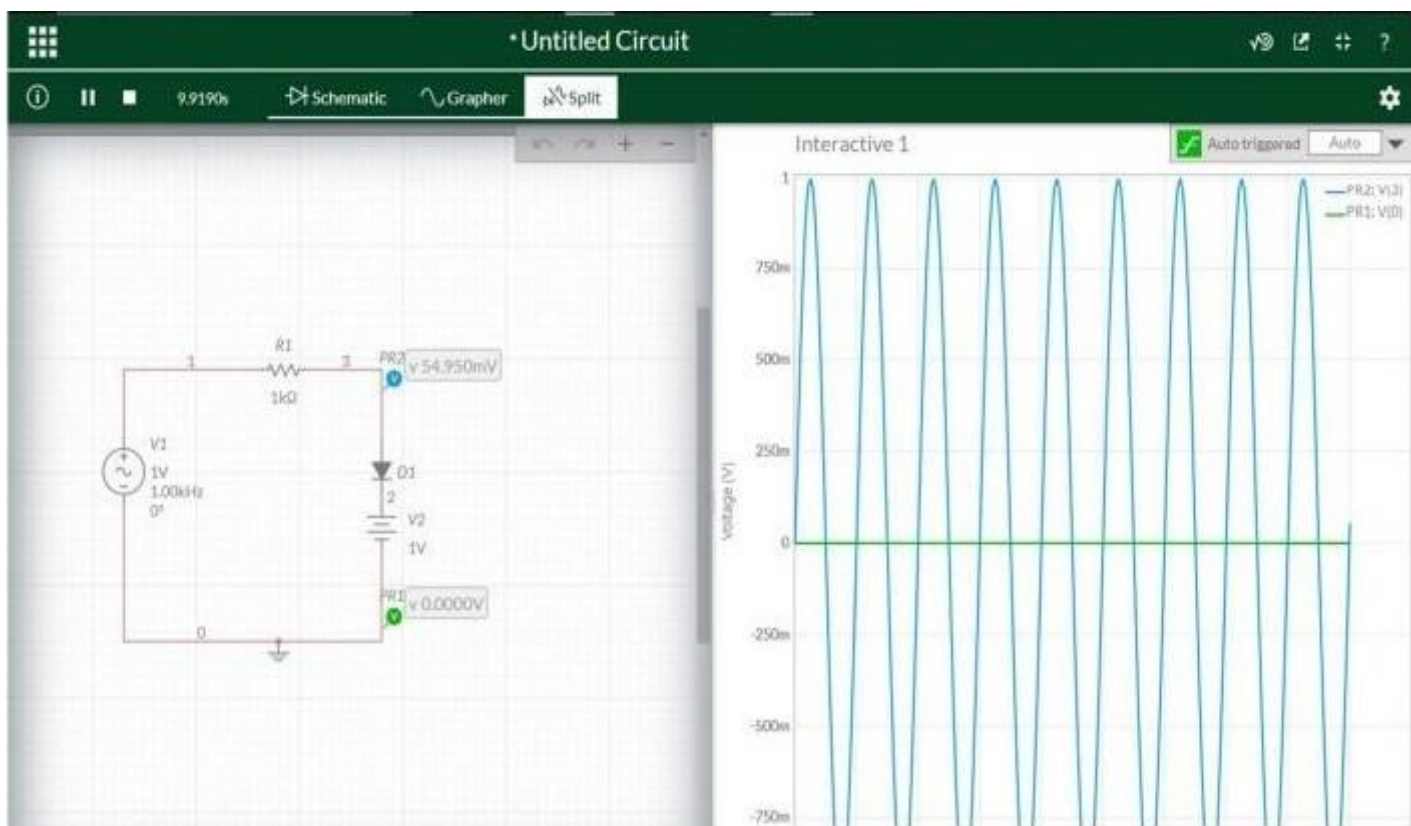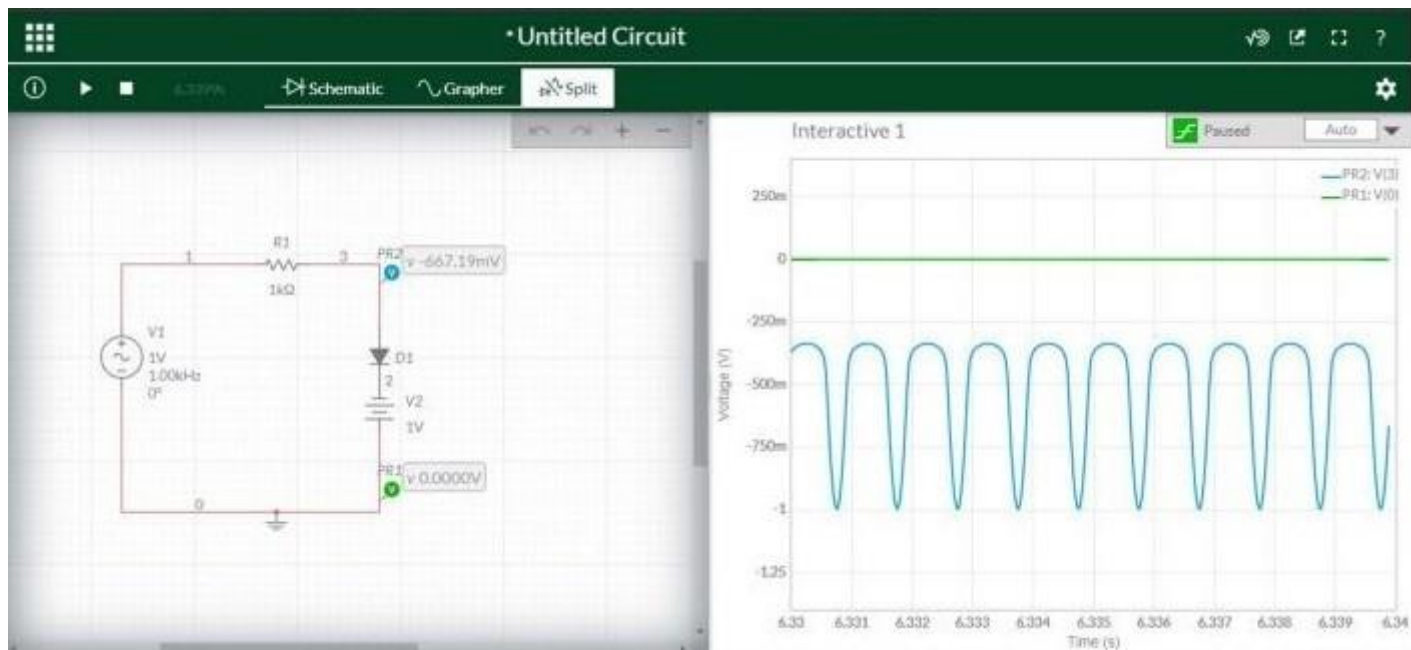

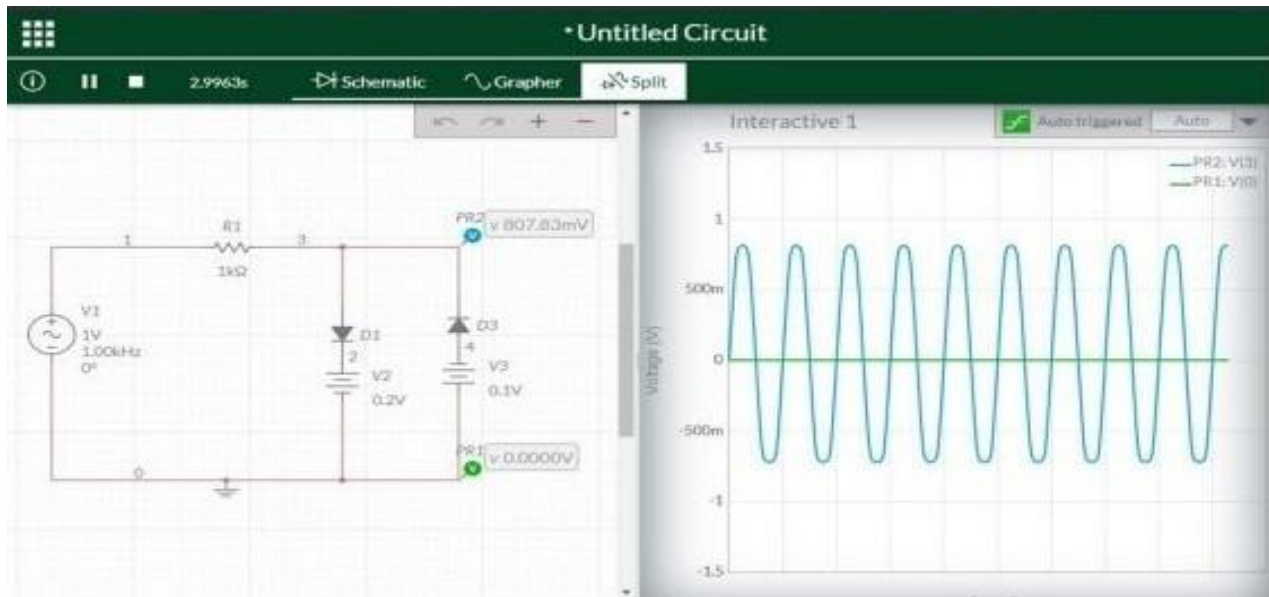


CONCLUSIONS:


Here, the theoretical and practical characteristics of various negative and positive and positive series clipper (with and without bias) are same. Hence verified.

ASSIGNMENT:

QUESTION 1-

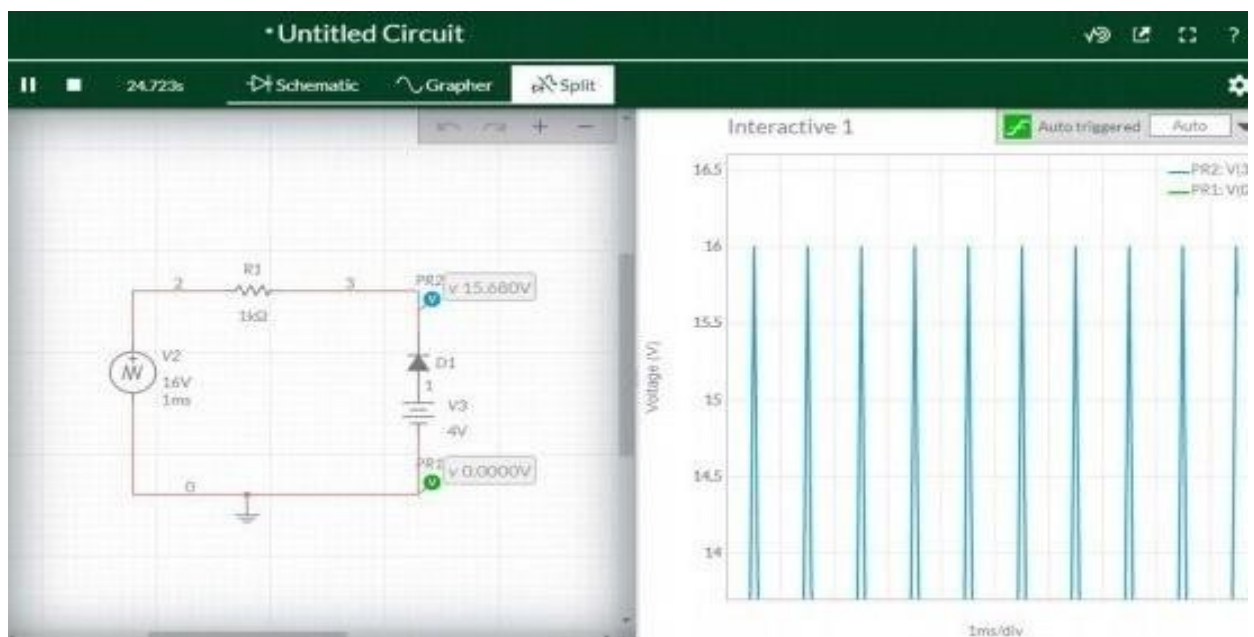


QUESTION 2:

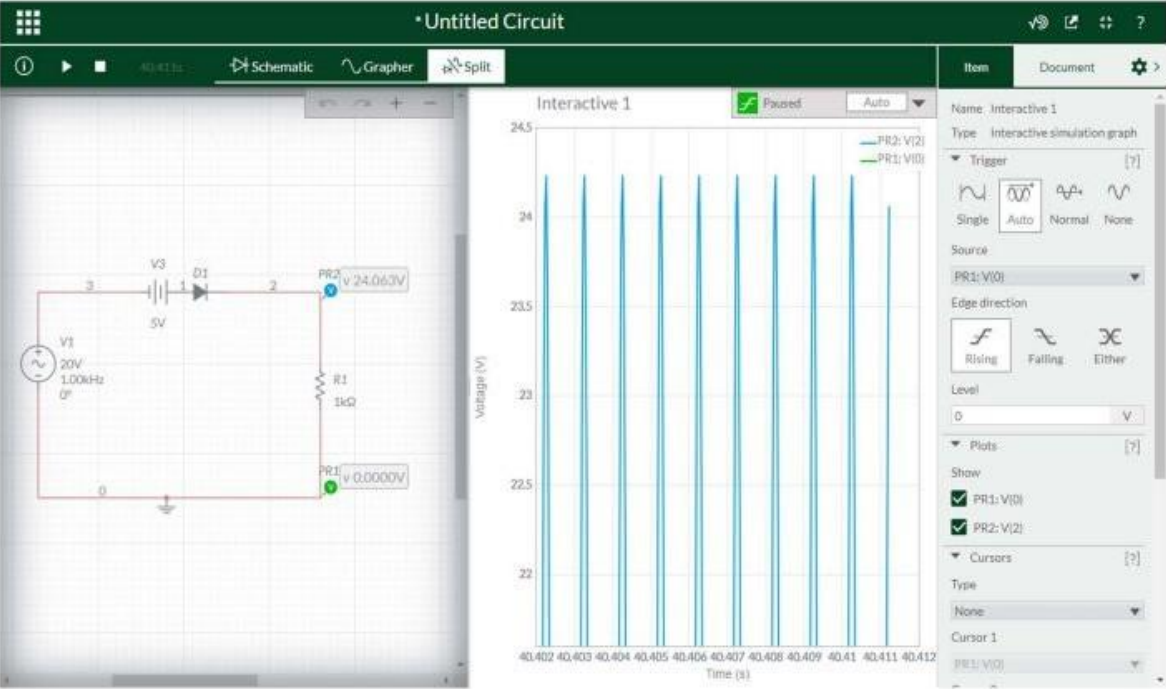



Calculations:

DELD-2 (Practical)

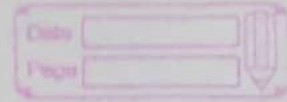

U20CS100 - ADITYA RAI

Calculations:

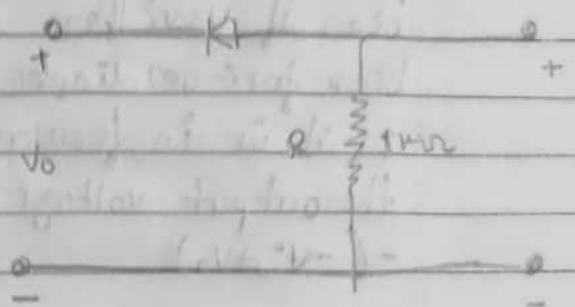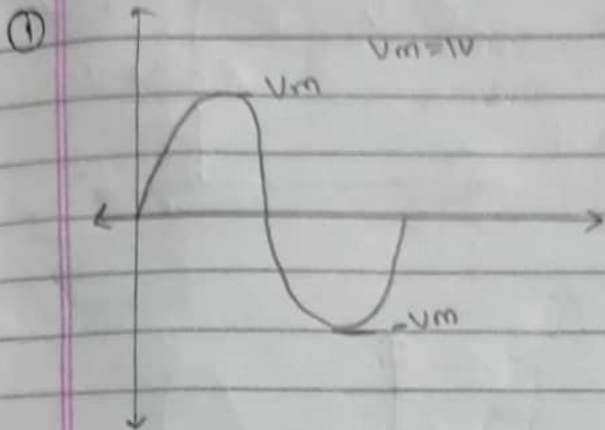

Given, here diode is ideal.

for positive cycle it is in reverse bias.

∴ The circuit opens

$$\therefore V_o = 0V$$



for negative cycle:

it is in forward bias

∴ diode behaves as

Conductor.

$$\therefore V_o = V_i = 1V$$

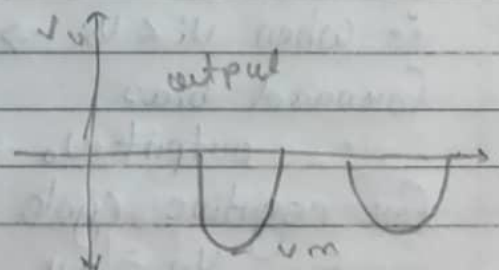
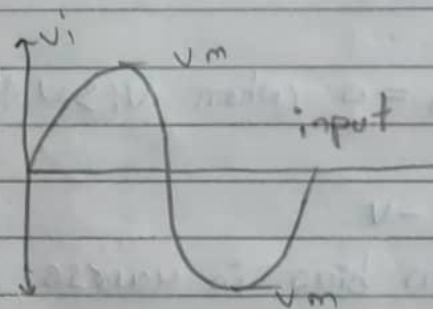


2.) → for positive cycle it is in forward bias. The diode behaves as conductor.

$$\therefore V_o = V_i = 1V$$

→ for negative cycle it is in reverse bias. The diode behaves as insulation.

$$\therefore V_o = 0V$$

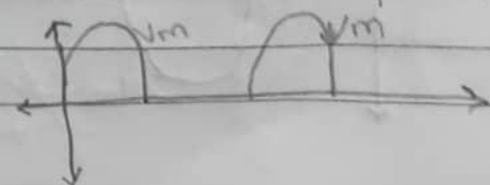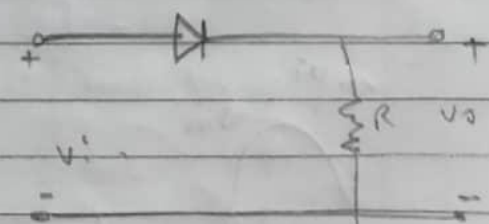

* for the circuit for positive cycle

when $V > V_i$ then it is forward




bias if $V < V_i$ then reverse

bias for (-ve) diode

as it is in forward bias

the output voltage is

$$-(-V_i + V_o)$$

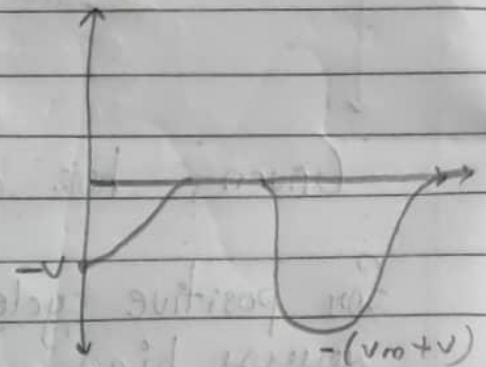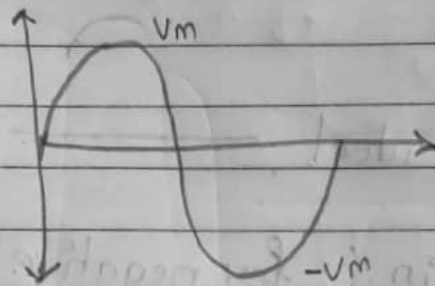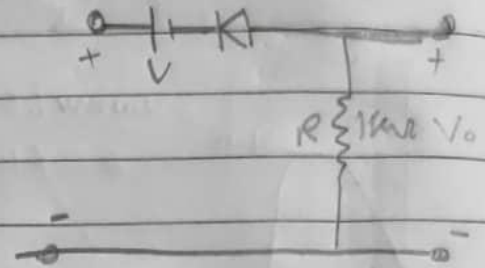



* for Positive cycle of circuit when $V_i < V_o$, then it is in reverse bias

\therefore when $V_i < V_o \Rightarrow V_o = 0$ when $V_i > V$ then forward bias

$$\therefore \text{output } V_o = V_i - V$$

for negative cycle then bias is reverse bias

$$\therefore V_o = 0 \text{ V}$$

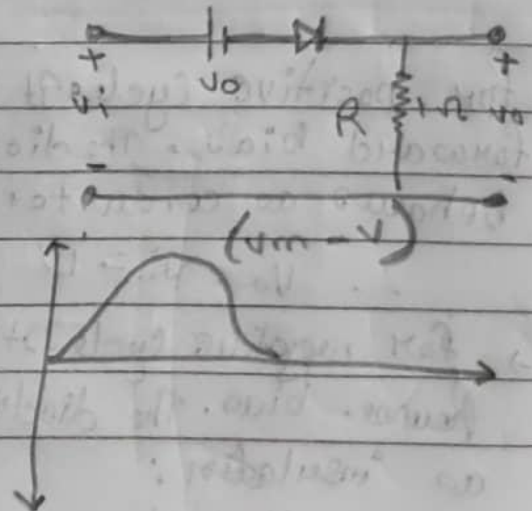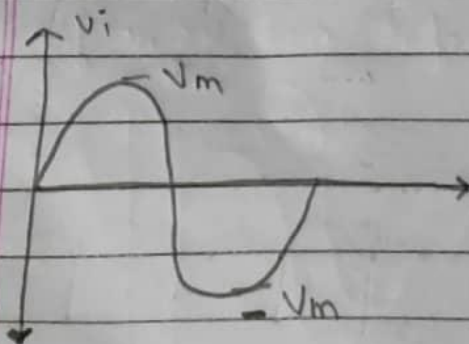

* for Positive Cycle the Circuit.




it is in reverse bias

$$\therefore V_o = 0V$$

for negative Cycle.

if $V > V_i$ then reverse.

Bias. for $V > V_i$, $V_o = 0V$.

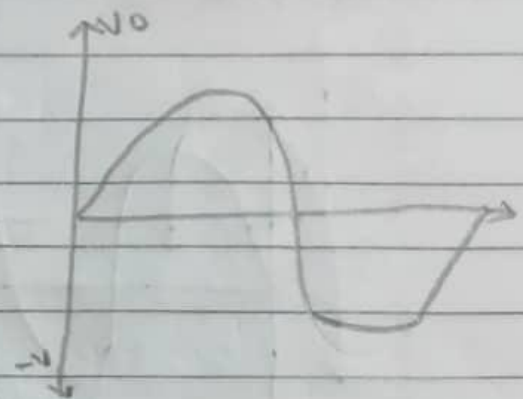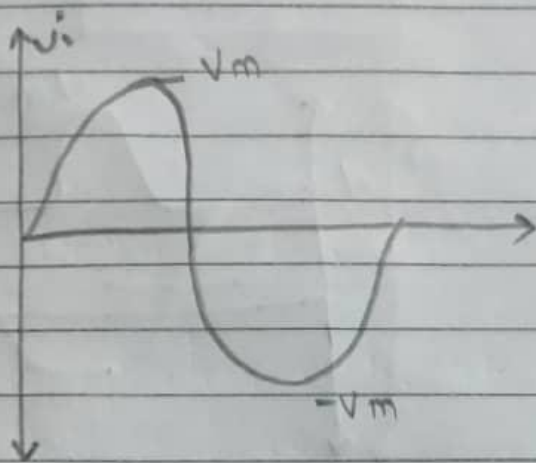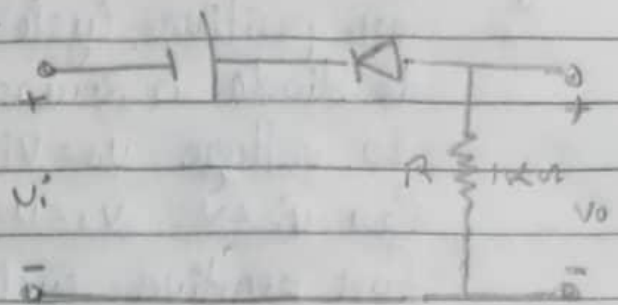

* for positive Cycle.

the diode is forward biased.

So the voltage across the load.




$$V_o = V$$

for negative cycle it is.

Reverse biased.

when $V_i > V$ the $V_o = V_i$.

if $V_i < V$ then $V_o = V$.

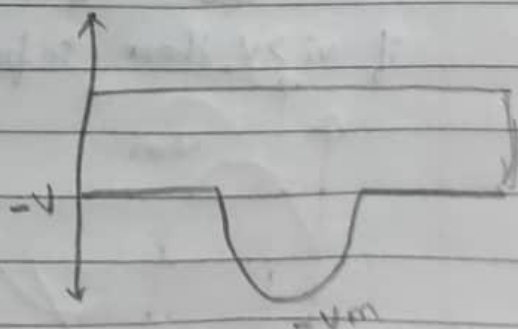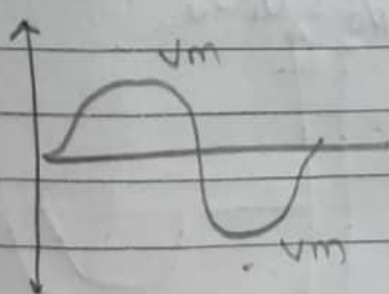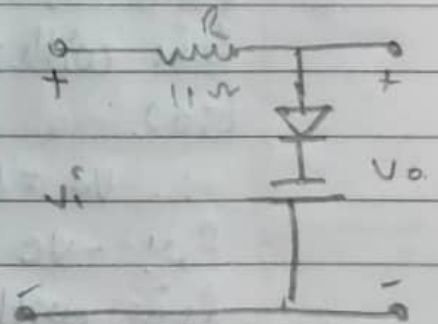

* For positive cycle




the diode is Reversed diode.

So, voltage $V_o = V_i$ ($V_i > V$)

For $V_i < V$ $V_o = V$

For negative cycle forward biased.

So, $V_o = V$.

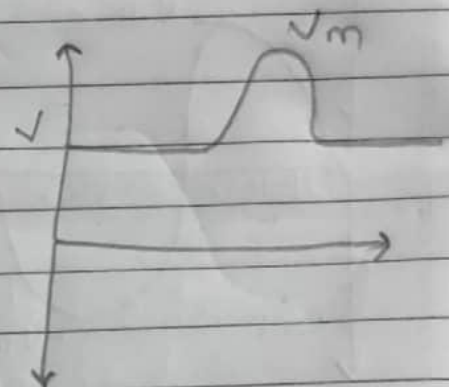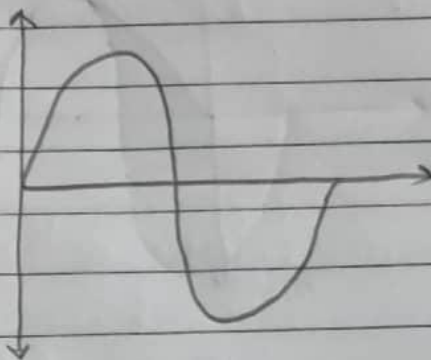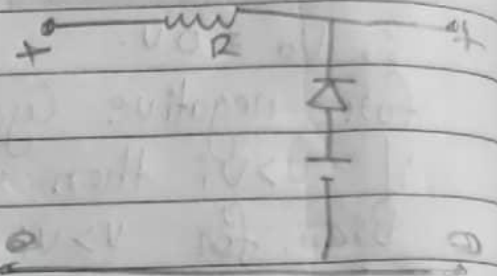

* Here For positive cycle.

line with V_1 is forward bias.




$\therefore V_o = V_1$

For -ve cycle

line with V_2 is forward biased

$\therefore V_o = V_2$

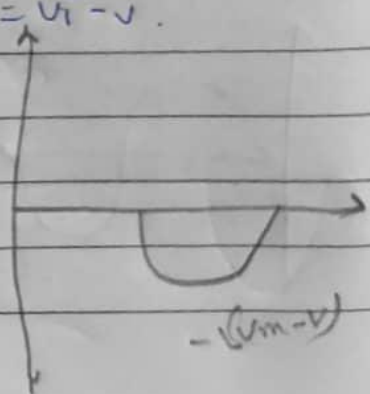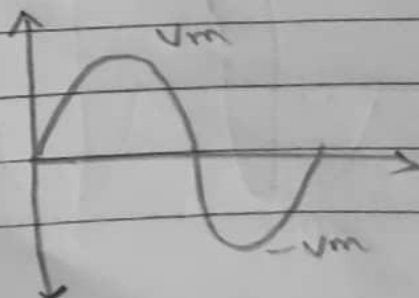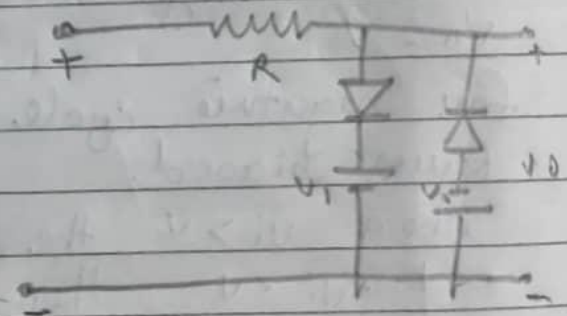if $V_i > V$, then in forward bias, $V_o = V_i - V$.



* for positive cycle it is in forward bias.




$$\therefore V_o = V_i + V$$

for negative cycle it is in reverse bias, if $V_i > V$,

$$\therefore \text{if } V_i > V \Rightarrow V_o = 0$$

$$\text{if } V_i < V$$

$$\therefore V_o = V - V_i$$

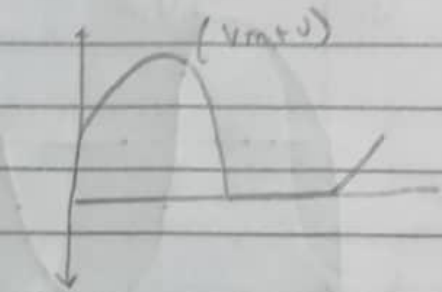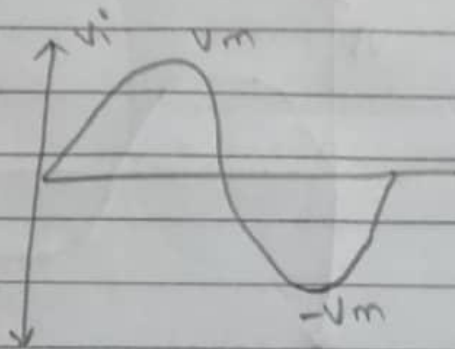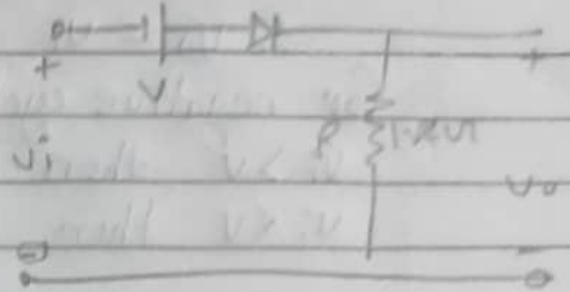

* for positive cycle when




$V > V_i$, it is in forward bias.

$$\therefore V_o = V$$

when $V_i > V$ then $V_o = 0$.

for negative cycle, it is in forward bias.

$$\therefore V_o = V_i$$

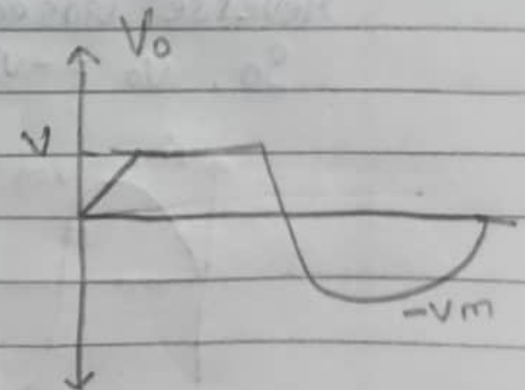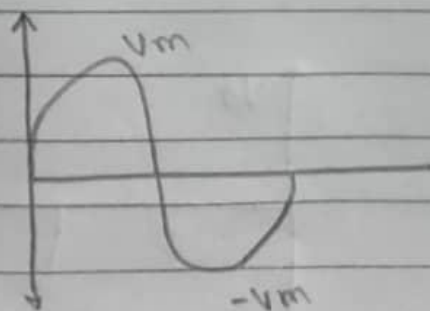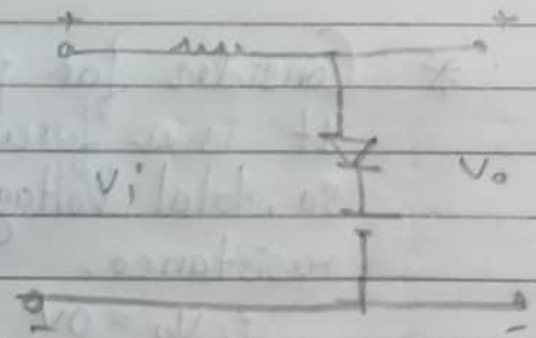




* for positive cycle then it is Reverse bias.

$$\therefore V_o = V_i$$

for negative cycle when,

$$V_i > V \text{ then } V_o = 0$$

$$V_i < V \text{ then } V_o = V$$

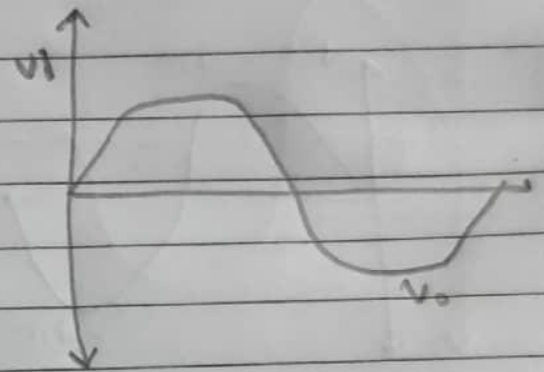
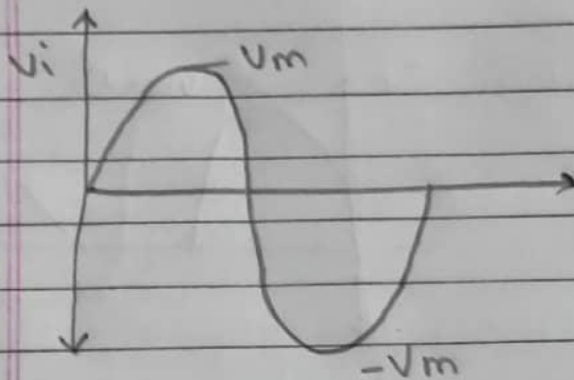
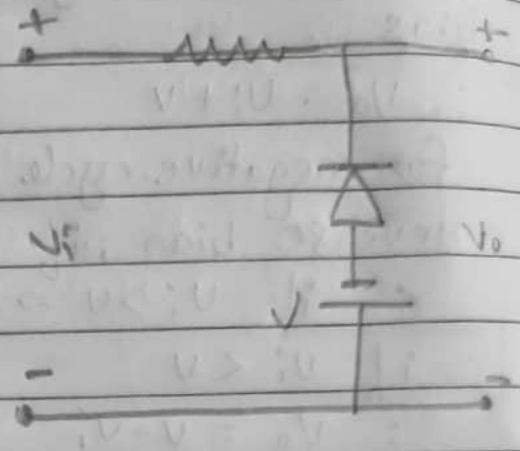


* Consider for positive cycle It is a forward biased. so, total Voltage taken by resistance.

$$\therefore V_o = 0V$$

for negative cycle, it is reverse biased.

$$\text{So, } V_o = -V_i$$

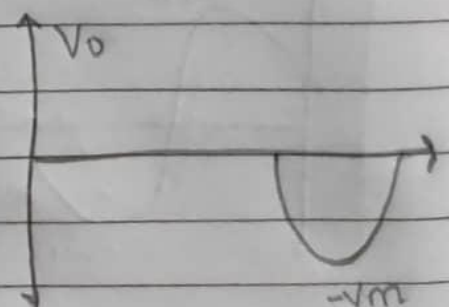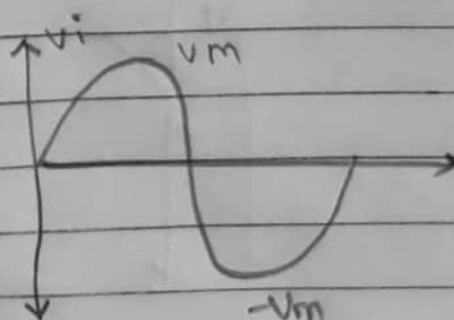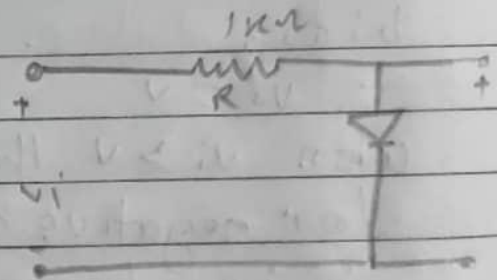

* Consider for positive cycle.
It is negative biased
(reversed), so, $V_o = 0$.
for, negative cycle
forward bias,
so, $V_o = 0$.

