

## Assignment – 5

Design a circuit to multiply two Arrays of 4 bits and 3 bits.

Follow this formula to build the circuit: If multiplicand =  $k$  bits, multiplier =  $j$  bits then  $(j * k)$  AND gates and  $(j-1)$   $k$  bit adders are required to produce a result. Use your own adders to build the circuits.