

Assignment – 4

Use Logisim software to create and store the followings circuits for further usage:

1. 1-bit Half Adder

Build a 1-bit half adder. This takes two input wires, x_0 and x_1 , and generates two output wires, s for the sum and c for the carry.

2. 1-bit Full Adder

The half-adder from the previous exercise can't be composed to make larger adders because it doesn't take a carry input, which is necessary if we're to chain them. Build a 1-bit full adder which takes c_{in} , x_0 , and x_1 as inputs, and generates s and c . (Note that we don't need any additional outputs here.)

3. 1-bit Half Subtractor

Build a 1-bit half subtractor. This takes two input wires, x_0 and x_1 , and generates two output wires, D for the difference and c for the borrow.

4. 1-bit Full Subtractor

Build a 1-bit full subtractor which takes $c_{in}(\text{Borrow})$, x_0 , and x_1 as inputs, and generates $D(\text{Difference})$ and $c(\text{Borrow})$.

Use Logisim software to create and store the followings circuits (Note: use the above circuits for implementation):

1. Implement 2 bit full adder.
2. Implement 2 bit full subtractor.

Use Logisim software to create and store the followings circuits (Note: use the above circuits for implementation):

1. Implement 4 bit full adder.
2. Implement 4 bit full subtractor.

Use Logisim software to create and store the followings circuits (Note: use the above circuits for implementation):

1. Implement 8 bit full adder.
2. Implement 8 bit full subtractor.