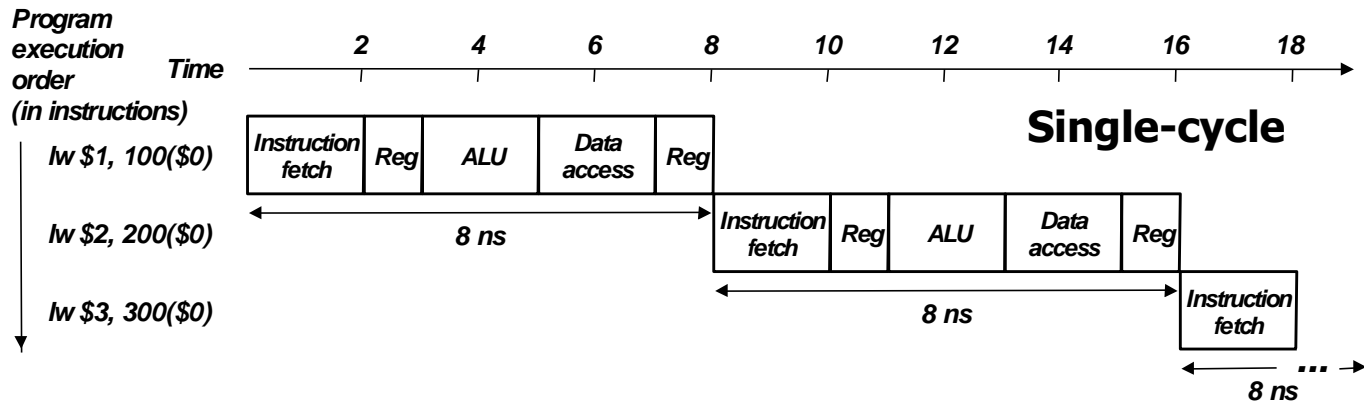


***Enhancing Performance
with
PIPELINING***


Pipelining

- ***Pipeline concepts***
- ***Hazards***
- ***Example***

Pipelined vs. Single-Cycle Instruction Execution



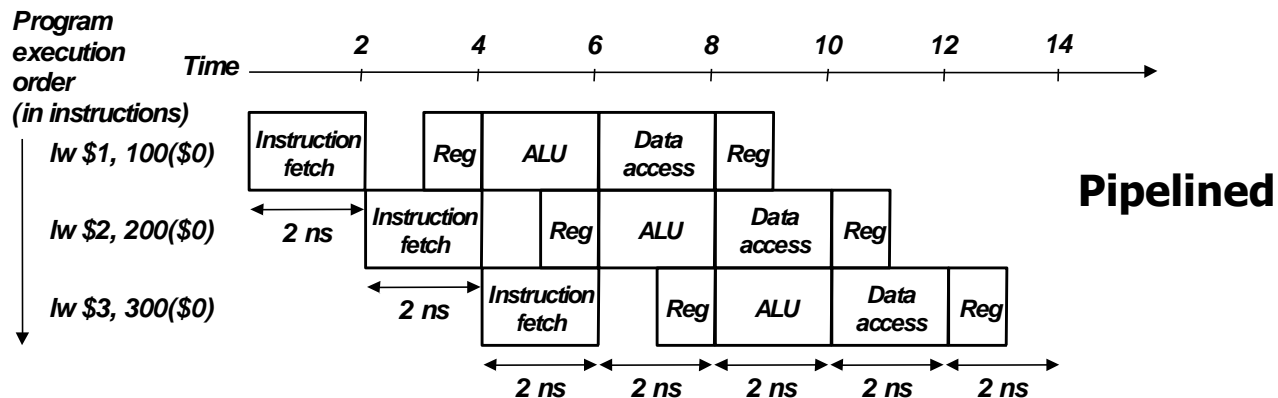Assume 2 ns for memory access, ALU operation; 1 ns for register access; therefore, single cycle clock 8 ns; pipelined clock cycle 2 ns.



Pipeline Implementation

- ***Pipelining***
 - ***Goal of MIPS: (Clock cycles Per Instruction) CPI ≤ 1***
 - ***Some instructions take longer to execute than others***
 - ***Don't want cycle time to depend on slowest instruction***
 - ***Want 100% hardware utilization***
 - ***Split execution of each instruction into several, balanced "stages"***
 - ***Each stage is a block of combinational logic***
 - ***Latency of each stage fits within 1 clock cycle***
 - ***Insert registers between each pipeline stage to hold intermediate results***
 - ***Execute each of these steps in parallel for a sequence of instructions***

Pipelining MIPS

- ***MIPS characteristics make pipelining easy***
 - ***All instructions are approx. same length***
 - ***Fetch and decode stages are similar for all instructions***
 - ***Just a few instruction formats***
 - ***Simplifies instruction decode and makes it possible in one stage***
 - ***Memory operands appear only in load/stores***
 - ***Memory access can be deferred to exactly one later stage***
 - ***Operands are aligned in memory***
 - ***One data transfer instruction requires one memory access stage***

MIPS pipeline stages


- ***Fetch (IF)***
 - *Read next instruction from memory*
 - *Increment address counter*
- ***Decode (ID)***
 - *Read register operands,*
 - *Resolve instruction in control signals*
 - *Compute branch target*
- ***Execute (EX)***
 - *Execute arithmetic/resolve branches*
- ***Memory (MEM)***
 - *Perform load/store accesses to memory*
 - *Take branches*
- ***Write back (WB)***
 - *Write arithmetic results to register file*

Pipelined Datapath

Recall the 5 steps in instruction execution

- 1. Instruction Fetch & PC Increment (IF)***
- 2. Instruction Decode and Register Read (ID)***
- 3. Execution or calculate address (EX)***
- 4. Memory access (MEM)***
- 5. Write result into register (WB)***


Review - Single-Cycle Datapath “Steps”

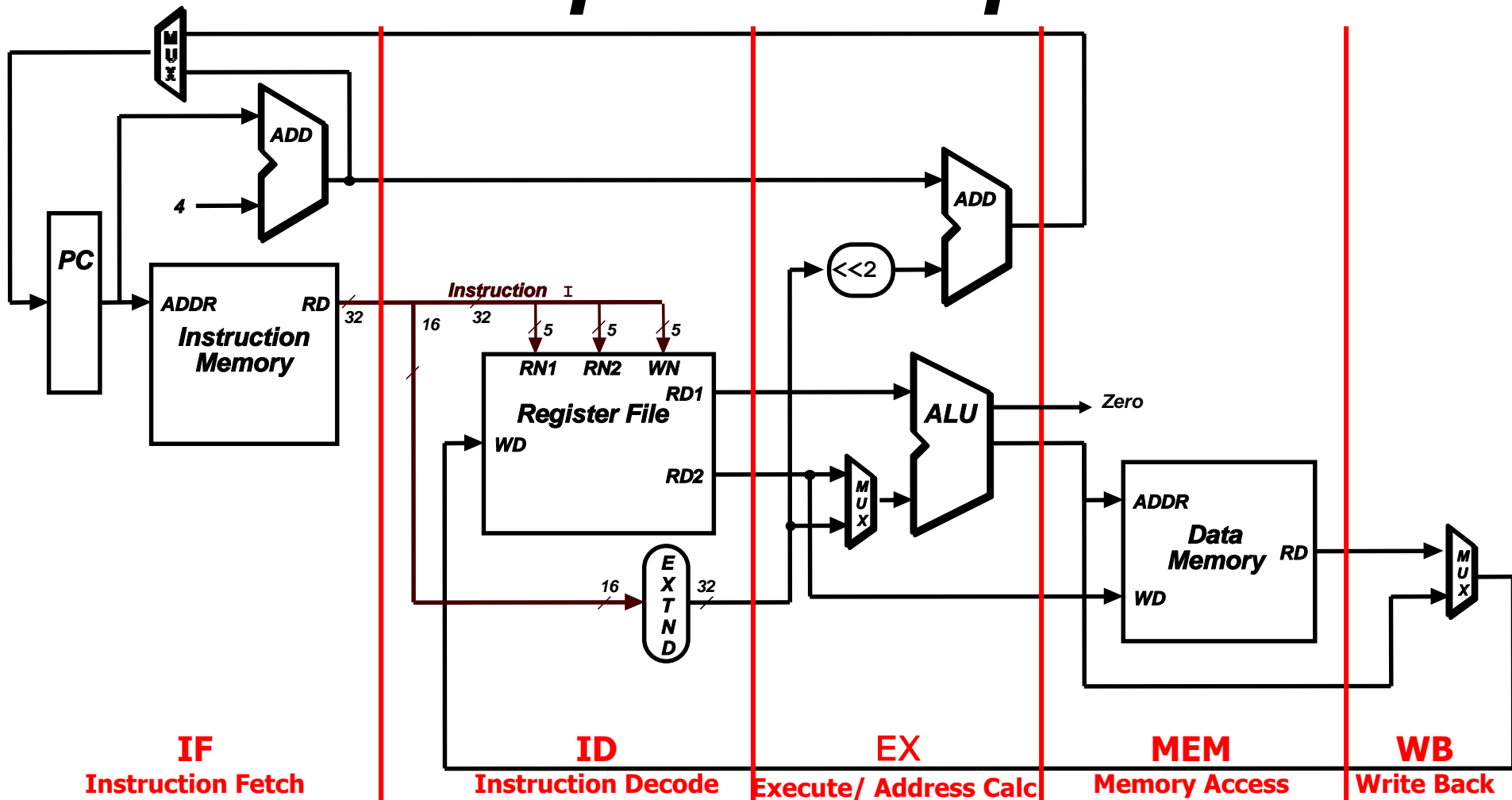


Pipelined Datapath – Key Idea

- What happens if we break the execution into multiple cycles, but keep the extra hardware?
 - ***Answer:*** We may be able to start executing a new instruction at each clock cycle - ***pipelining***
- ***...but we shall need extra registers to hold data between cycles – pipeline registers***


Pipelined Datapath

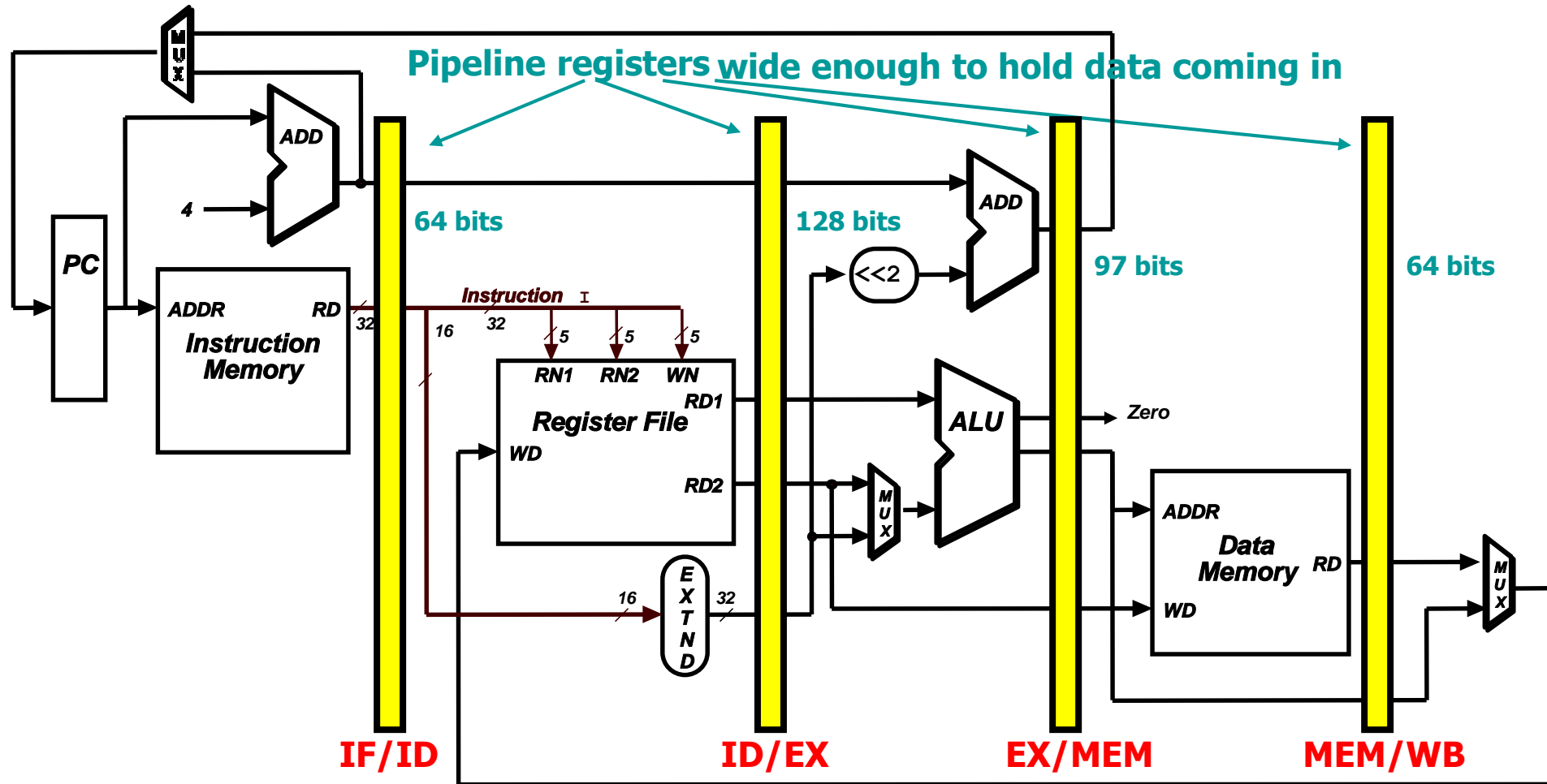

Pipelined Datapath

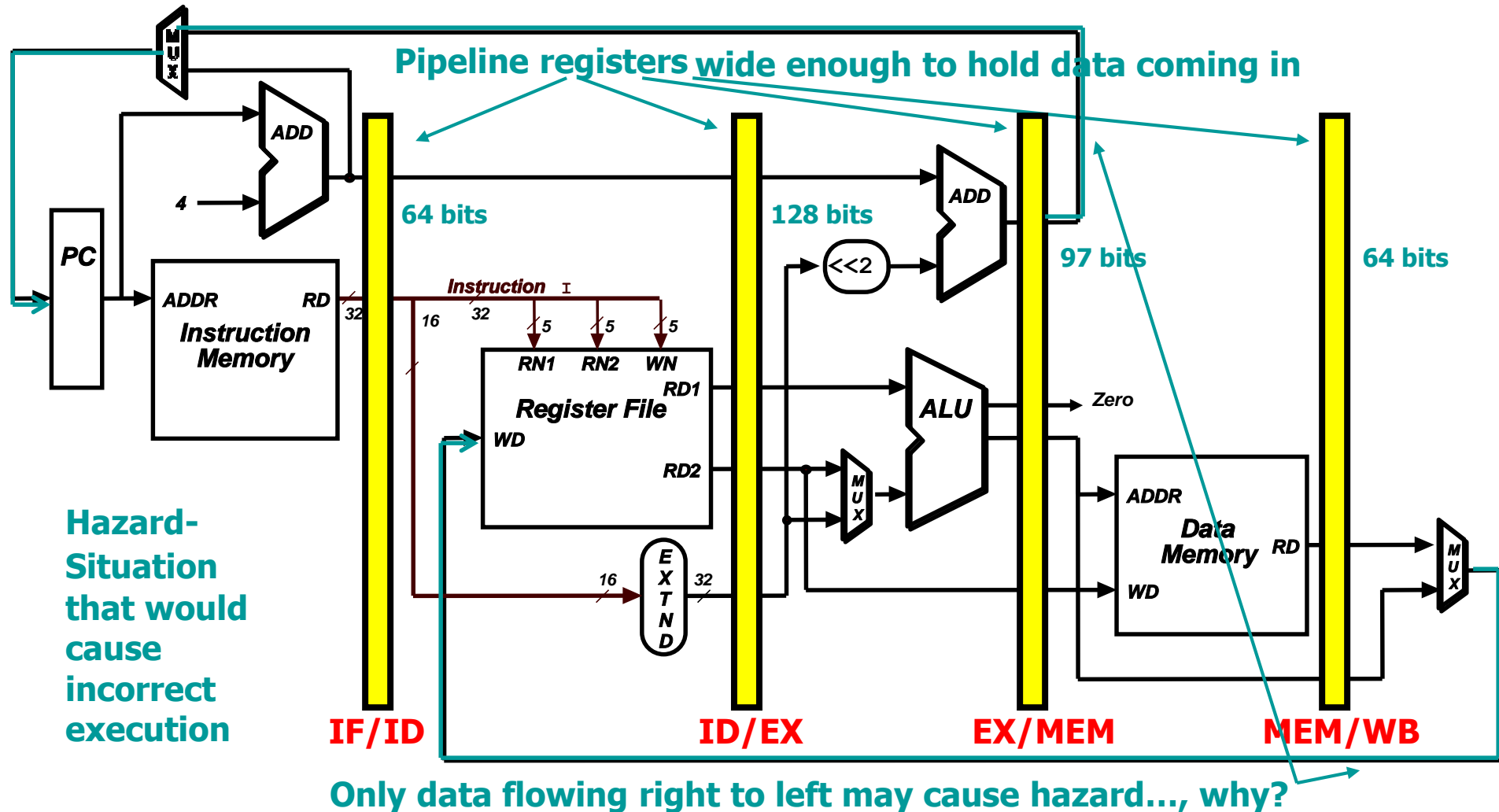


Bug in the Datapath

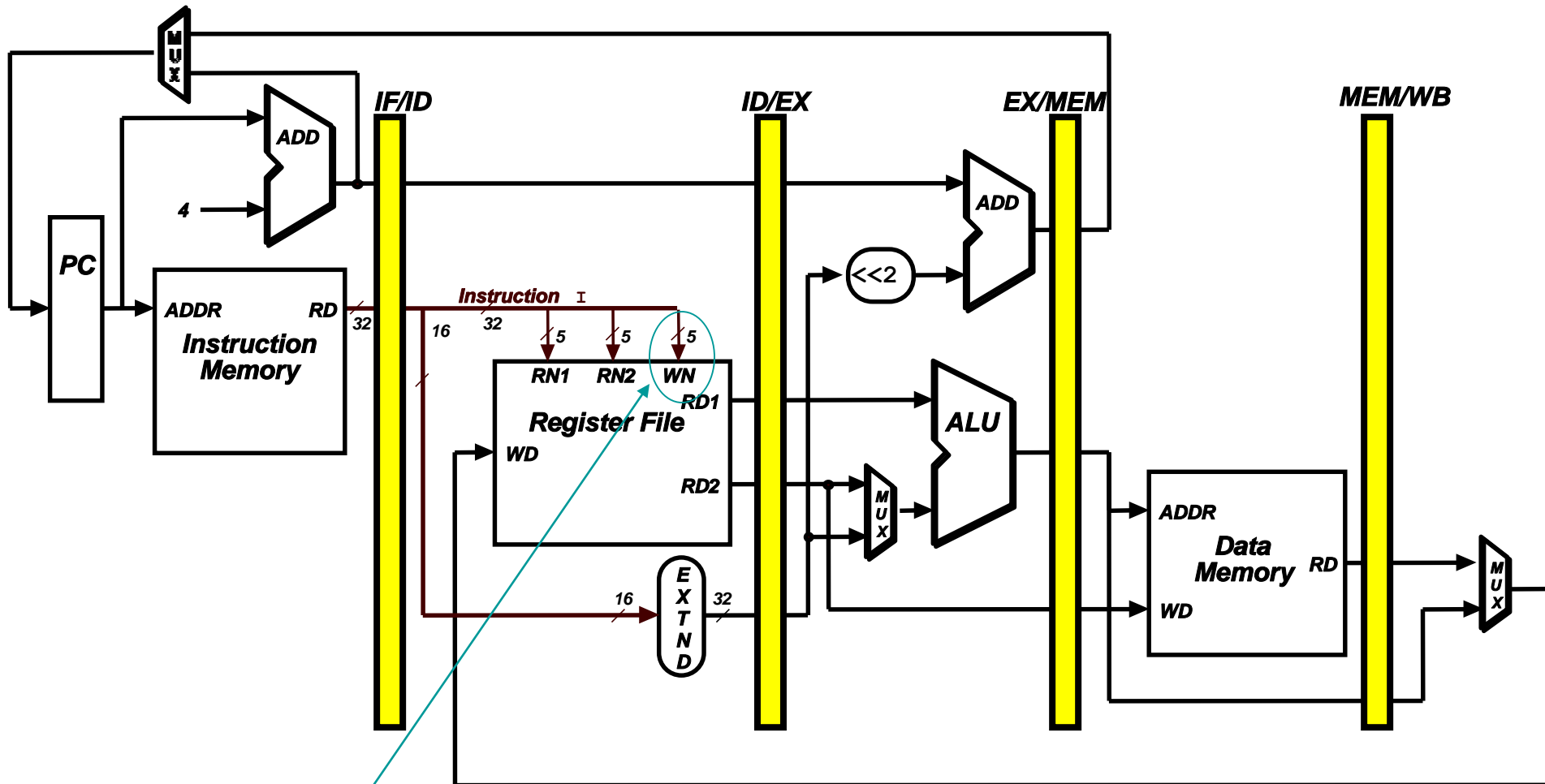

Write register number comes from another *later* instruction!

Corrected Datapath

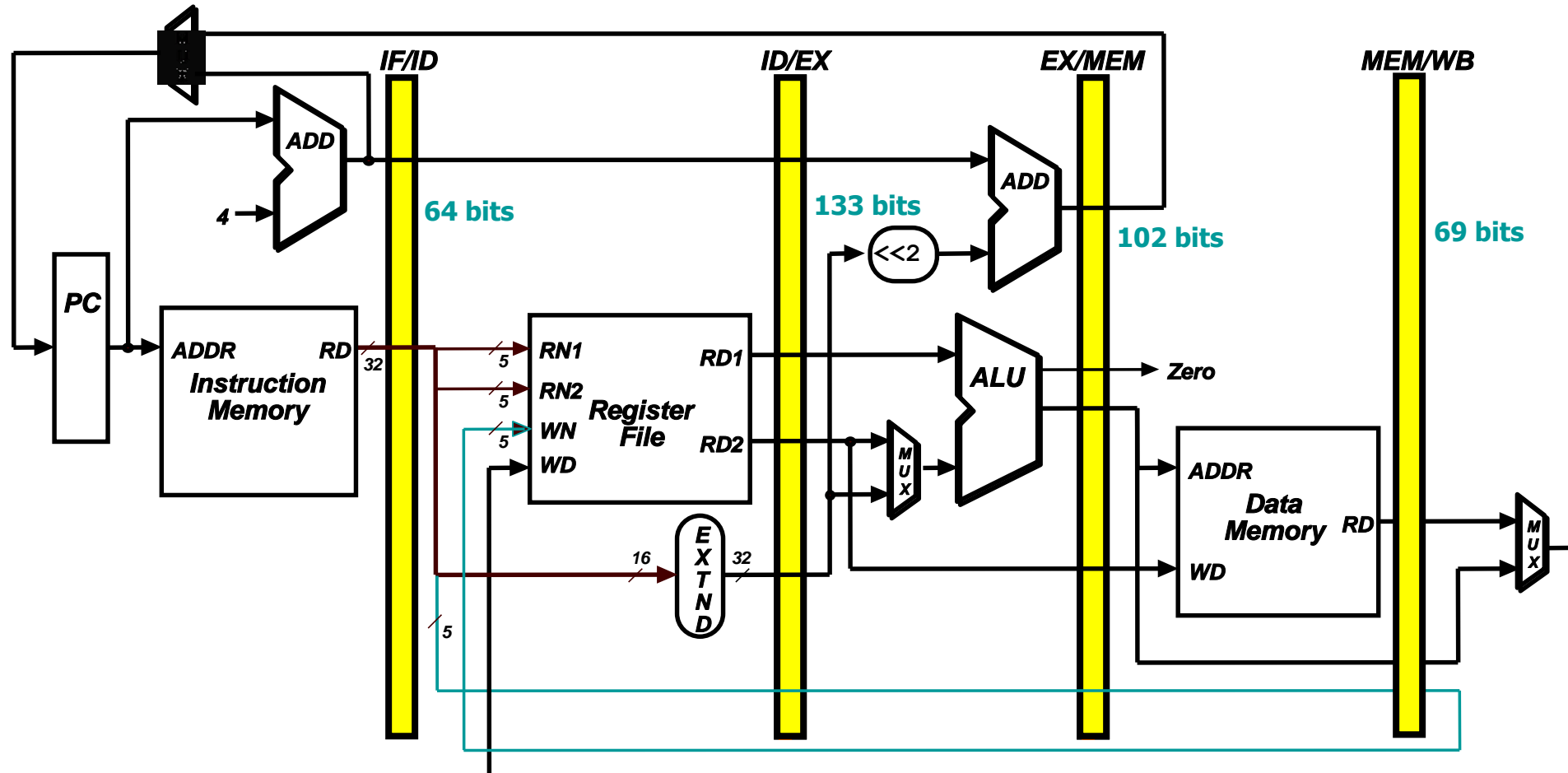

Destination register number is also passed through ID/EX, EX/MEM and MEM/WB registers, which are now wider by 5 bits

Pipelined Example

- ***Consider the following instruction sequence:***


```
lw    $t0, 10($t1)
```

```
sw    $t3, 20($t4)
```

```
add   $t5, $t6, $t7
```


```
sub   $t8, $t9, $t10
```

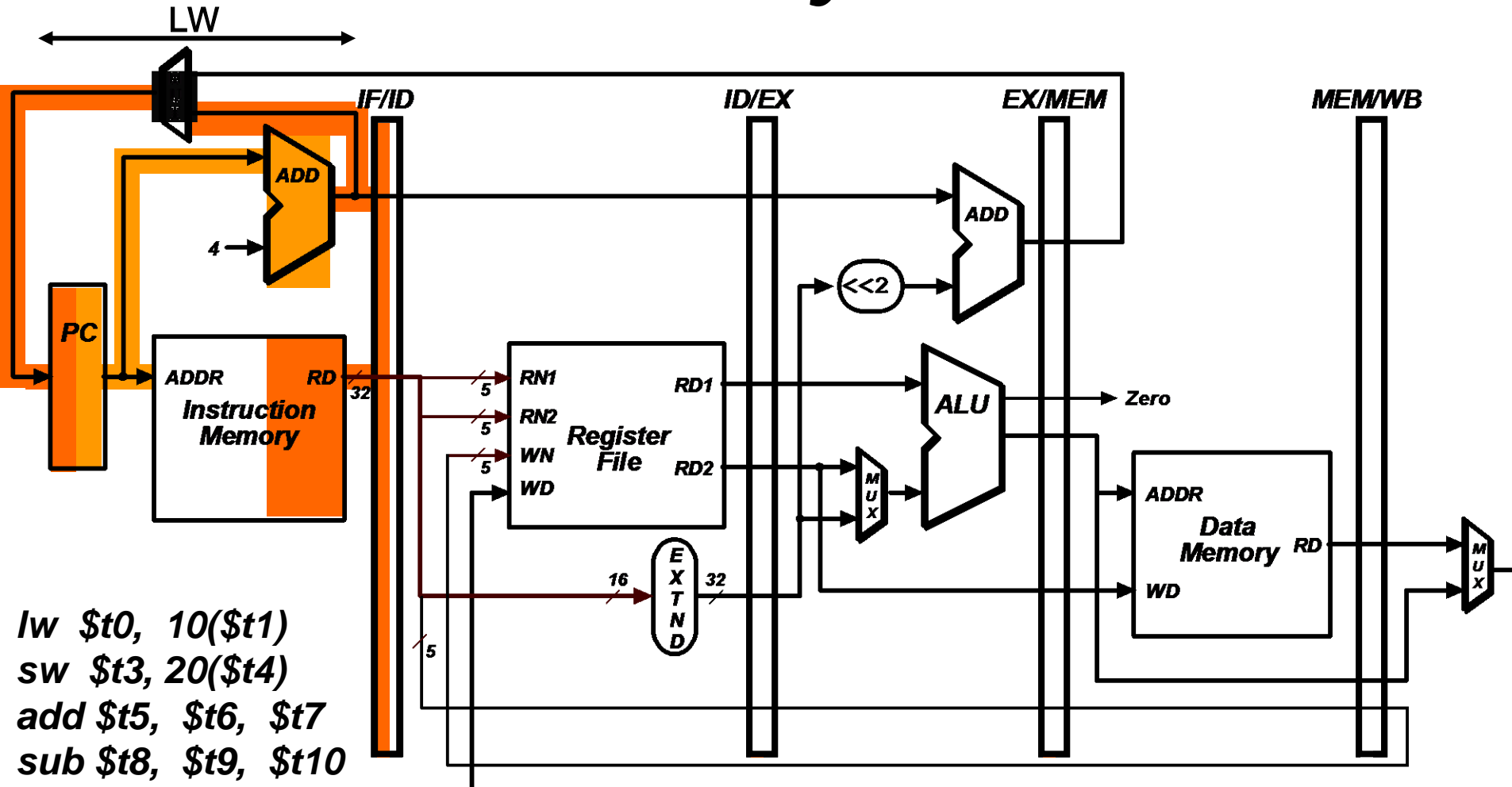Single-Clock-Cycle Diagram: Clock Cycle 1




```
lw $t0, 10($t1)
sw $t3, 20($t4)
add $t5, $t6, $t7
sub $t8, $t9, $t10
```

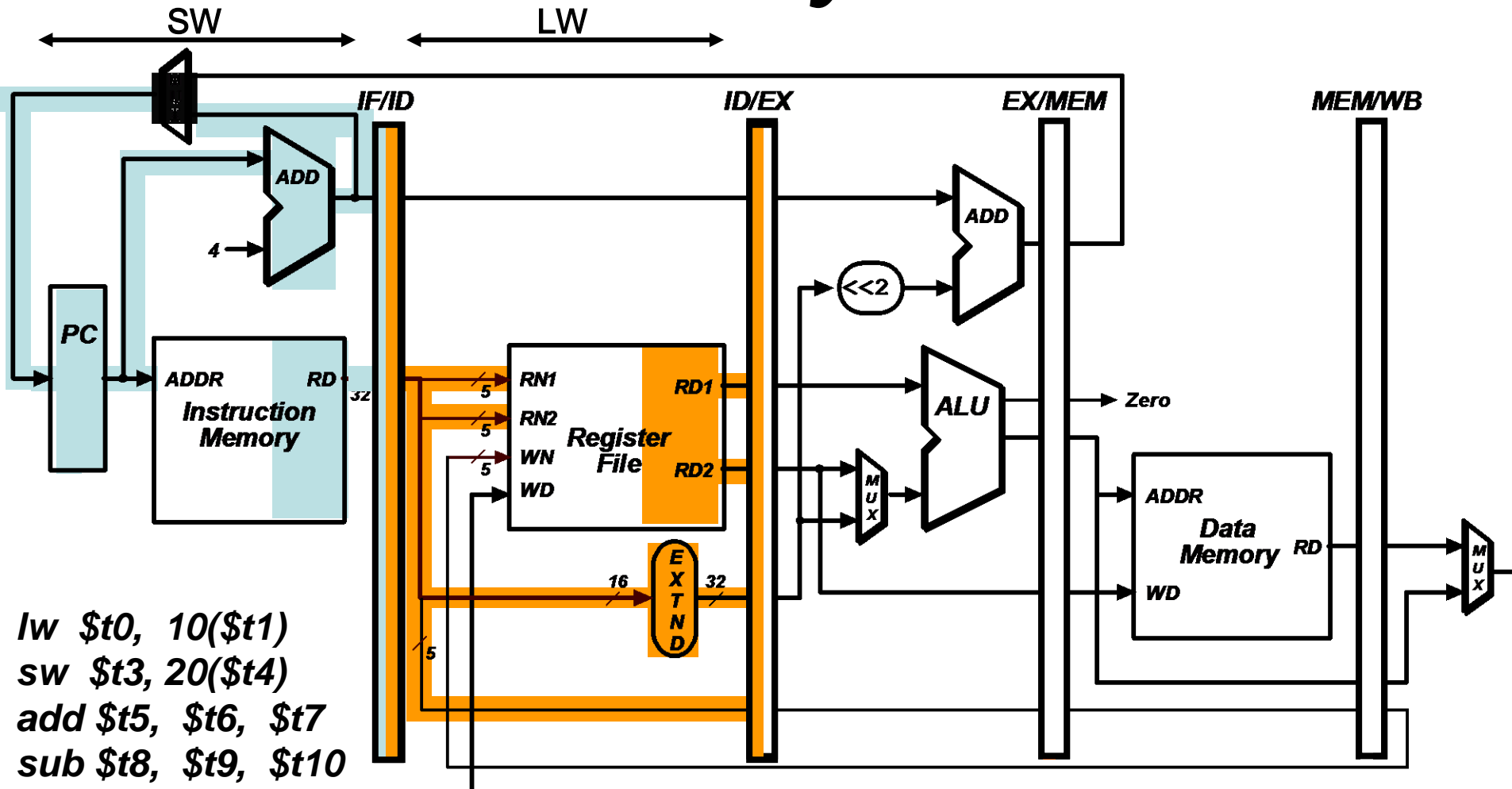
Single-Clock-Cycle Diagram: Clock Cycle 2



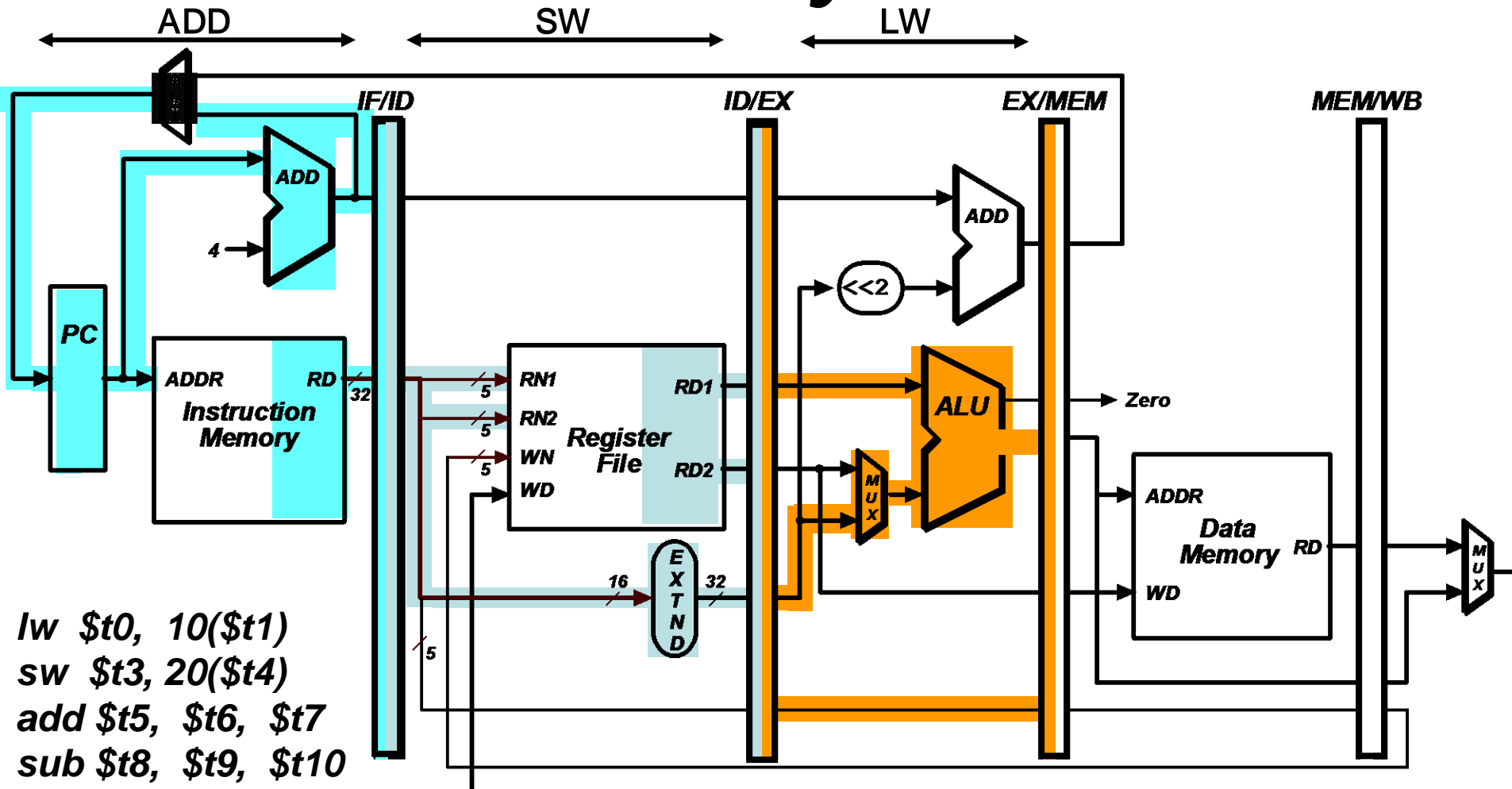Single-Clock-Cycle Diagram: Clock Cycle 3




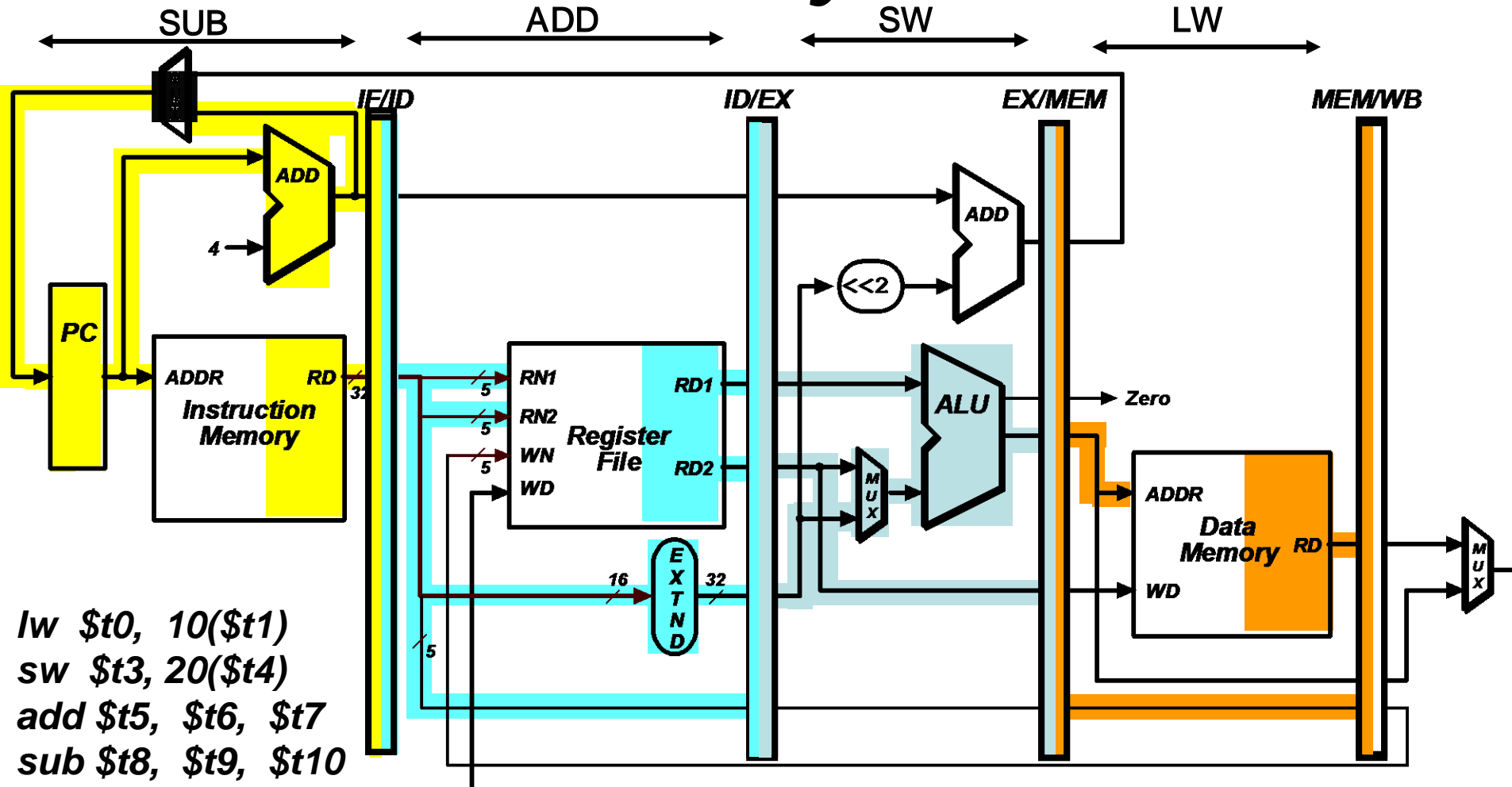Single-Clock-Cycle Diagram: Clock Cycle 4




```
lw $t0, 10($t1)
sw $t3, 20($t4)
add $t5, $t6, $t7
sub $t8, $t9, $t10
```

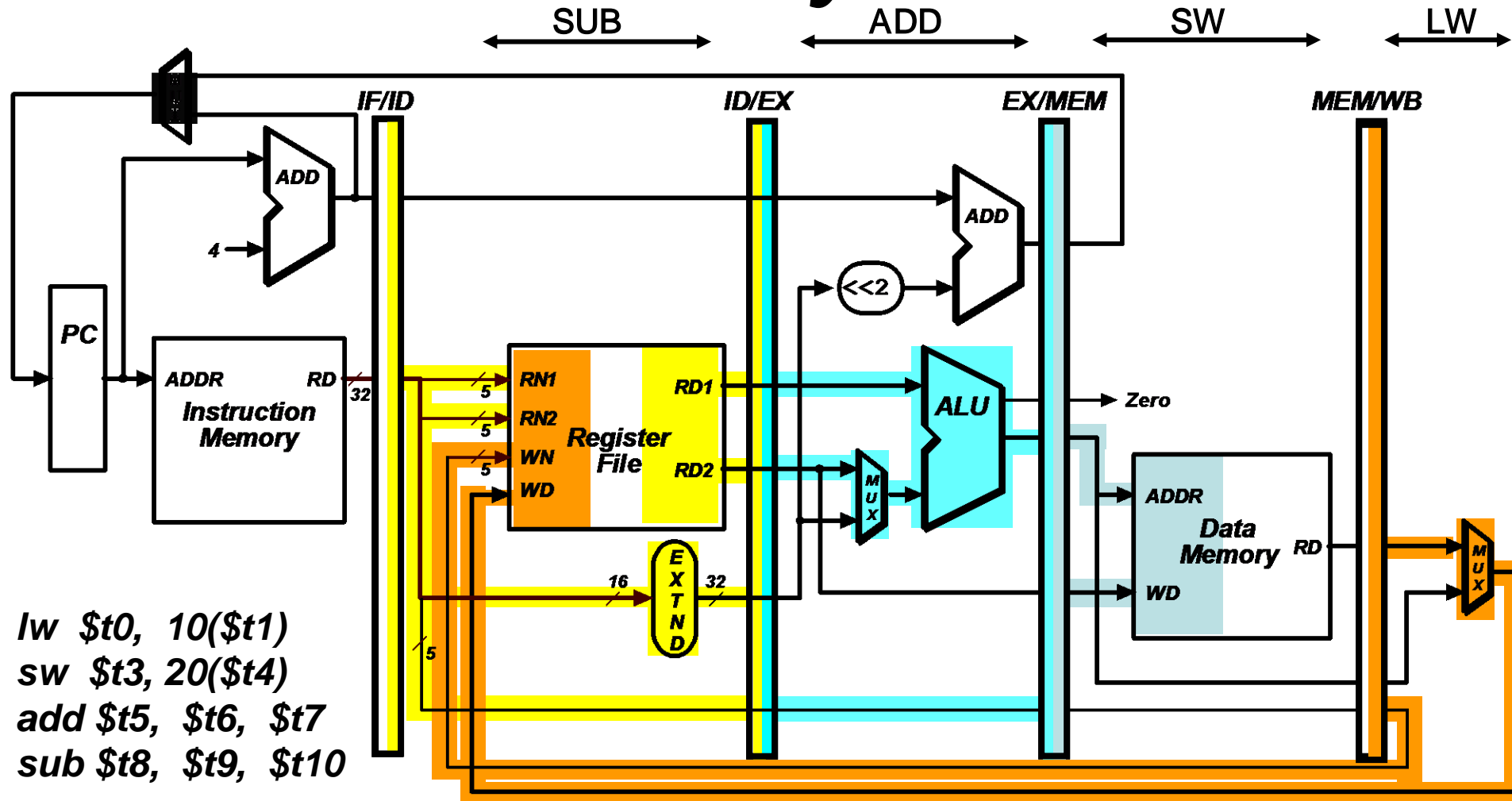
Single-Clock-Cycle Diagram: Clock Cycle 5



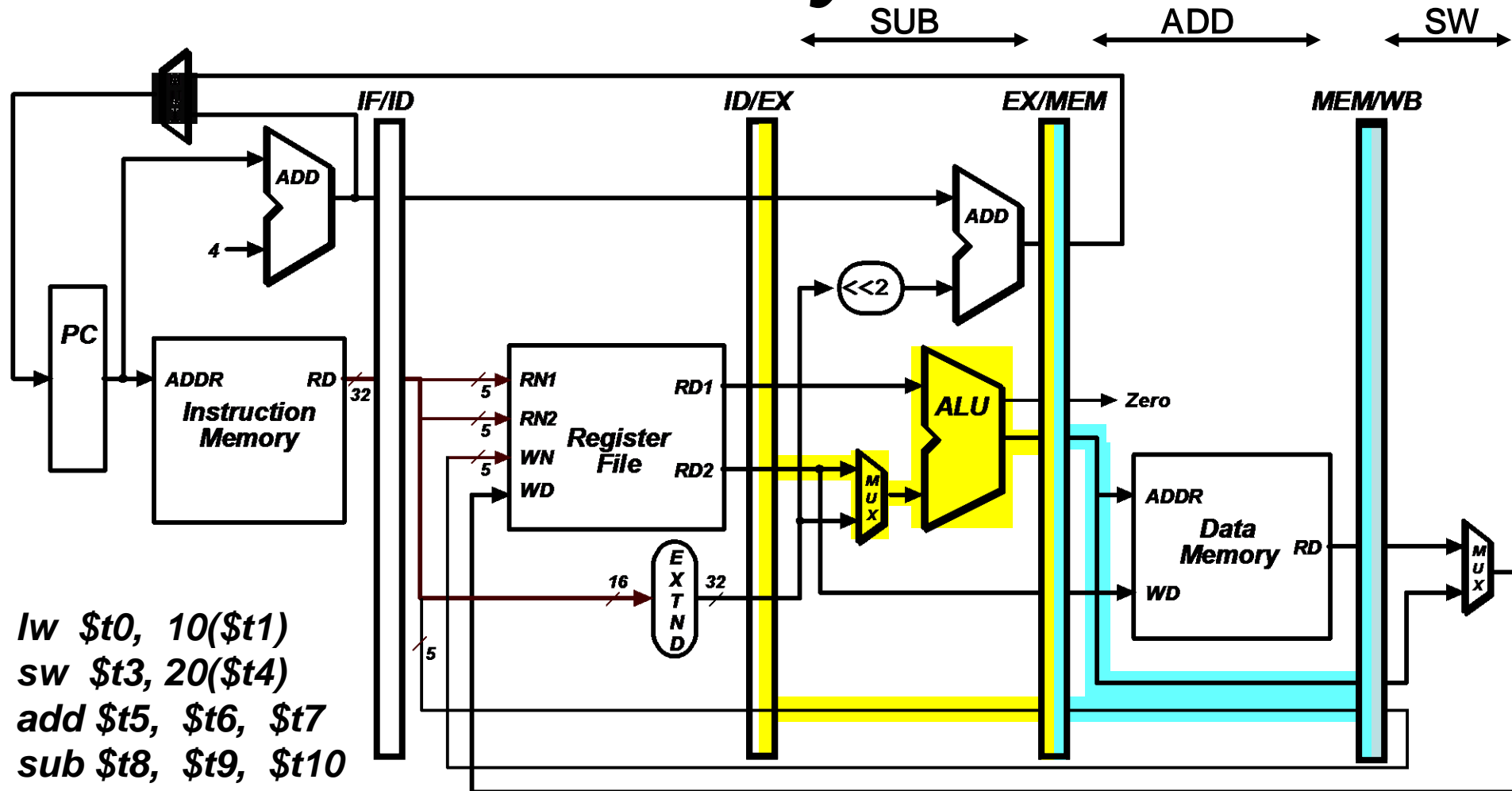Single-Clock-Cycle Diagram: Clock Cycle 6




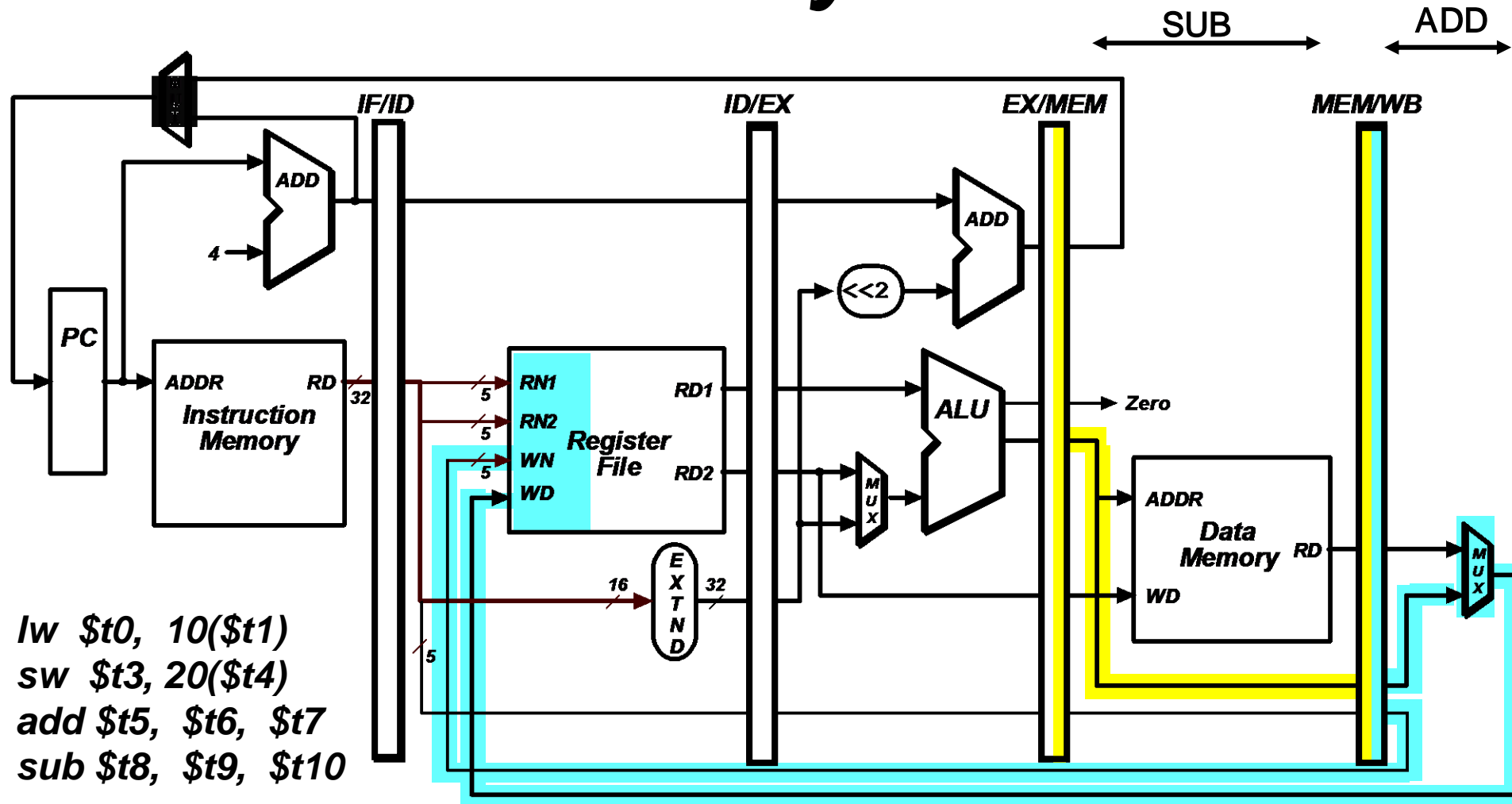Single-Clock-Cycle Diagram: Clock Cycle 7



```
lw $t0, 10($t1)
sw $t3, 20($t4)
add $t5, $t6, $t7
sub $t8, $t9, $t10
```

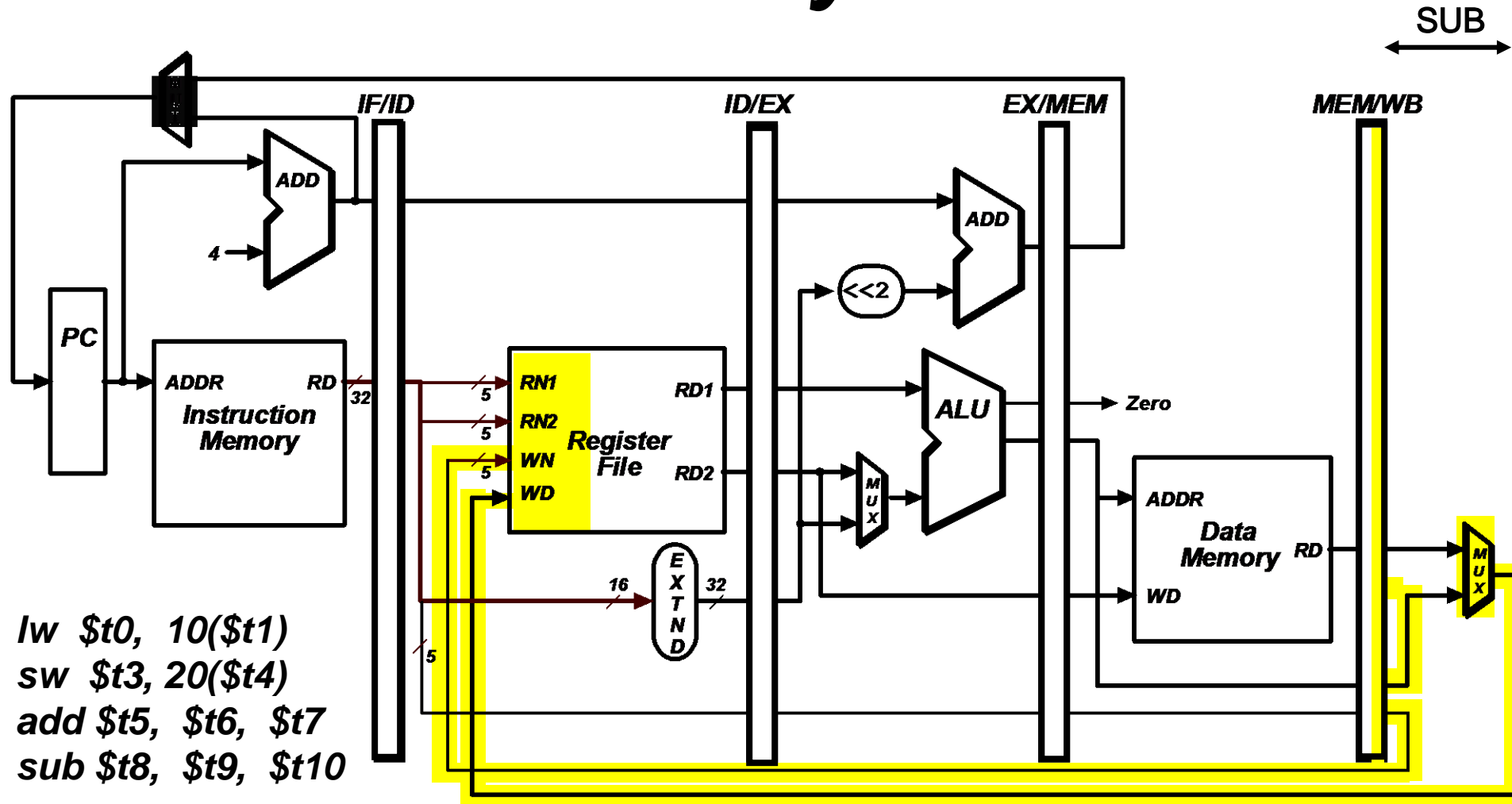Single-Clock-Cycle Diagram: Clock Cycle 8




Represent Pipelines Graphically

- ***Multiple instruction execution over multiple clock cycles***
 - ***Instructions are listed in execution order from top to bottom***
 - ***Clock cycles move from left to right***
 - ***Show the use of resources at each stage and each cycle***

Represent Pipelines Graphically

- 1. Lw \$t6, 8(\$s5)***
- 2. Add \$s1, \$s2, \$s3***
- 3. Ori \$s4, \$t3, 7***
- 4. Sub \$t5, \$s2, \$t3***
- 5. Sw \$s2, 10(\$t3)***

Graphically Representing Pipelines

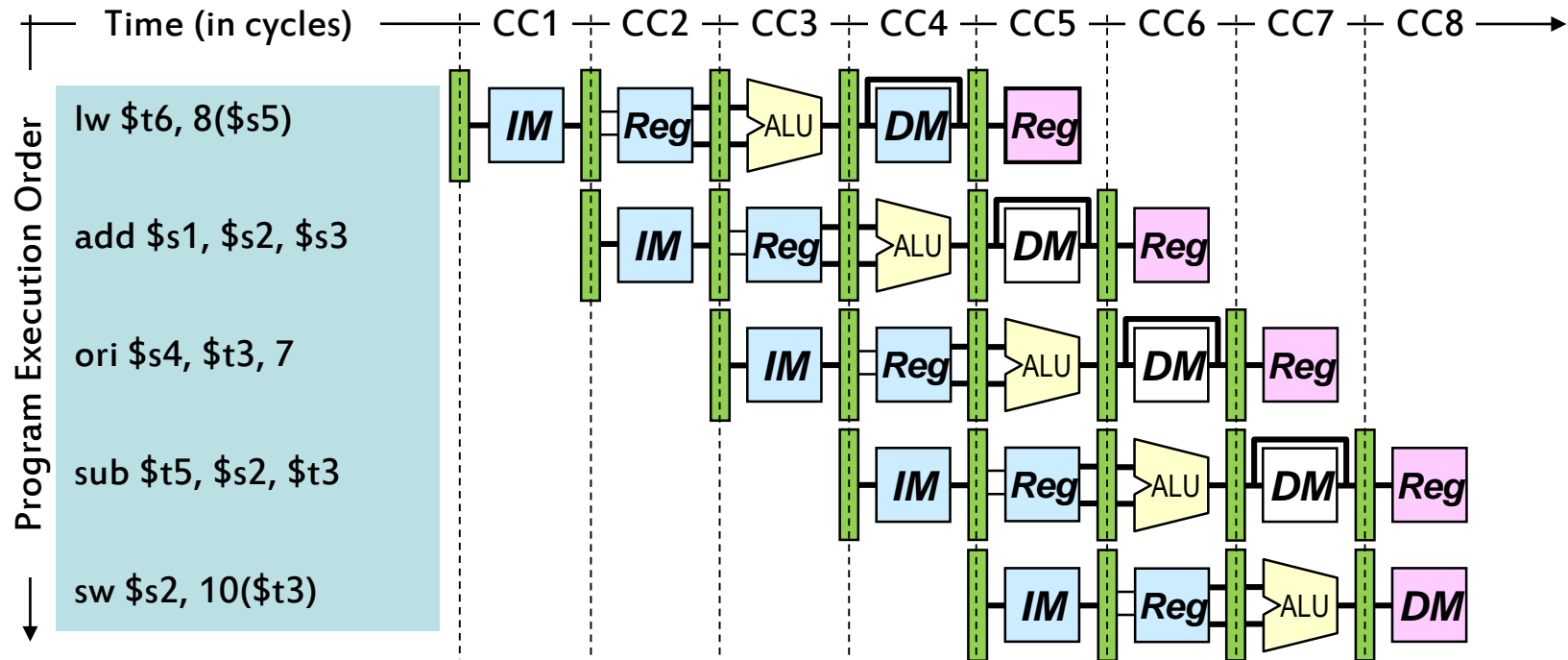


Instruction-Time Diagram

- ***Instruction-Time Diagram shows:***
 - ***Which instruction occupying what stage at each clock cycle***
 - ***Instruction flow is pipelined over the 5 stages***
1. ***Lw \$t7, 8(\$s3)***
 2. ***Lw \$t6, 8(\$st)***
 3. ***Ori \$t4, \$s3, 7***
 4. ***Sub \$s5, \$s2, \$t3***
 5. ***Sw \$s2, 10(\$s3)***

Instruction-Time Diagram

Up to five instructions can be in the pipeline during the same cycle
Instruction Level Parallelism (ILP)

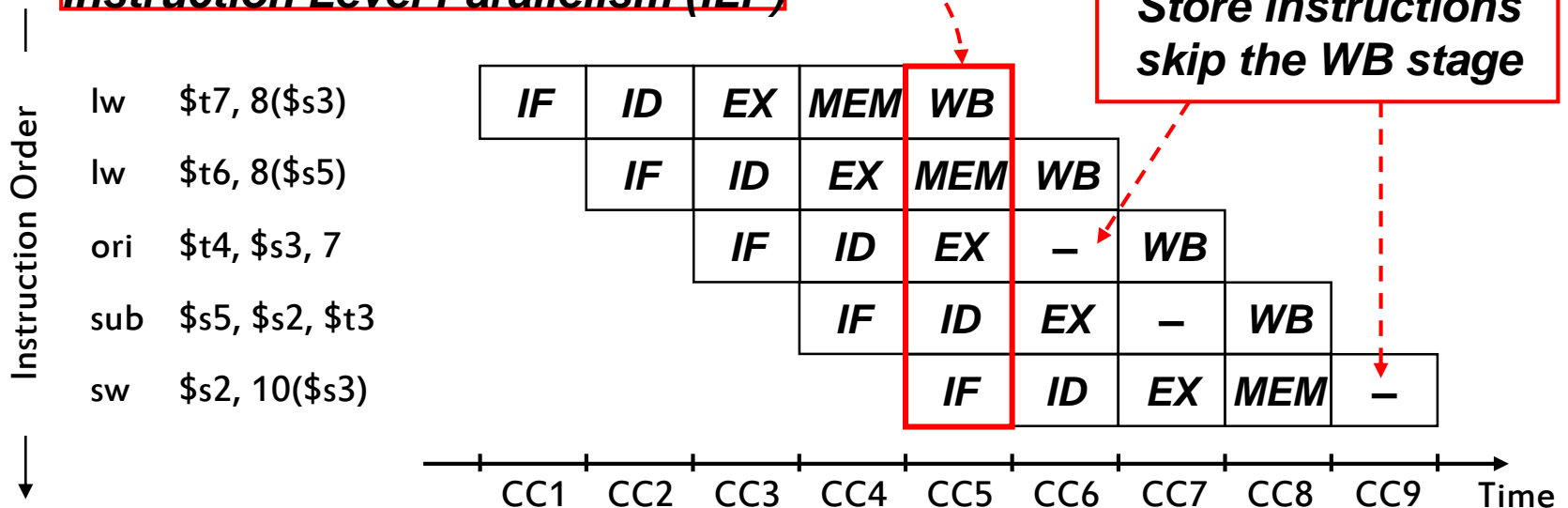
ALU instructions skip the MEM stage.
Store instructions skip the WB stage



How many Clock Cycles?

5 Instructions + (5 step pipelining - 1) = 9 Clock cycles

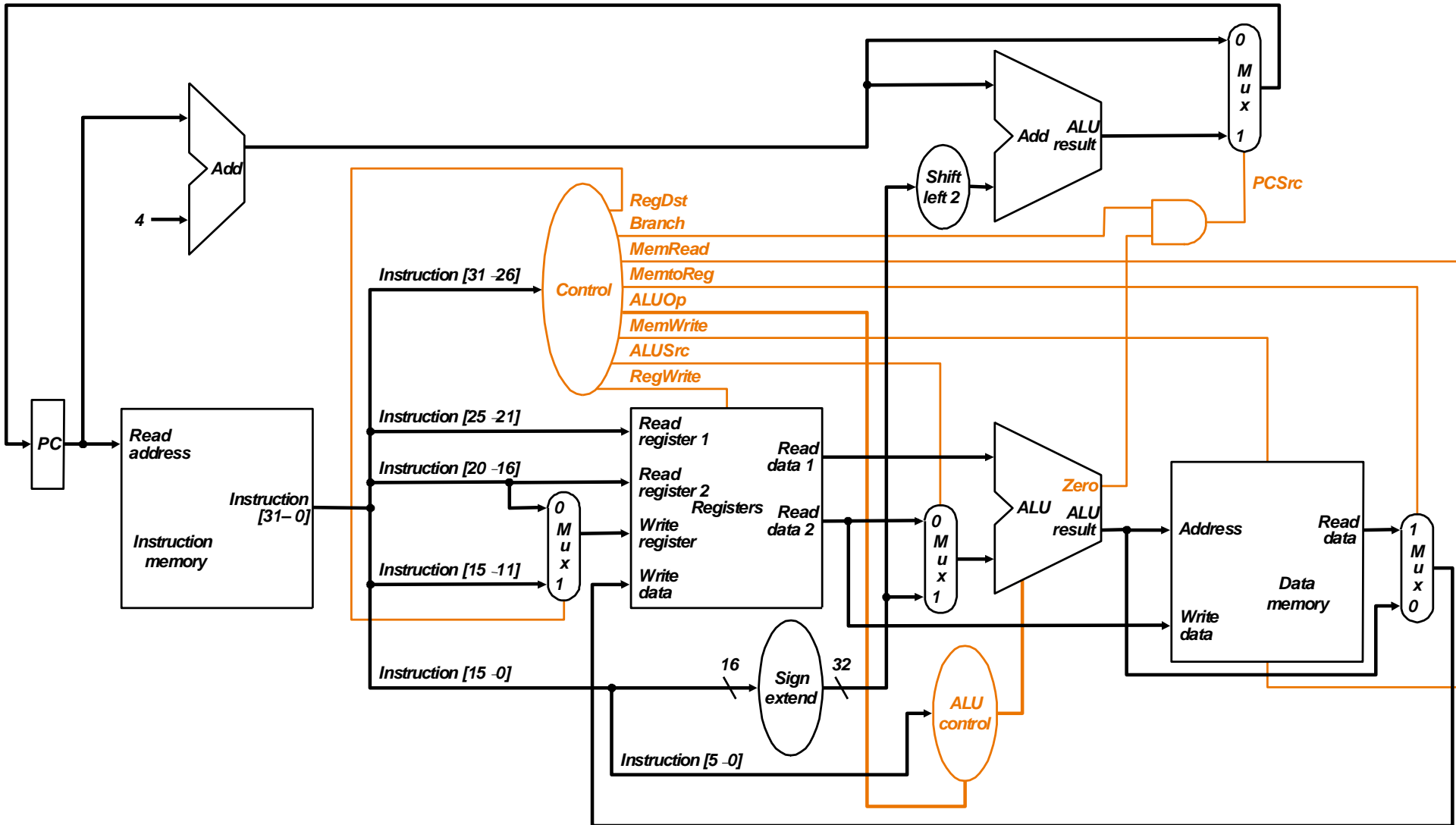Recall Single-Cycle Control – the Datapath



Recall Single-Cycle – ALU Control

<i>Instruction</i>	<i>AluOp</i>	<i>Instruction</i>	<i>Func Field</i>	<i>Desired</i>	<i>ALU control</i>
<i>opcode</i>		<i>operation</i>		<i>ALU action</i>	<i>input</i>
LW	00	load word	xxxxxx	add	010
SW	00	store word	xxxxxx	add	010
Branch eq	01	branch eq	xxxxxx	subtract	110
R-type	10	add	100000	add	010
R-type	10	subtract	100010	subtract	110
R-type	10	AND	100100	and	000
R-type	10	OR	100101	or	001
R-type	10	set on less	101010	set on less	111

<i>ALUOp</i>		<i>Func field</i>						<i>Operation</i>
<i>ALUOp1</i>	<i>ALUOp0</i>	<i>F5</i>	<i>F4</i>	<i>F3</i>	<i>F2</i>	<i>F1</i>	<i>F0</i>	
0	0	X	X	X	X	X	X	010
0	1	X	X	X	X	X	X	110
1	X	X	X	0	0	0	0	010
1	X	X	X	0	0	1	0	110
1	X	X	X	0	1	0	0	000
1	X	X	X	0	1	0	1	001
1	X	X	X	1	0	1	0	111

Truth table for ALU control bits

Recall Single-Cycle – Control Signals

Effect of control bits

Signal Name	Effect when deasserted	Effect when asserted
<i>RegDst</i>	<i>The register destination number for the Write register comes from the rt field (bits 20-16)</i>	<i>The register destination number for the Write register comes from the rd field (bits 15-11)</i>
<i>RegWrite</i>	<i>None</i>	<i>The register on the Write register input is written with the value on the Write data input</i>
<i>ALUSrc</i>	<i>The second ALU operand comes from the second register file output (Read data 2)</i>	<i>The second ALU operand is the sign-extended, lower 16 bits of the instruction</i>
<i>PCSrc</i>	<i>The PC is replaced by the output of the adder that computes the value of PC + 4</i>	<i>The PC is replaced by the output of the adder that computes the branch target</i>
<i>MemRead</i>	<i>None</i>	<i>Data memory contents designated by the address input are put on the first Read data output</i>
<i>MemWrite</i>	<i>None</i>	<i>Data memory contents designated by the address input are replaced by the value of the Write data input</i>
<i>MemtoReg</i>	<i>The value fed to the register Write data input comes from ALU</i>	<i>The value fed to the register Write data input comes from the data memory</i>


Determining control bits

	<i>Instruction</i>	<i>RegDst</i>	<i>ALUSrc</i>	<i>Memto-Reg</i>	<i>Reg Write</i>	<i>Mem Read</i>	<i>Mem Write</i>	<i>Branch</i>	<i>ALUOp1</i>	<i>ALUOp0</i>
<i>R-format</i>		<i>1</i>	<i>0</i>	<i>0</i>	<i>1</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>1</i>	<i>0</i>
<i>lw</i>		<i>0</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>1</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>sw</i>		<i>X</i>	<i>1</i>	<i>X</i>	<i>0</i>	<i>0</i>	<i>1</i>	<i>0</i>	<i>0</i>	<i>0</i>
<i>beq</i>		<i>X</i>	<i>0</i>	<i>X</i>	<i>0</i>	<i>0</i>	<i>0</i>	<i>1</i>	<i>0</i>	<i>1</i>

Pipeline Control


- *Initial design – motivated by single-cycle datapath control– use the same control signals*
 - *Modified Signals:*
 - *No separate write signal for the PC as it is written every cycle*
 - *No separate write signals for the pipeline registers as they are written every cycle*
 - *No separate read signal for instruction memory as it is read every clock cycle*
 - *No separate read signal for register file as it is read every clock cycle*
 - *Need to set control signals during each pipeline stage*
 - *Since control signals are associated with components active during a single pipeline stage, can group control lines into five groups according to pipeline stage*
- Will be modified by hazard detection unit!!

Pipelined Datapath with Control I

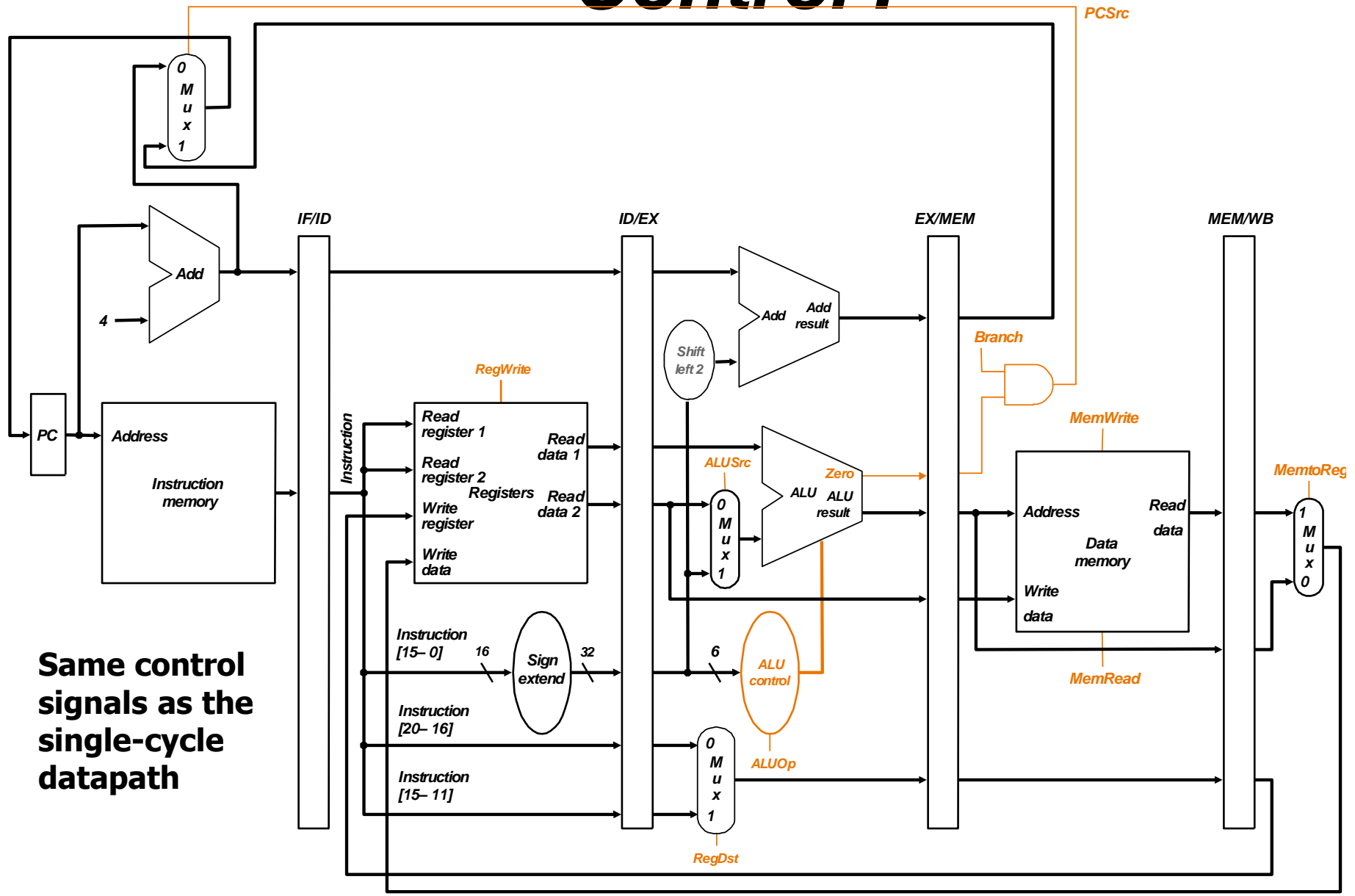

Pipeline Control Signals

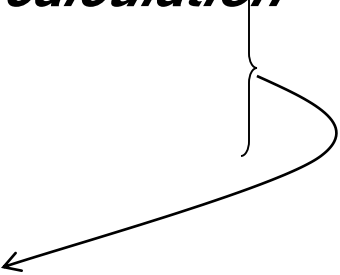
- **There are five stages in the pipeline**
 - ***instruction fetch / PC increment***
 - ***instruction decode / register fetch***
 - ***execution / address calculation***
 - ***memory access***
 - ***write back***
- Nothing to control as instruction memory read and PC write are always enabled



	Execution/Address Calculation stage control lines				Memory access stage control lines			stage control lines	
	Reg Dst	ALU Op1	ALU Op0	ALU Src	Branch	Mem Read	Mem Write	Reg write	Mem to Reg
R-format	1	1	0	0	0	0	0	1	0
lw	0	0	0	1	0	1	0	1	1
sw	X	0	0	1	0	0	1	0	X
beq	X	0	1	0	1	0	0	0	X

Pipeline Control Implementation

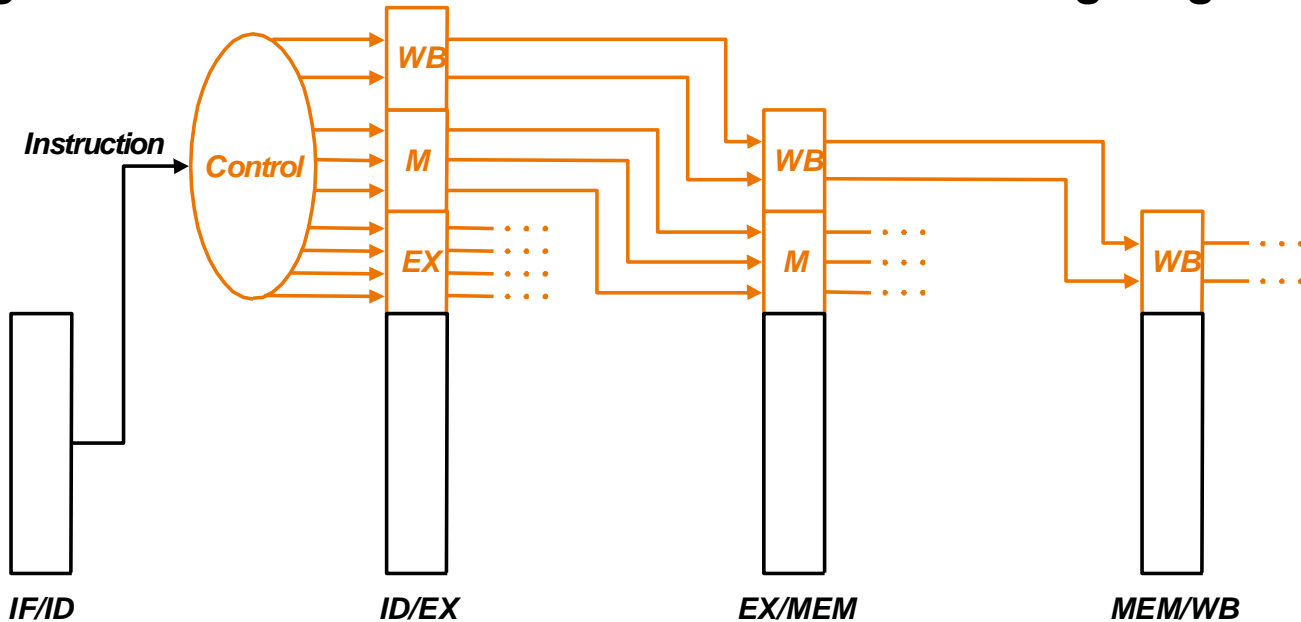- ***Pass control signals along just like the data– extend each pipeline register to hold needed control bits for succeeding stages***



- ***Note: The 6-bit `funct` field of the instruction required in the EX stage to generate ALU control can be retrieved as the 6 least significant bits of the immediate field which is sign-extended and passed from the IF/ID register to the ID/EX register***

Pipeline Hazards


- ***Situations that would cause incorrect execution***
- ***Data flow problems that arise as a result of pipelining***
 - ***Limits the amount of parallelism, sometimes induces “penalties” that prevent one instruction per clock cycle***
- ***Types***
 - ***Structural hazards***
 - ***Data hazards***
 - ***Control hazards***

Hazards

Draw pipeline diagram, and check hazard is exist or not?


- ***lw \$1, 100(\$0)***
- ***lw \$2, 200(\$0)***
- ***lw \$3, 300(\$0)***
- ***lw \$4, 400(\$0)***

Hazard

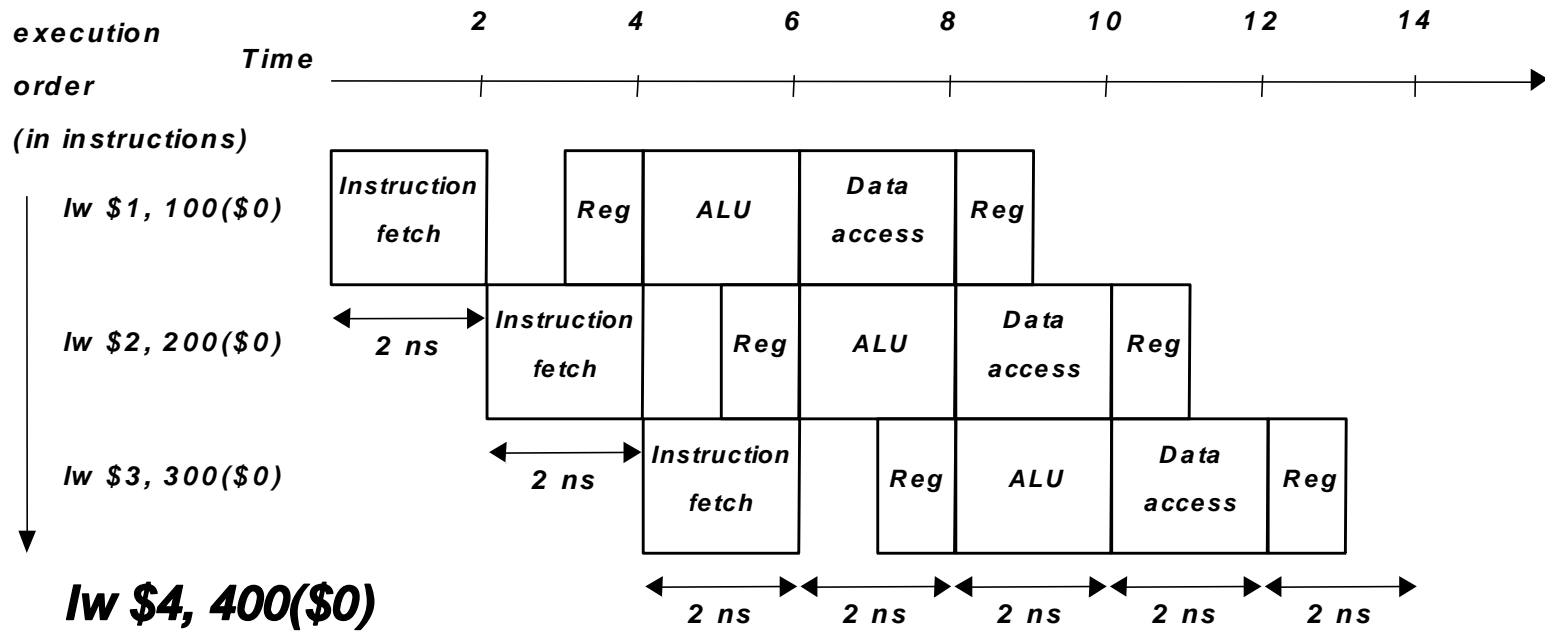

Structural Hazards

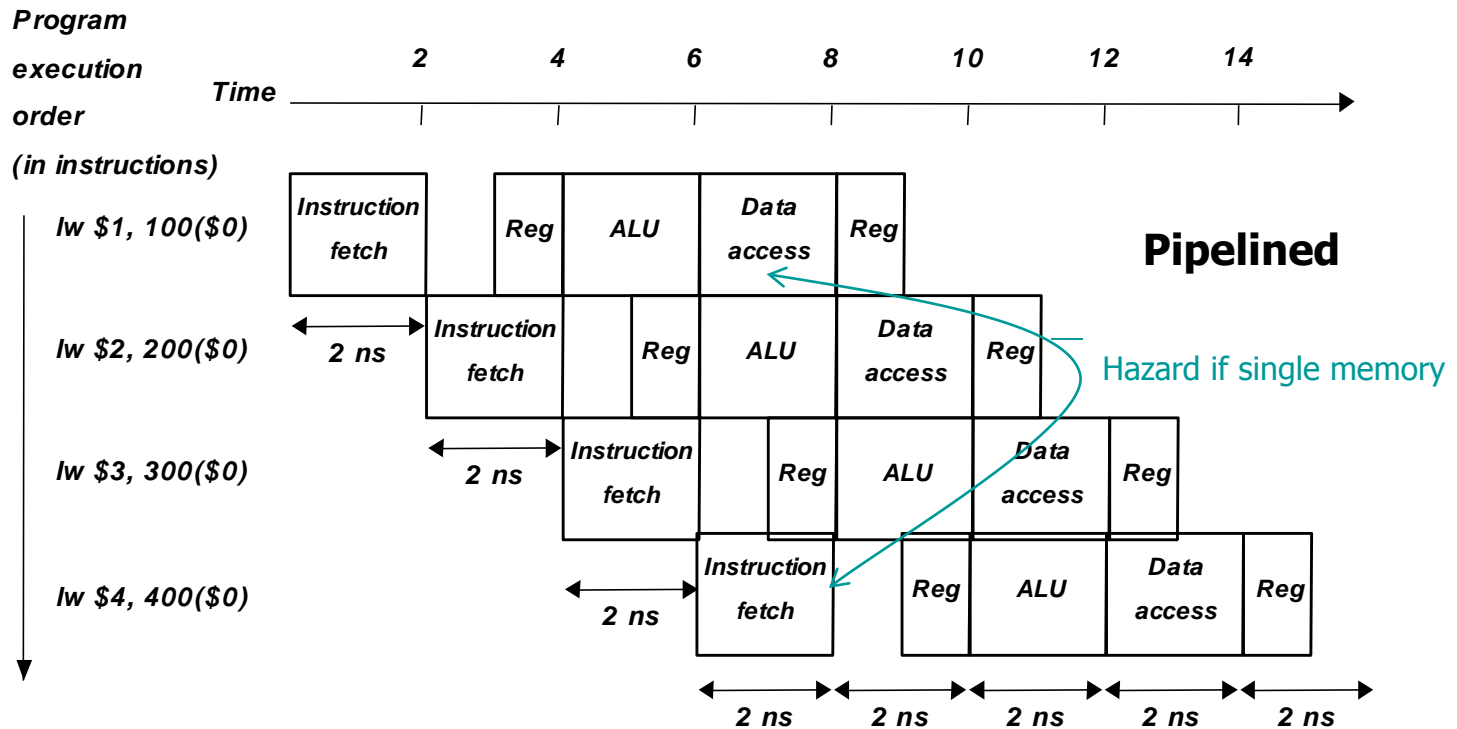- ***E.g., suppose *single – not separate* – instruction and data memory in pipeline below with *one read port****
 - ***then a structural hazard between first and fourth \perp_w instructions***



Structural Hazards

- ***Inadequate hardware to simultaneously support all instructions in the pipeline in the same clock cycle***
- ***Attempt to use the same hardware resource by two different instructions during the same cycle***
- ***Structural hazards can be overcome by adding additional hardware***
- ***lw \$1, 100(\$0)***
- ***lw \$2, 200(\$0)***
- ***lw \$3, 300(\$0)***
- ***lw \$4, 400(\$0)***

Resolving Structural Hazards

- ***Serious Hazard:***
 - *Hazard cannot be ignored*
 - *Easy to avoid*
- ***Solution: Add more hardware resources (more costly)***
 - *Add more additional hardware to eliminate the structural hazard*
 - *Like, two separate memories*

Data Hazards

- ***Dependency between instructions causes a data hazard***
- ***Instruction needs data from the result of a previous instruction still executing in pipeline***
- ***The dependent instructions are close to each other***
 - ***Pipelined execution might change the order of operand access***

Data Hazards Type

- ***RAR (Read After Read) hazard***
 - *Occurs when two instructions both read from the same register*
 - ***Example:***
 - ADD \$s1, \$s2, \$s3***
 - SUB \$s4, \$s5, \$s3***
 - *Both instructions reading \$s3, creating a RAR hazard*
 - *Don't cause a problem for the processor because reading a register doesn't change the register's value*

Data Hazards Type

- **RAW (Read After Write) hazard**
 - Occurs when, one instruction reads a location after an earlier instruction writes new data to it
 - instruction *j* tries to read a source before instruction *i* writes it, so *j* incorrectly gets the old value
 - **Example:**
 - i*: Add \$s3, \$s1, \$s2
 - j*: Add \$s5, \$s3, \$s4
 - Result is the instruction reading stale data
 - Detected when Output_n register (\$s3) and Input_{n+1} registers (\$s3, \$s4) contain at least one common register
 - Need to resolve

Data Hazards Type

- ***WAR (Write After Read) hazard***
 - *Hazards occur when the output register of an instruction is used for write after read by a previous instruction*
 - *Instruction j tries to write a destination before it is read by instruction i, so i incorrectly gets the new value*
 - ***Example:***
 - i: Add \$s3, \$s1, \$s2*
 - j: Add \$s1, \$s3, \$s4*
 - *Detected when $Input_n$ register and $Output_{n+1}$ register contain at least one common operand*
 - ***Such hazards are rare***

Data Hazards Type

- ***WAW (Write After Write) hazard***
 - *Hazard occur when the output register of an instruction is used for write after written by a previous instruction*
 - ***Example:***
ADD \$s1, \$s2, \$s3
SUB \$s1, \$s5, \$s6 //Subtract writes the same register as the addition
 - *If a processor executes instructions in the order that they appear in the program and uses the same pipeline for all instructions, WAR and WAW hazards do not cause the delays because of the way instructions flow through the pipeline*

Hazard

Example: Draw pipeline diagram and show the hazards if any.

sub \$s2, \$t1, \$t3

add \$s4, \$s2, \$t5

or \$s6, \$t3, \$s2

and \$s7, \$t4, \$s2

sw \$t8, 10(\$s2)

RAW Data Hazard Solutions

Example:

sub \$s2, \$t1, \$t3

add \$s4, \$s2, \$t5

or \$s6, \$t3, \$s2

and \$s7, \$t4, \$s2

sw \$t8, 10(\$s2)

RAW Data Hazard Solutions

Example:

sub **\$s2**, \$t1, \$t3


add \$s4, **\$s2**, \$t5

or \$s6, \$t3, **\$s2**

and \$s7, \$t4, **\$s2**


sw \$t8, 10(**\$s2**)

Example of a RAW Data Hazard

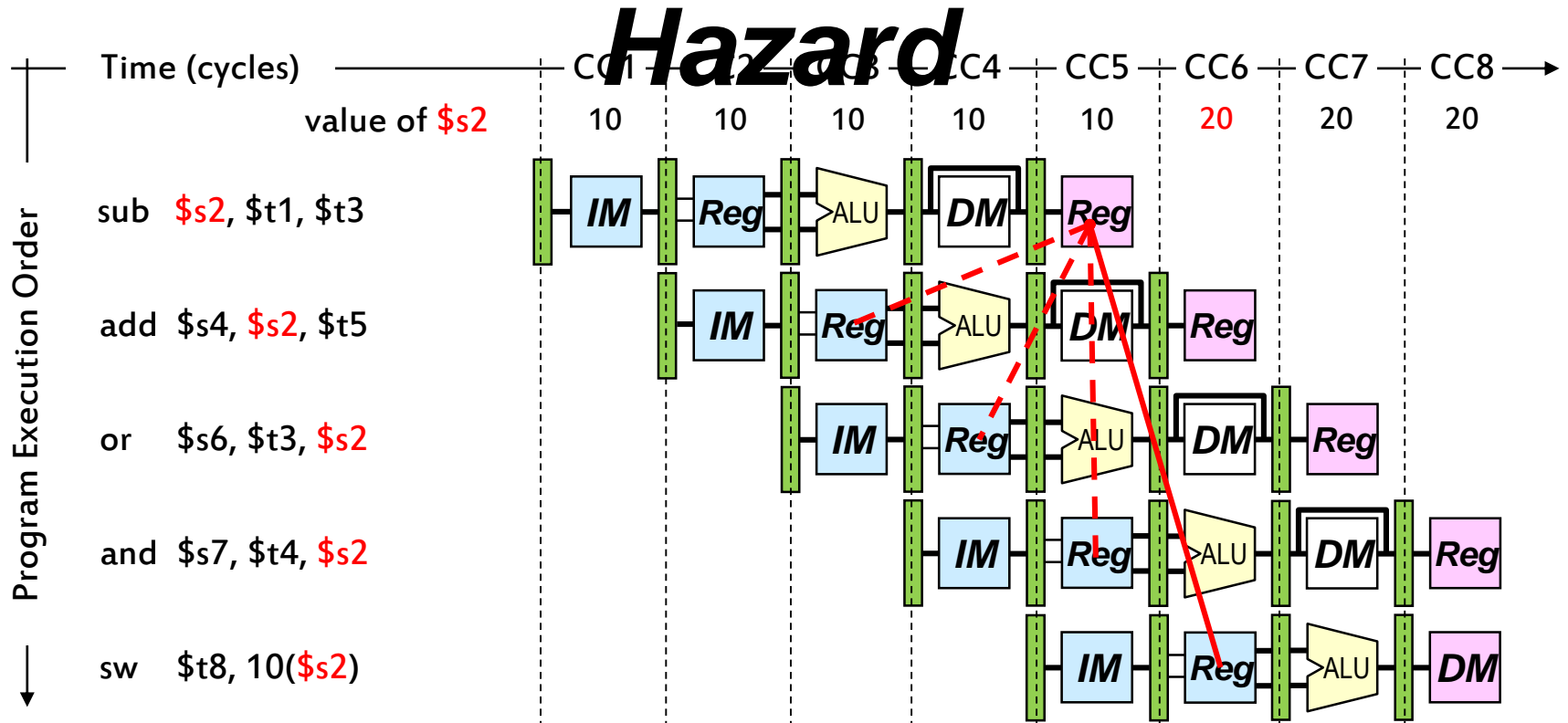

- **Result of **sub** is needed by **add**, **or**, **and**, & **sw** instructions**
- **Instructions **add** & **or** will read **old value** of **\$s2** from reg file**
- **During CC5, **\$s2** is written at end of cycle, **old value** is read**
 - **But, can be eliminated by considering in first half write to register and in second half read from register**


Solution 1: Stalling the Pipeline

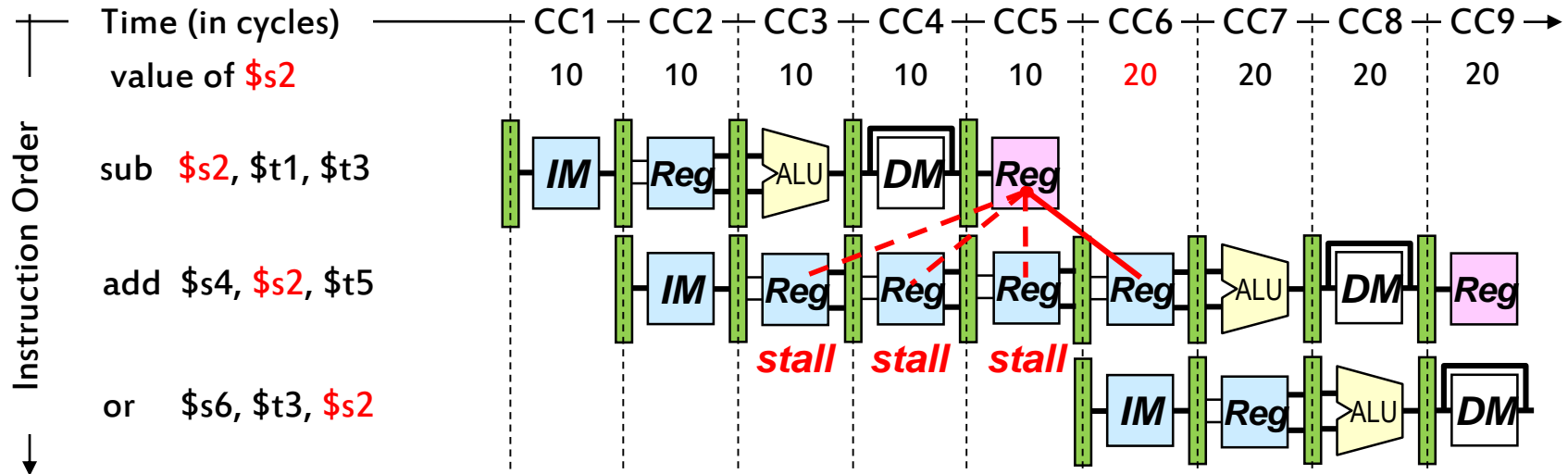

- **Three stall cycles during CC3 thru CC5 (wasting 3 cycles)**
 - Stall cycles delay execution of add & fetching of or instruction
- **The add instruction cannot read \$s2 until beginning of CC6**
 - The add instruction remains in the Instruction register until CC6
 - The PC register is not modified until beginning of CC6

Solution 2: Forwarding ALU Result

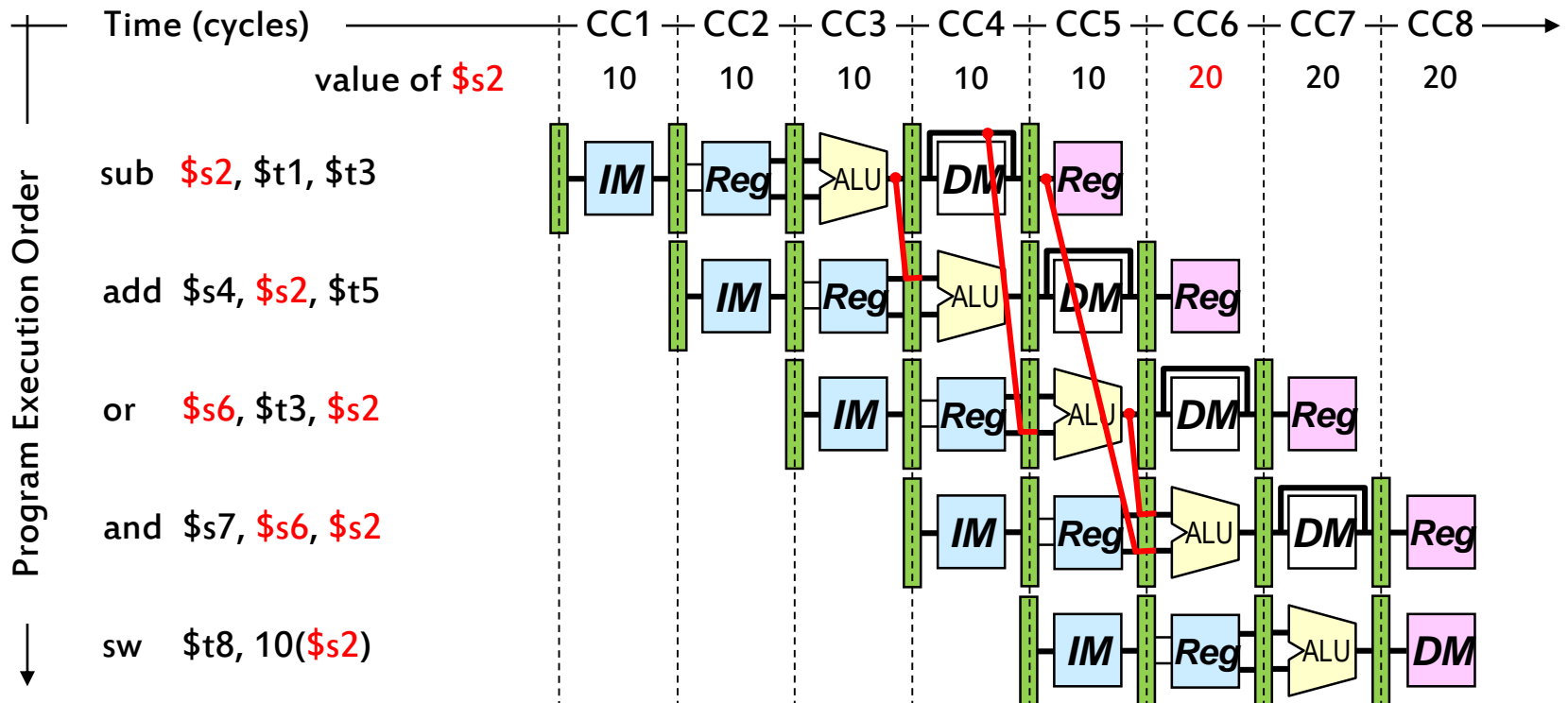- **The ALU result is forwarded (fed back) to the ALU input**
 - **No bubbles are inserted into the pipeline and no cycles are wasted**
- **ALU result is forwarded from ALU, MEM, and WB stages**



RAW Data Hazard Solutions

- ***For the following code, detect the hazard, if any.***


lw \$s0, 20(\$t1)

sub \$t2, \$s0,\$t3

- ***Is forwarding useful?***
- ***If an R-type instruction following a load uses the result of the load – called *load-use data hazard****


RAW Data Hazard Solutions

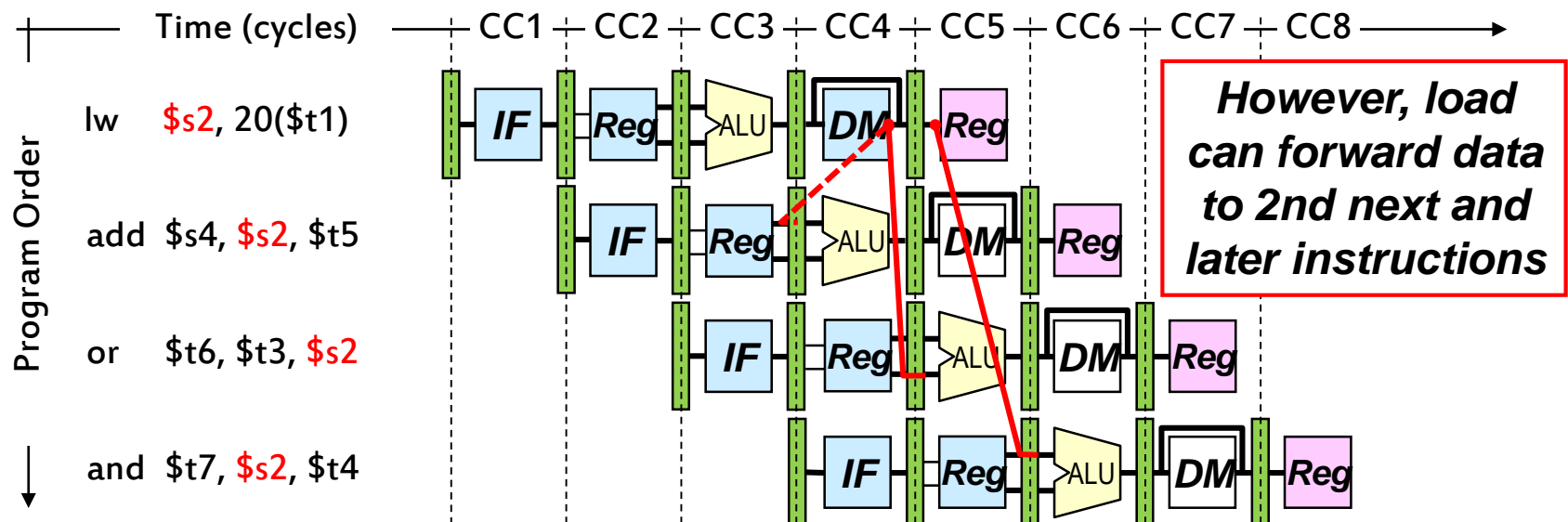- **Unfortunately, not all data hazards can be forwarded**
 - **Load has a delay that cannot be eliminated by forwarding**
- **In the example shown below ...**
 - **The LW instruction does not read data until end of CC4**
 - **Cannot forward data to ADD at end of CC3 - NOT possible**



Stall the Pipeline for one Cycle

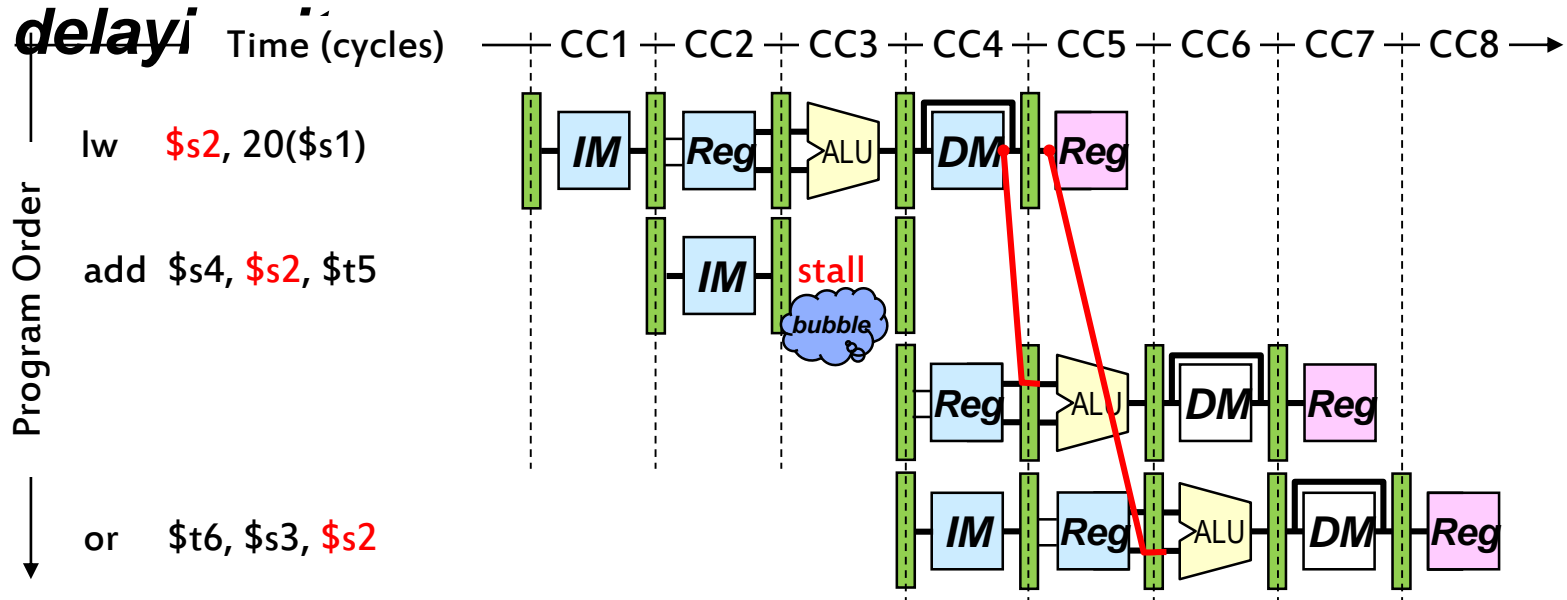- *ADD instruction depends on LW → stall at CC3*
 - *Allow Load instruction in ALU stage to proceed*
 - *Freeze PC and Instruction registers (NO instruction is fetched)*
 - *Introduce a bubble into the ALU stage (bubble is a NO-OP)*
- *Load can forward data to next instruction after delay*



Showing Stall Cycles

- *Stall cycles can be shown on instruction-time diagram*
- *Hazard is detected in the Decode stage*
- *Stall indicates that instruction is delayed*
- *Instruction fetching is also delayed after a stall*
- **Example:**

Data forwarding is to be shown using *green*


arrows

lw **\$s1**, (\$t5)

lw **\$s2**, 8(**\$s1**)


add **\$v0**, **\$s2**, \$t3

sub **\$v1**, **\$s2**, **\$v0**

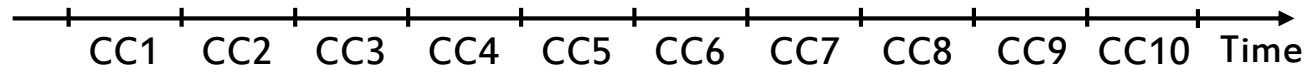

Showing Stall Cycles

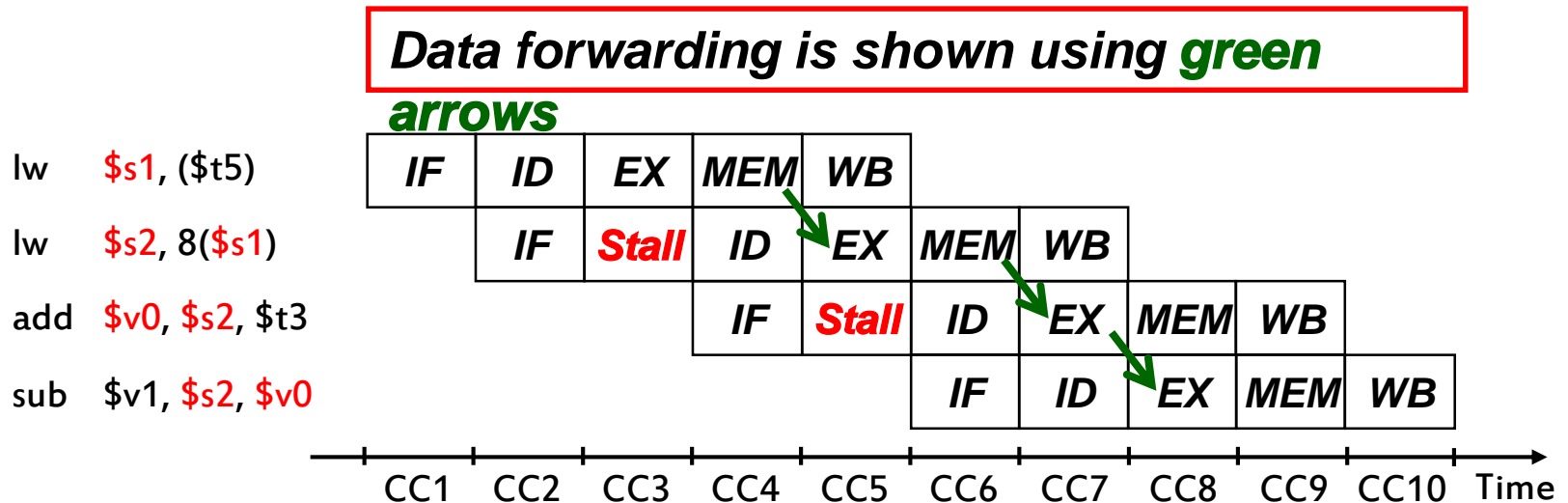- *Stall cycles can be shown on instruction-time diagram*
- *Hazard is detected in the Decode stage*
- *Stall indicates that instruction is delayed*
- *Instruction fetching is also delayed after a stall*
- **Example:**



RAW Data Hazard Solutions

- ***Software Solution***
 - ***Reordering Code to Avoid Pipeline Stall***
- ***Example:***

```
lw  $t0, 0($t1)
```

```
lw  $t2, 4($t1)
```


```
sw  $t2, 0($t1)
```

```
sw  $t0, 4($t1)
```

RAW Data Hazard Solutions

- **Example:**


```
lw $t0, 0($t1)
lw $t2, 4($t1)
sw $t2, 0($t1)
sw $t0, 4($t1)
```



A teal curved arrow points from the **\$t2** in the third instruction (`sw $t2, 0($t1)`) back to the `$t2` in the second instruction (`lw $t2, 4($t1)`). The text "Data hazard" is written in teal next to the arrow.

- **Reordered code:**

```
lw $t0, 0($t1)
lw $t2, 4($t1)
sw $t0, 4($t1)
sw $t2, 0($t1)
```



A teal curved arrow points from the **\$t2** in the fourth instruction (`sw $t2, 0($t1)`) back to the `$t2` in the second instruction (`lw $t2, 4($t1)`). The text "Interchanged" is written in teal next to the arrow.


Example

- ***Draw the pipelining execution for the following code and detect and resolve the hazard, if any.***

```
sub  $2,  $1,  $3
and  $12, $2,  $5
or   $13, $6,  $2
add  $14, $2,  $2
sw   $15, 100($2)
```

<p>\$2 = 10 before sub \$2 = -20 after sub</p>
--

Data Hazards and Forwarding

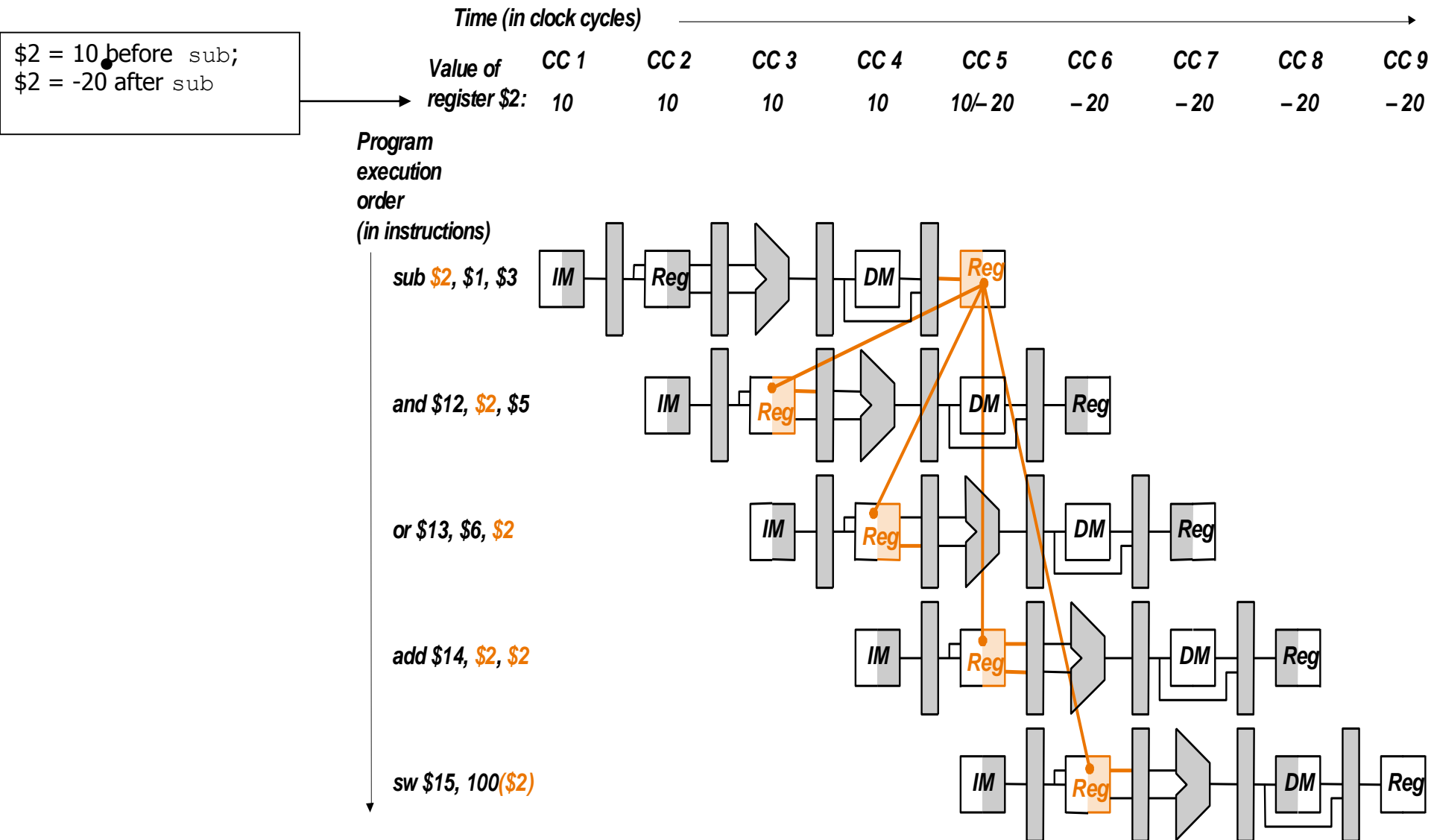

Example: Software Solution

- *By rearranging instructions to insert independent instructions between instructions that would otherwise have a data hazard between them,*
- *Or, if such rearrangement is not possible, **insert** nops*

sub \$2, \$1, \$3	sub \$2, \$1, \$3	sub \$2, \$1, \$3
and \$12, \$2, \$5	lw \$10, 40(\$3)	nop
or \$13, \$6, \$2	slt \$5, \$6, \$7	nop
add \$14, \$2, \$2	and \$12, \$2, \$5	or and \$12, \$2, \$5
sw \$15, 100(\$2)	or \$13, \$6, \$2	or \$13, \$6, \$2
	add \$14, \$2, \$2	add \$14, \$2, \$2
	sw \$15, 100(\$2)	sw \$15, 100(\$2)

- ***Such compiler solutions may not always be possible, and nops slow the machine down***


MIPS: nop = "no operation" = 00...0 (32bits) = sll \$0, \$0, 0

RAW Hazard-Hardware Solution


- ***Forwarding***
- ***Idea: Use intermediate data, do not wait for result to be finally written to the destination register.***
- ***Two steps:***
 1. ***Detect data hazard***
 2. ***Forward intermediate data to resolve hazard***

Pipelined Datapath with Control II (as before)
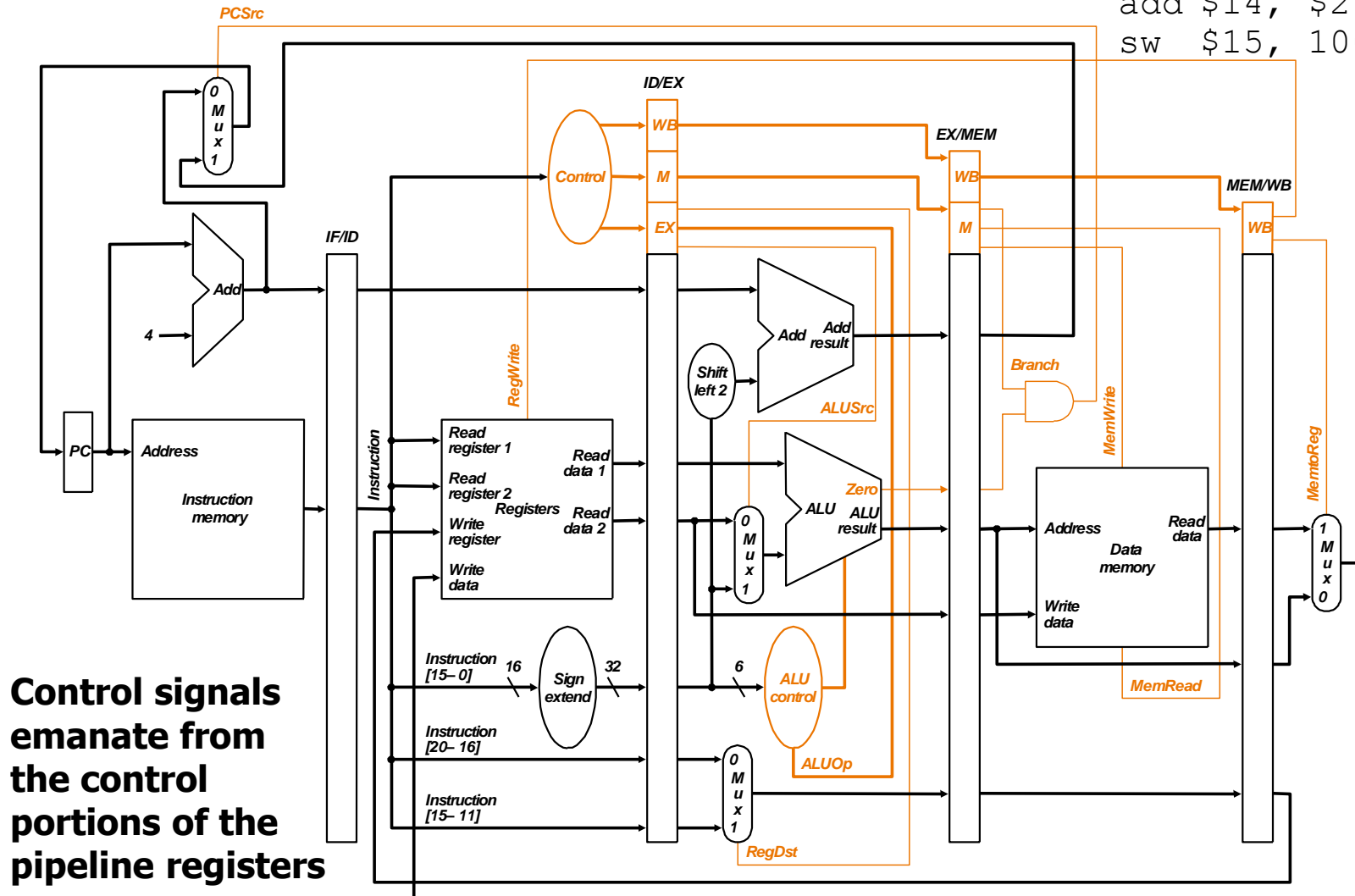
```
sub $2, $1, $3
and $12, $2, $5
or $13, $6, $2
add $14, $2, $2
sw $15, 100($2)
```



Data Hazards and Forwarding

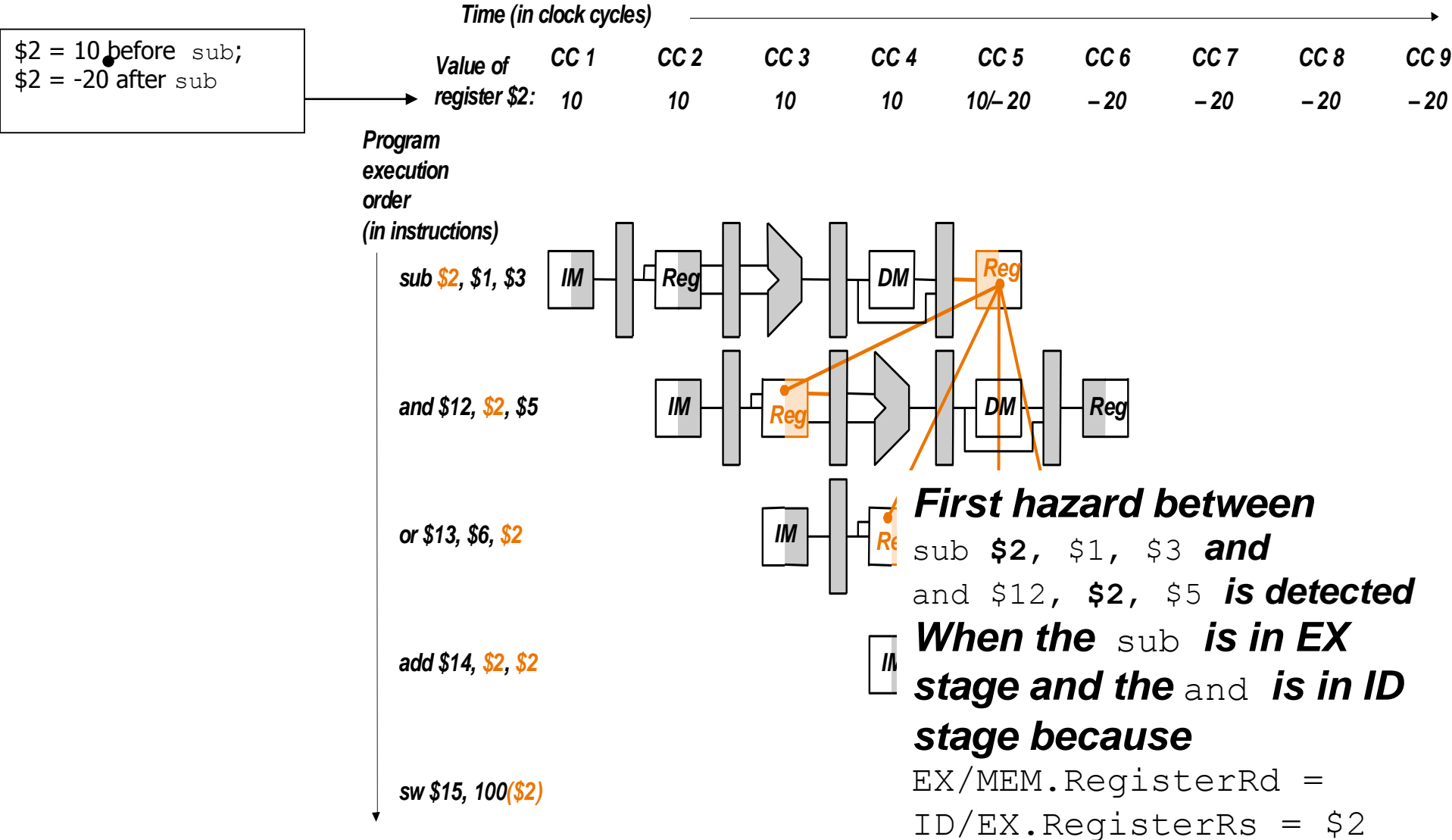

Hazard Detection

- **Hazard conditions:**

1a. $EX/MEM.RegisterRd = ID/EX.RegisterRs$

1b. $EX/MEM.RegisterRd = ID/EX.RegisterRt$

2a. $MEM/WB.RegisterRd = ID/EX.RegisterRs$

2b. $MEM/WB.RegisterRd = ID/EX.RegisterRt$

```
sub $2, $1, $3
and $12, $2, $5
or $13, $6, $2
add $14, $2, $2
sw $15, 100($2)
```


– **Eg., in the example, first hazard between**

- **sub \$2, \$1, \$3 and**
- **and \$12, \$2, \$5 is detected**

– **When the sub is in EX stage and the and is in ID stage because**

- **$EX/MEM.RegisterRd = ID/EX.RegisterRs = \2 (1a)**

Hazard Detection

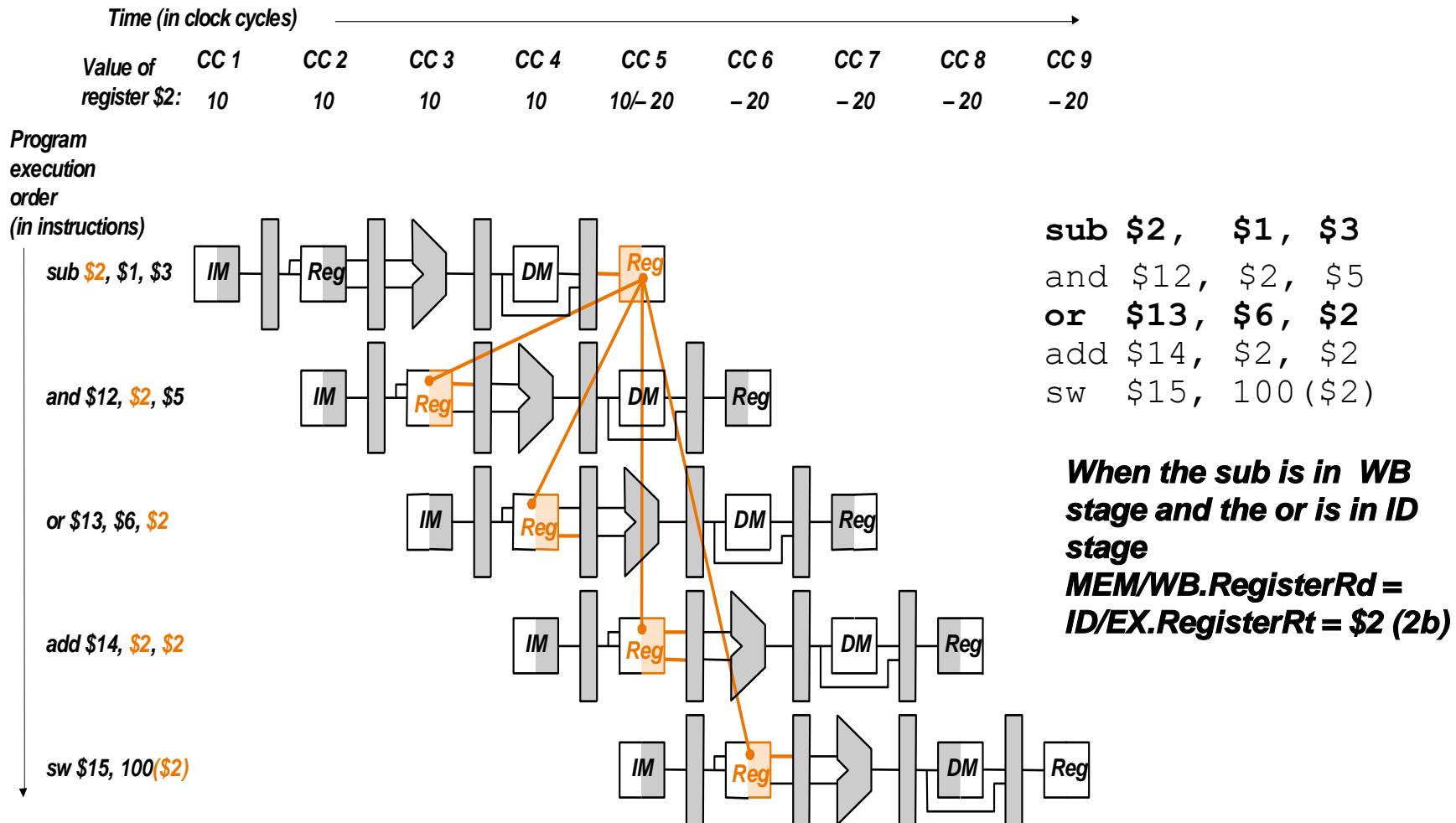

Hazard Detection

- ***Whether to forward also depends on:***
 - ***if the later instruction is going to write a register***
 - ***if not, no need to forward***
 - ***if the destination register of the later instruction is \$0***
 - ***no need to forward value (\$0 is always 0 and never overwritten)***

Data Forwarding

- Plan:

- Allow inputs to the ALU not just from ID/EX, but also later pipeline registers, and
- Use multiplexors and control signals to choose appropriate inputs to ALU


Time (in clock cycles) →

	CC 1	CC 2	CC 3	CC 4	CC 5	CC 6	CC 7	CC 8	CC 9
Value of register \$2 :	10	10	10	10	10/- 20	- 20	- 20	- 20	- 20
Value of EX/MEM :	X	X	X	- 20	X	X	X	X	X
Value of MEM/WB :	X	X	X	X	- 20	X	X	X	X

```


sub $2, $1, $3
and $12, $2, $5
or $13, $6, $2
add $14, $2, $2
sw $15, 100($2)
    
```

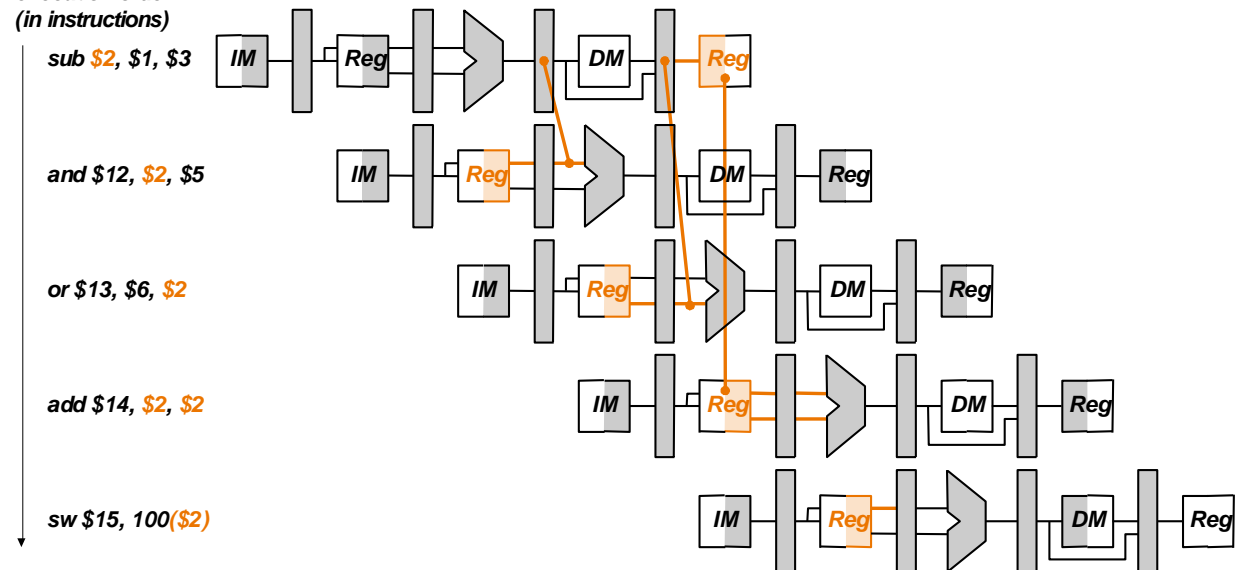Program
execution order
(in instructions)



Dependencies between pipelines move forward in time


Datapath Before Forwarding Hardware

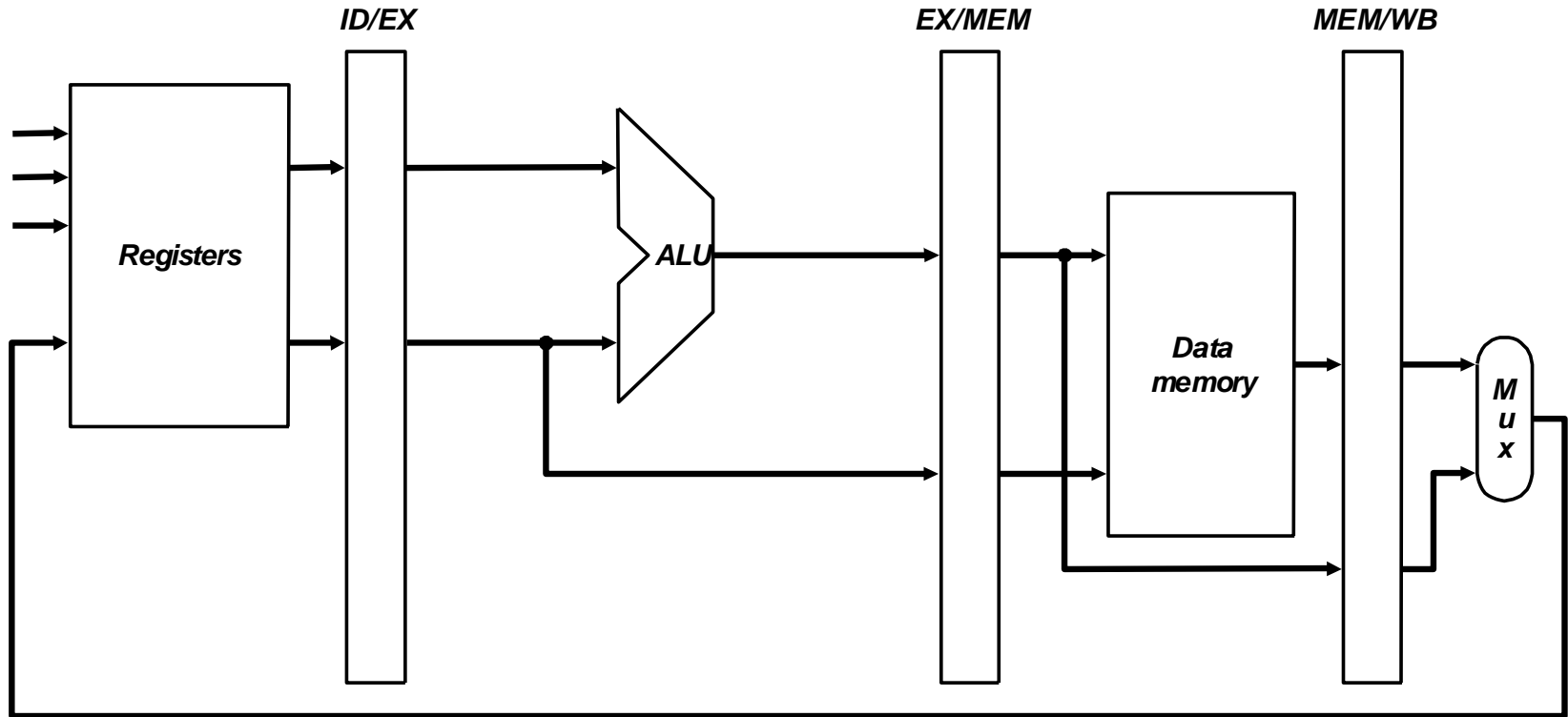

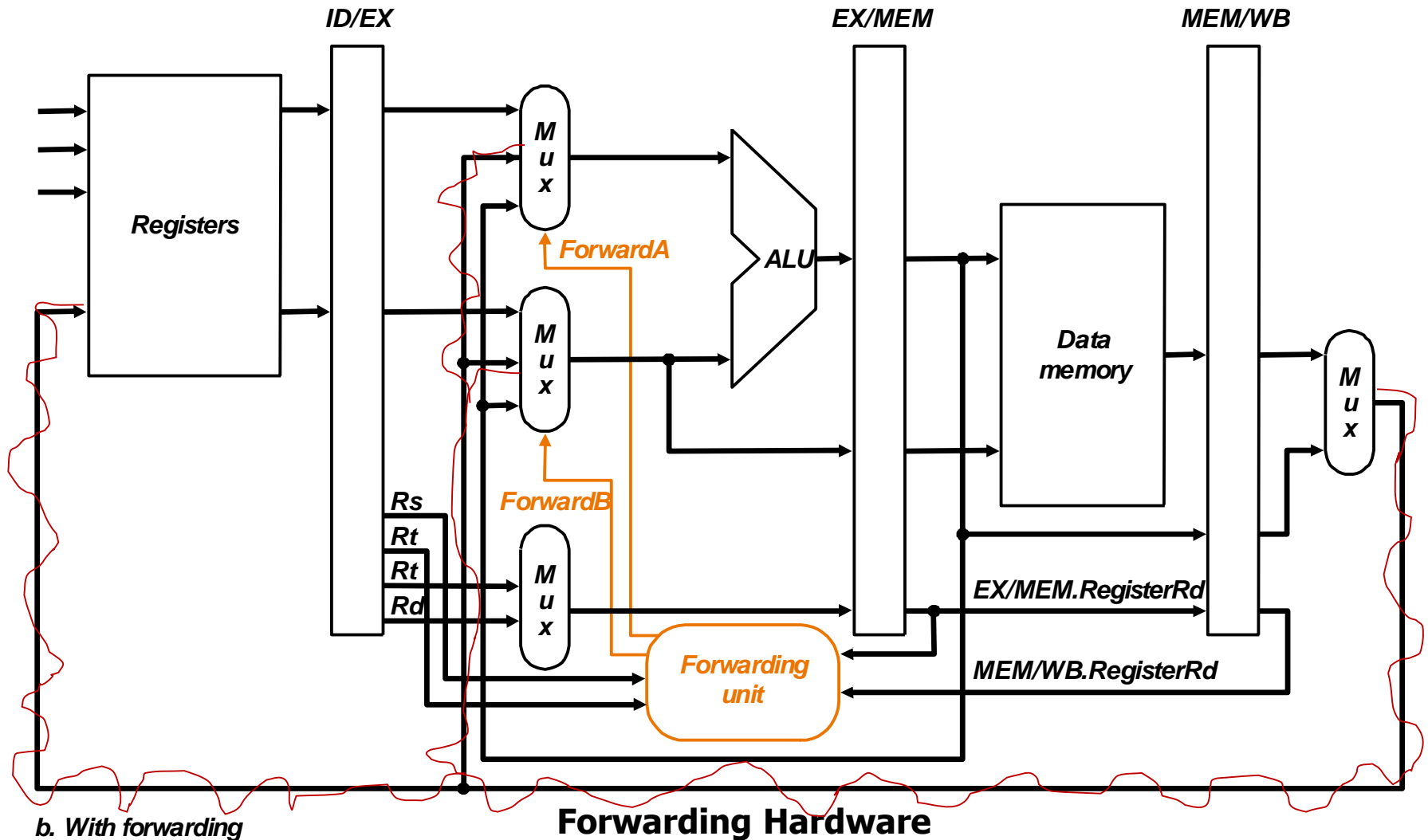a. No forwarding


Datapath after adding forwarding hardware

Datapath after adding *Forwarding Hardware*



Forwarding Hardware: Multiplexor Control

Mux control	Source	Explanation
ForwardA = 00	ID/EX	The first ALU operand comes from the register file
ForwardA = 10 result	EX/MEM	The first ALU operand is forwarded from prior ALU
ForwardA = 01	MEM/WB	The first ALU operand is forwarded from data memory or an earlier ALU result
ForwardB = 00	ID/EX	The second ALU operand comes from the register file
ForwardB = 10 result	EX/MEM	The second ALU operand is forwarded from prior ALU
ForwardB = 01 memory	MEM/WB	The second ALU operand is forwarded from data or an earlier ALU result

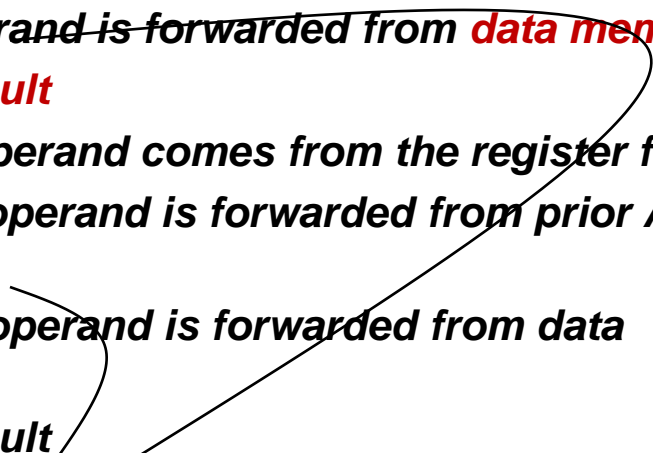

Depending on the selection in the rightmost multiplexor
(see datapath with control diagram)

Data Hazard: Detection and Forwarding

- **Forwarding unit determines multiplexor control according to the following rules:**

1. *EX* hazard

```
if ( EX/MEM.RegWrite // if there is a write...  
    and ( EX/MEM.RegisterRd  $\neq$  0 ) // to a non-$0  
register...
```

**and (EX/MEM.RegisterRd = ID/EX.RegisterRs) // matches,
then ForwardA = 10**

```
if ( EX/MEM.RegWrite           // if there is a write...  
    and ( EX/MEM.RegisterRd  $\neq$  0 ) // to a non-$0  
register...
```

**and (EX/MEM.RegisterRd = ID/EX.RegisterRt)) // matches
then... ForwardB = 10**

Data Hazard: Detection and Forwarding

2. MEM hazard

```
if (      MEM/WB.RegWrite           // if there is a write...
    and ( MEM/WB.RegisterRd  $\neq$  0 ) // to a non-$0 register...
    and ( EX/MEM.RegisterRd  $\neq$  ID/EX.RegisterRs ) // and not already a
//register match with earlier pipeline register...
    and ( MEM/WB.RegisterRd = ID/EX.RegisterRs ) ) // but match with later
//pipeline register, then...
```

ForwardA = 01


```
if (      MEM/WB.RegWrite           // if there is a write...
    and ( MEM/WB.RegisterRd  $\neq$  0 ) // to a non-$0 register...
    and ( EX/MEM.RegisterRd  $\neq$  ID/EX.RegisterRt ) // and not already a
// register match with earlier pipeline register...
    and ( MEM/WB.RegisterRd = ID/EX.RegisterRt ) ) // but match with later
pipeline register, then...
```

ForwardB = 01

This check is necessary, e.g., for sequences such as add \$1, \$1, \$2; add \$1, \$1, \$3; add \$1, \$1, \$4; (array summing...), where an earlier pipeline (EX/MEM) register has more recent data

Forwarding Hardware with Control

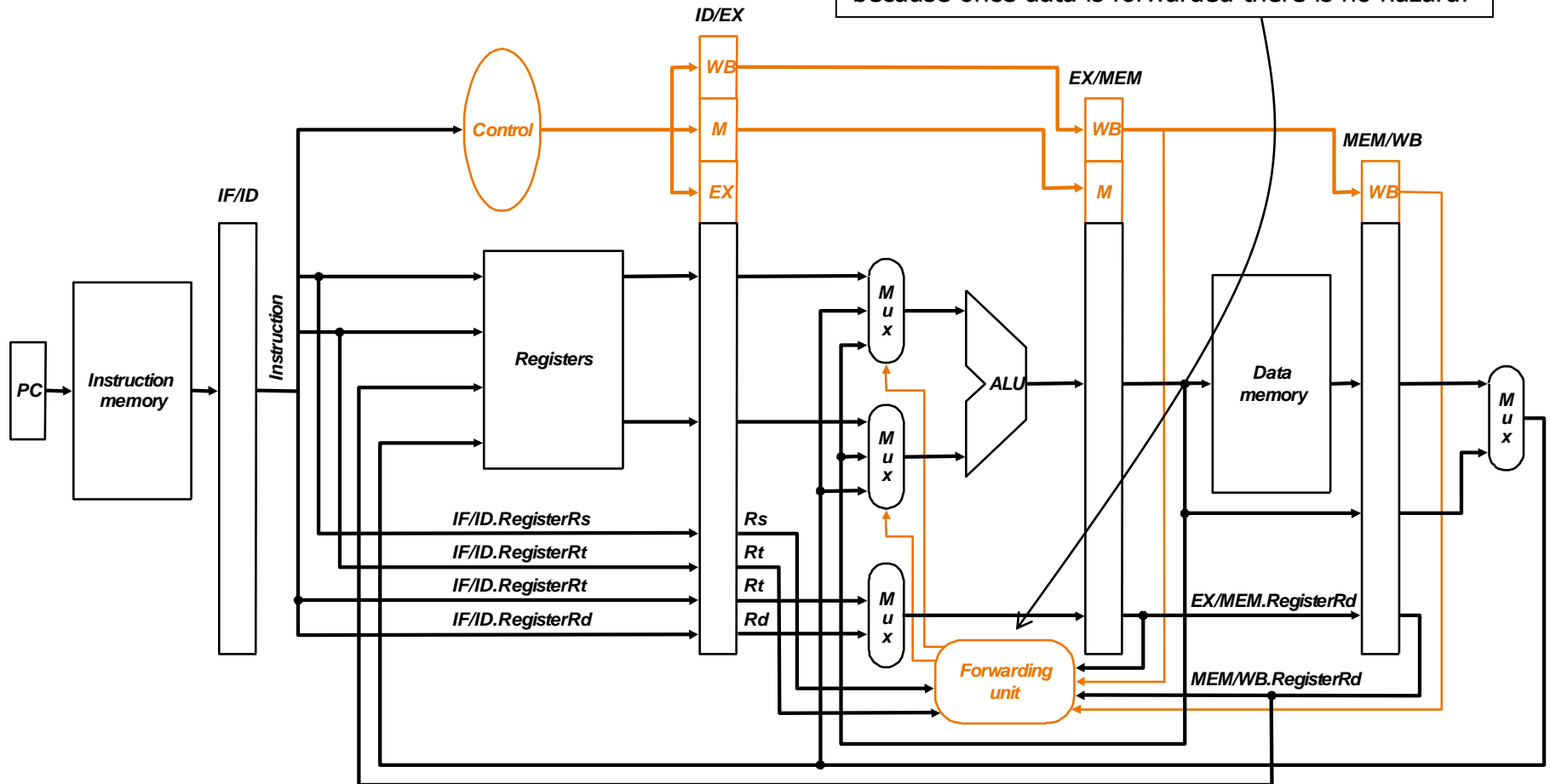Called forwarding unit, not hazard detection unit,
because once data is forwarded there is no hazard!



Datapath with forwarding hardware and control wires – certain details, e.g., branching hardware, are omitted to simplify the drawing

Note: so far we have only handled forwarding to R-type instructions...!

Forwarding

- Execution example:**

```
sub $2, $1, $3
and $4, $2, $5
or $4, $4, $2
add $9, $4, $2
```

Clock cycle 3

Clock 3


add \$9, \$4, \$2

or \$4, \$4, \$2

sub \$2, \$1, \$3

before<1>

before<2>

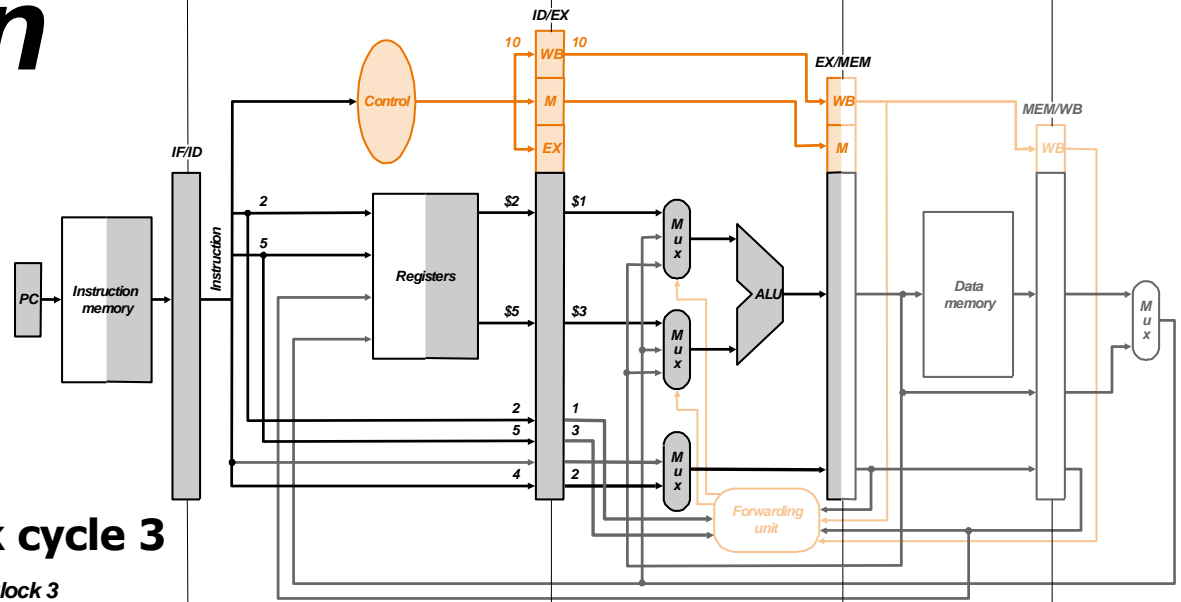

Clock cycle 4


Clock 4

or \$4, \$4, \$2

and \$4, \$2, \$5

sub \$2, ...

before<1>

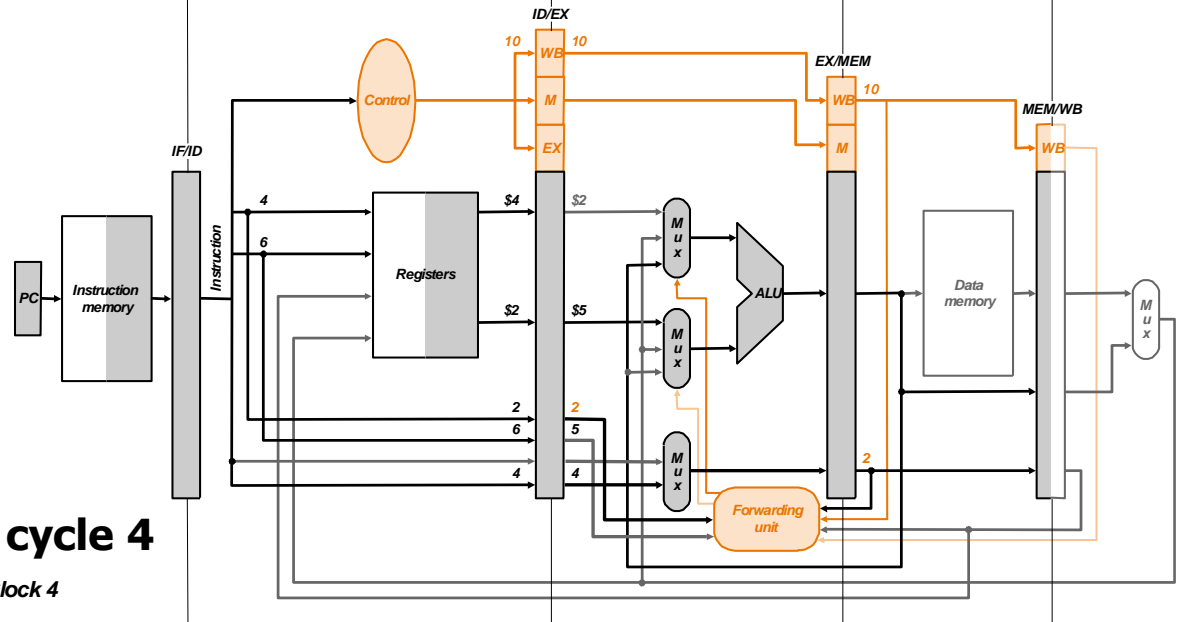

Forwarding

- Execution example (cont.):

```
sub $2, $1, $3
and $4, $2, $5
or $4, $4, $2
add $9, $4, $2
```

Clock cycle 5

Clock 5


after<2>

add \$9, \$4, \$2

or \$4, \$4, \$2

and \$4, ...

sub \$2, ...

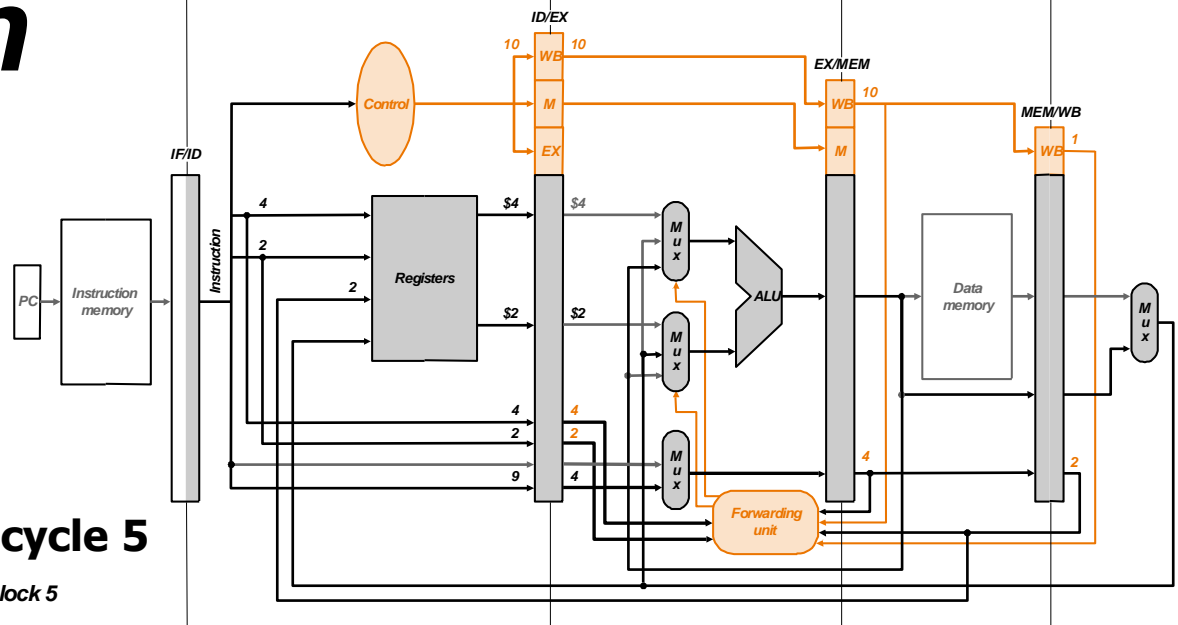

Clock cycle 6


Clock 6

after<1>

add \$9, \$4, \$2

or \$4, ...

and \$4, ...

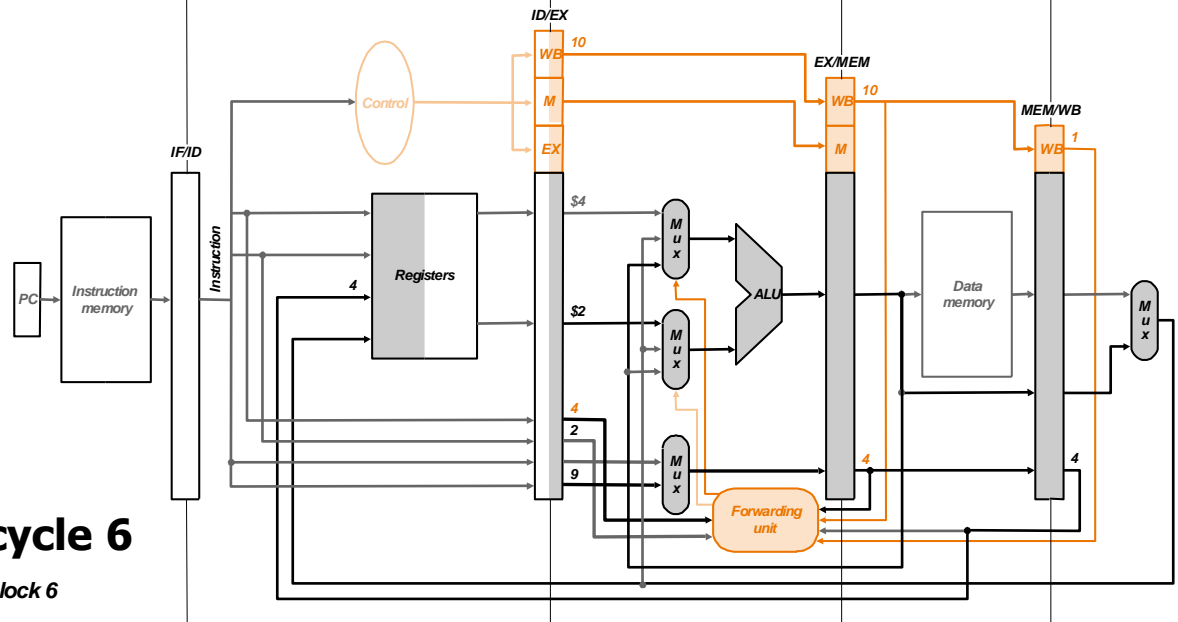


Data Hazards and Stalls

- **Load word can cause a hazard:**
 - **An instruction tries to read a register following a load instruction that writes to the same register**


```
lw $2, 20($1)
and $4, $2, $5
or $8, $2, $6
add $9, $4, $2
slt $1, $6, $7
```

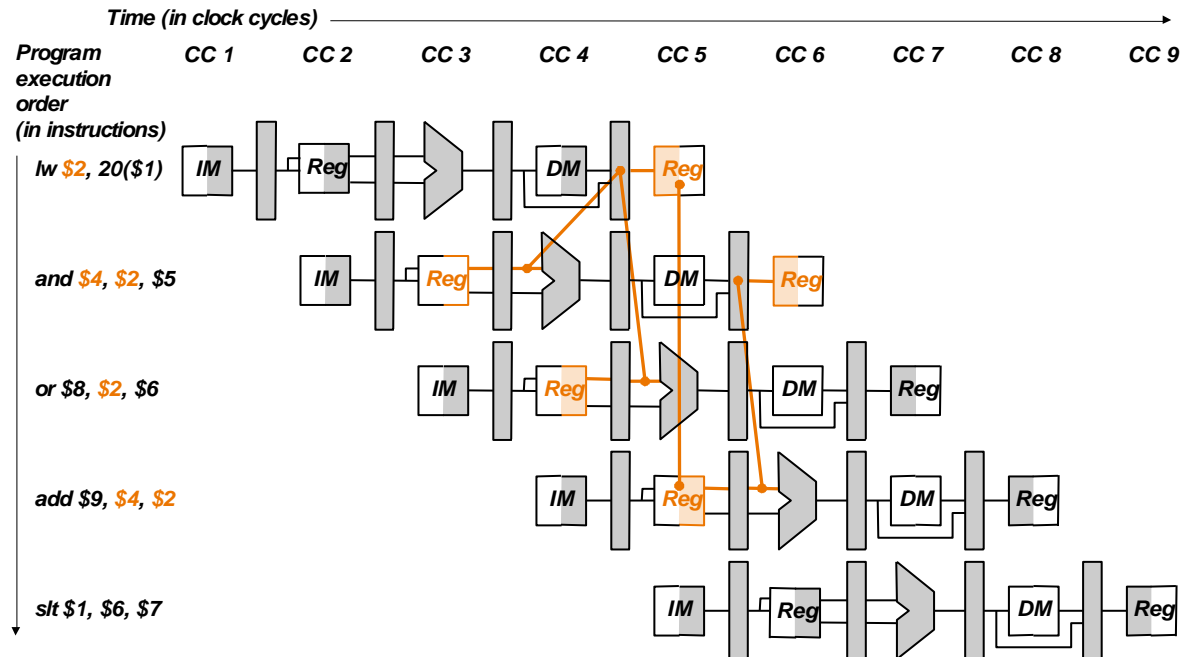As even a pipeline dependency goes backward in time forwarding will not solve the hazard



Therefore, we need a hazard detection unit to stall the pipeline after the load instruction

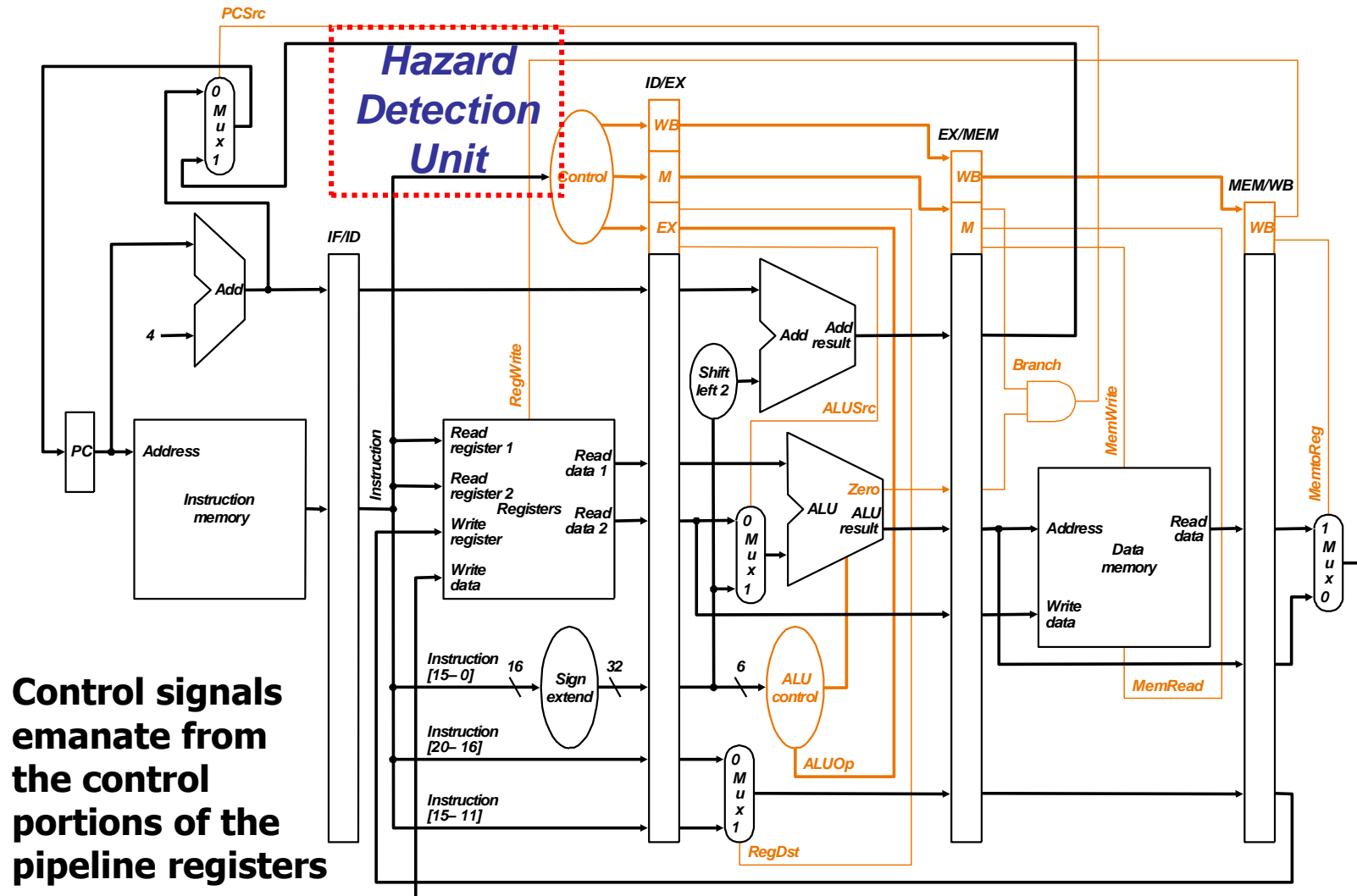Pipelined Datapath with Control II (as before)




Hazard Detection Logic to Stall

- **Hazard detection unit implements the following check at ID stage, if to stall by inserting a bubble into the pipeline by changing the EX, MEM and WB control fields of the ID/EX pipeline register to 0**

```
if ( ID/EX.MemRead                                // if the instruction in the EX stage is a load...
    and ( ( ID/EX.RegisterRt = IF/ID.RegisterRs )    // and the destination register
        or ( ID/EX.RegisterRt = IF/ID.RegisterRt ) ) // matches either source register
    STALL                                           // of the instruction in the ID stage, then...stall the
    pipeline
```

- **Insert a *bubble* into the EX stage after a load instruction**
 - **Bubble is a *no-op* that wastes one clock cycle**
 - **By deasserting all nine control signals (setting them to 0) in EX, MEM and WB stages**
 - **Restrict the write operation to any register or memory**

Hazard Detection Unit

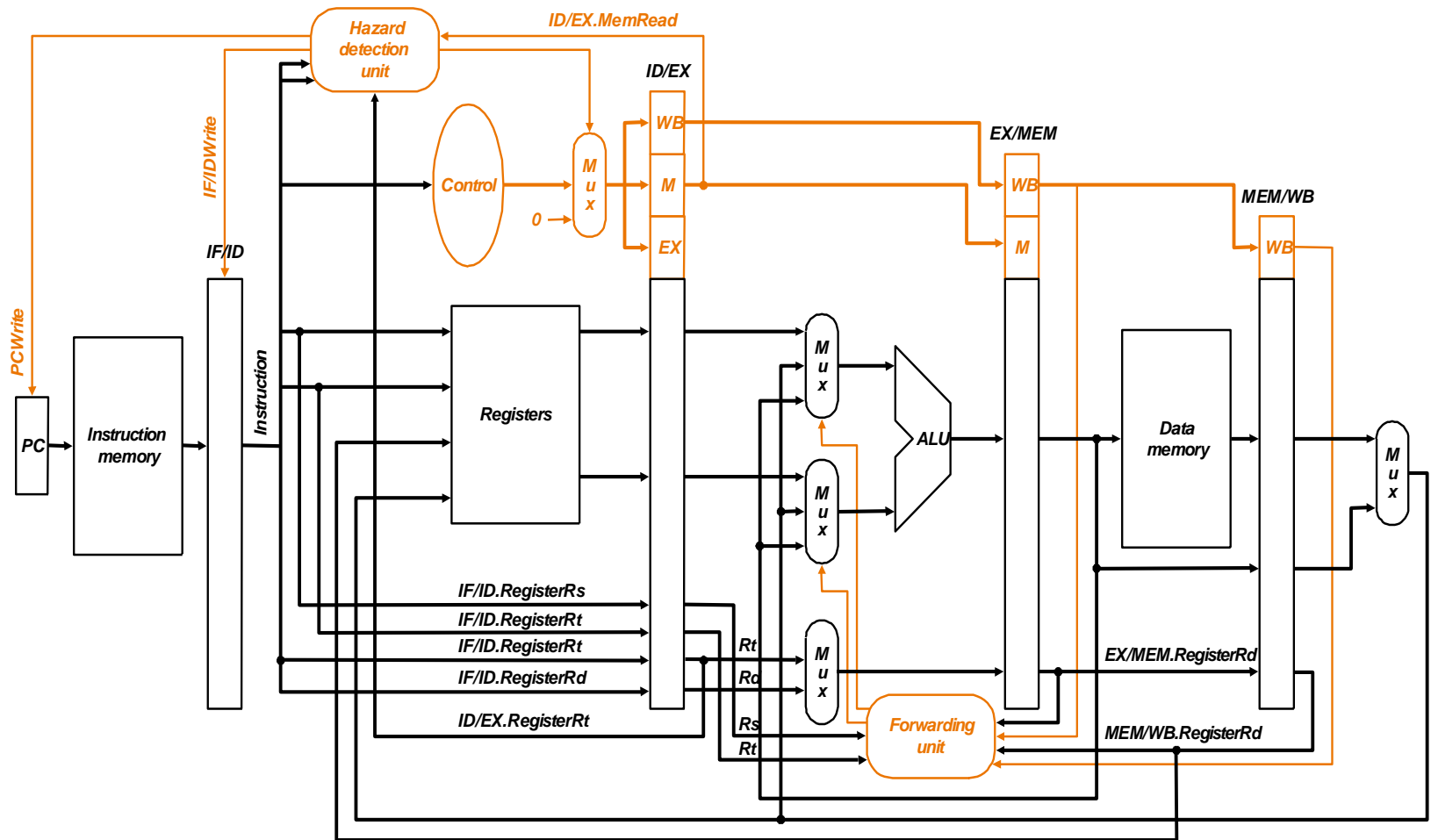


Datapath with forwarding hardware, the hazard detection unit and controls wires – certain details, e.g., branching hardware are omitted to simplify the drawing

Mechanics of Stalling

- *If the check to stall verifies, then the pipeline needs to stall only 1 clock cycle after the load as after that the forwarding unit can resolve the dependency*
- *What the hardware does to stall the pipeline 1 cycle:*
 - *does not let the IF/ID register change (disable write!) – this will cause the instruction in the ID stage to repeat, i.e., stall*
 - *therefore, the instruction, just behind, in the IF stage must be stalled as well – so hardware does not let the PC change (disable write!) – this will cause the instruction in the IF stage to repeat, i.e., stall*
 - *changes all the EX, MEM and WB control fields in the ID/EX pipeline register to 0, so effectively the instruction just behind the load becomes a nop – a bubble is said to have been inserted into the pipeline*
 - *note that we cannot turn that instruction into an nop by 0ing all the bits in the instruction itself – recall nop = 00...0 (32*

Stalling Resolves a Hazard

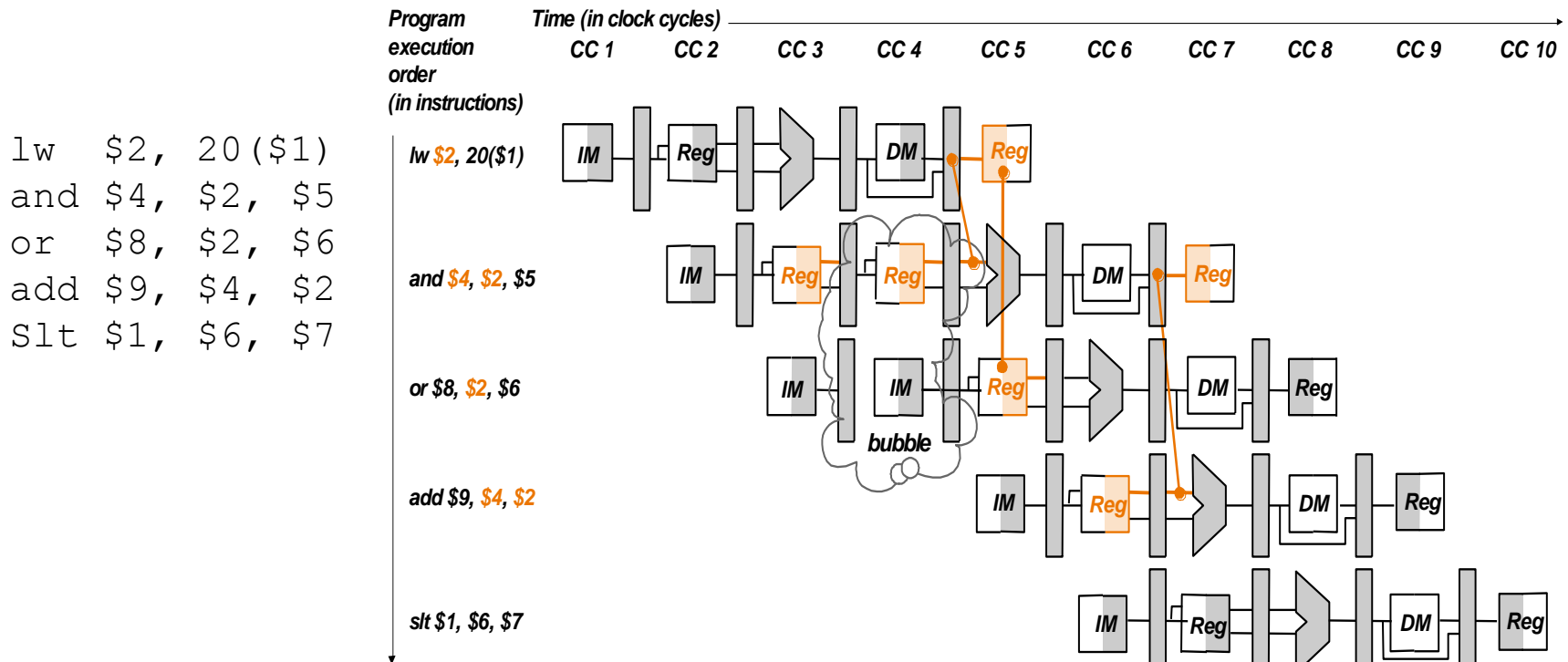- **Same instruction sequence as before for which forwarding by itself could not resolve the hazard:**



Hazard detection unit inserts a 1-cycle bubble in the pipeline, after which all pipeline register dependencies go forward so then the forwarding unit can handle them and there are no more hazards


Stalling

- Execution example:

```
lw $2, 20($1)
and $4, $2, $5
or $4, $4, $2
add $9, $4, $2
```


Clock cycle 2

Clock 2

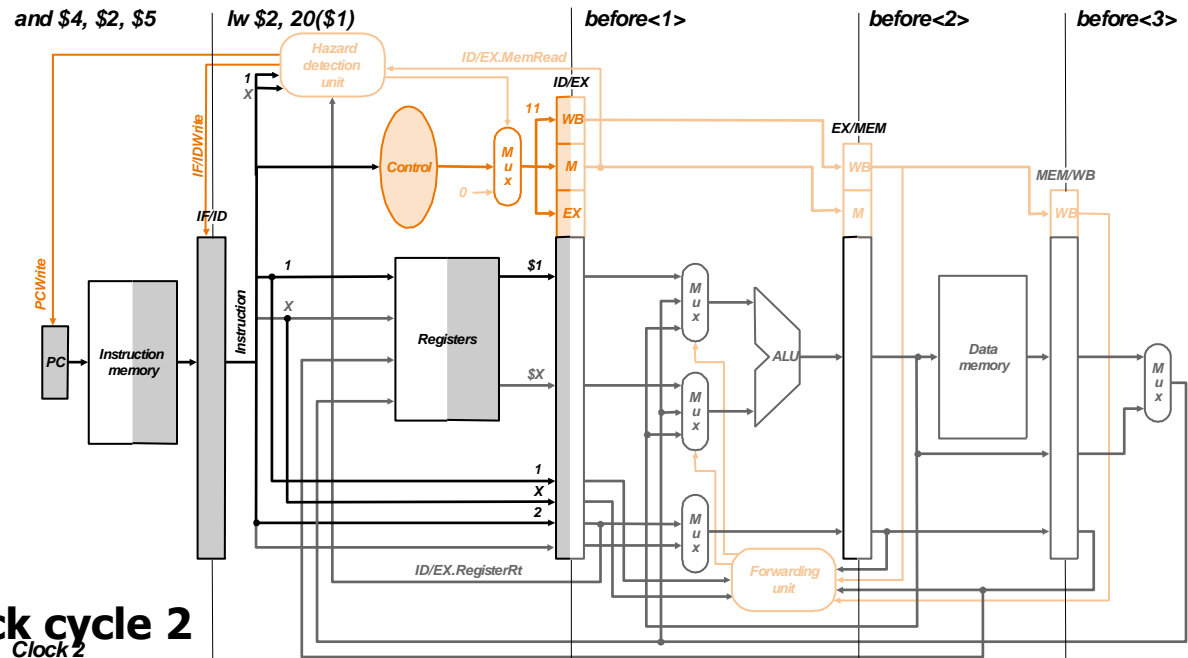

Clock cycle 3

Clock 3

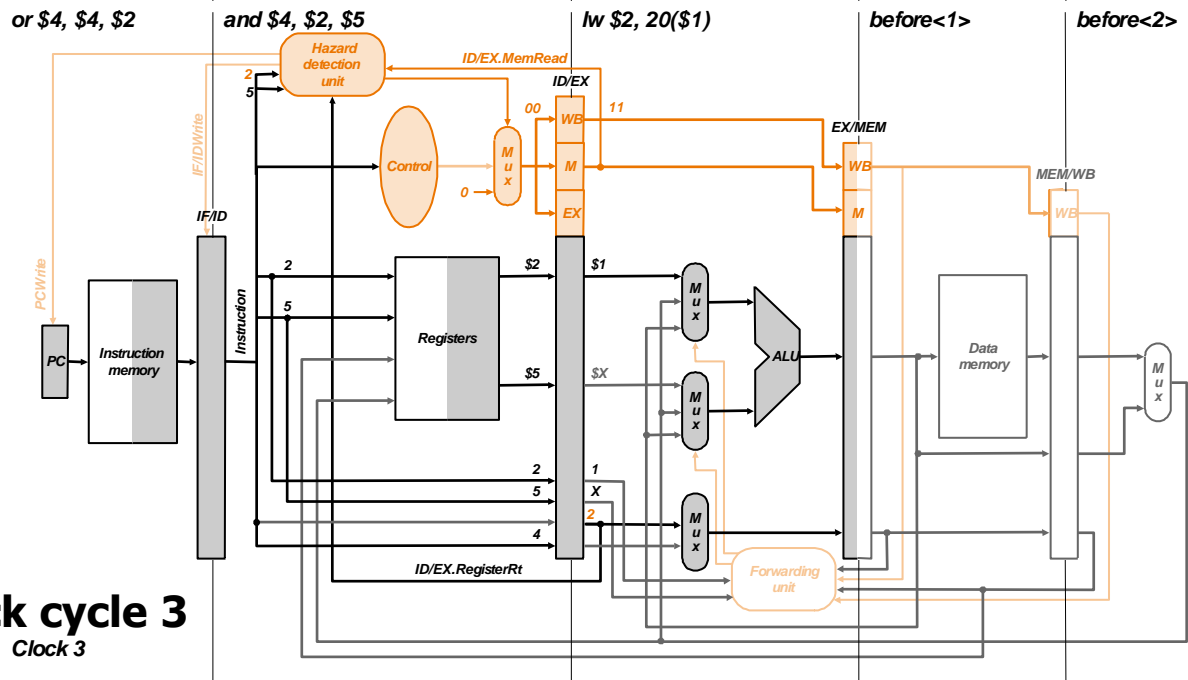

- **Execution example (cont.):**

Clock cycle 4

add \$9, \$4, \$2

or \$4, \$4, \$2


and \$4, \$2, \$5

| ***bubble***

| **lw \$2,...**

Clock cycle 5

Clock 5

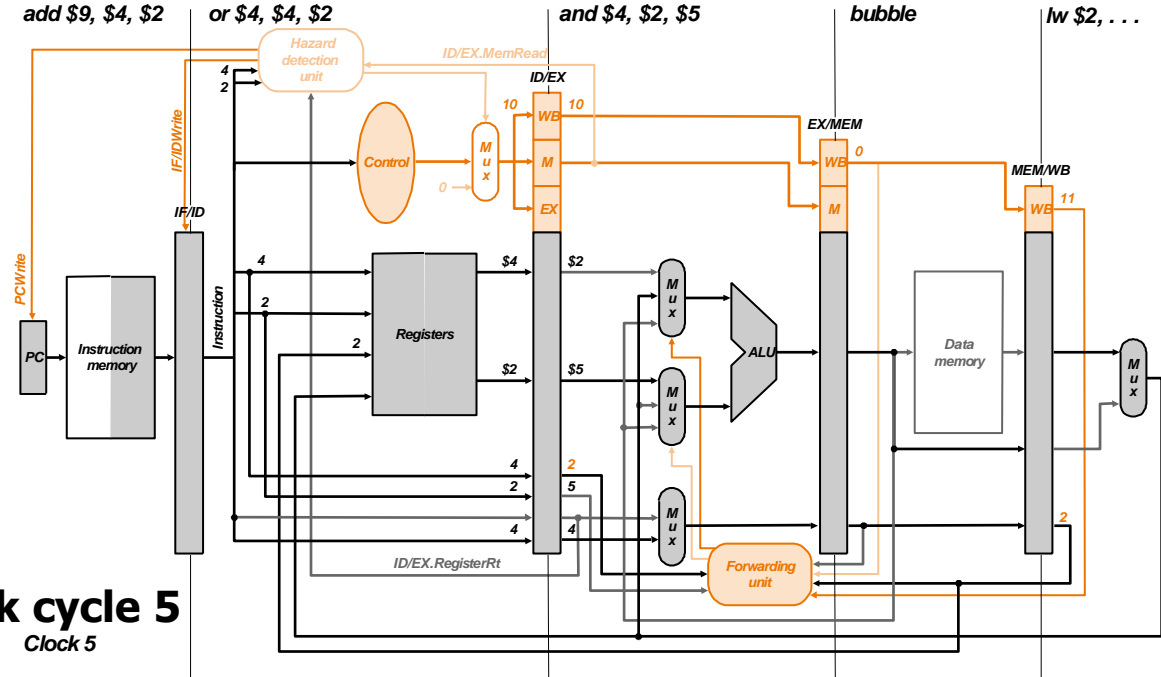


Stalling


- Execution example (cont.):

```
lw    $2, 20($1)
and   $4, $2, $5
or    $4, $4, $2
add   $9, $4, $2
```

Clock cycle 6
Clock 6

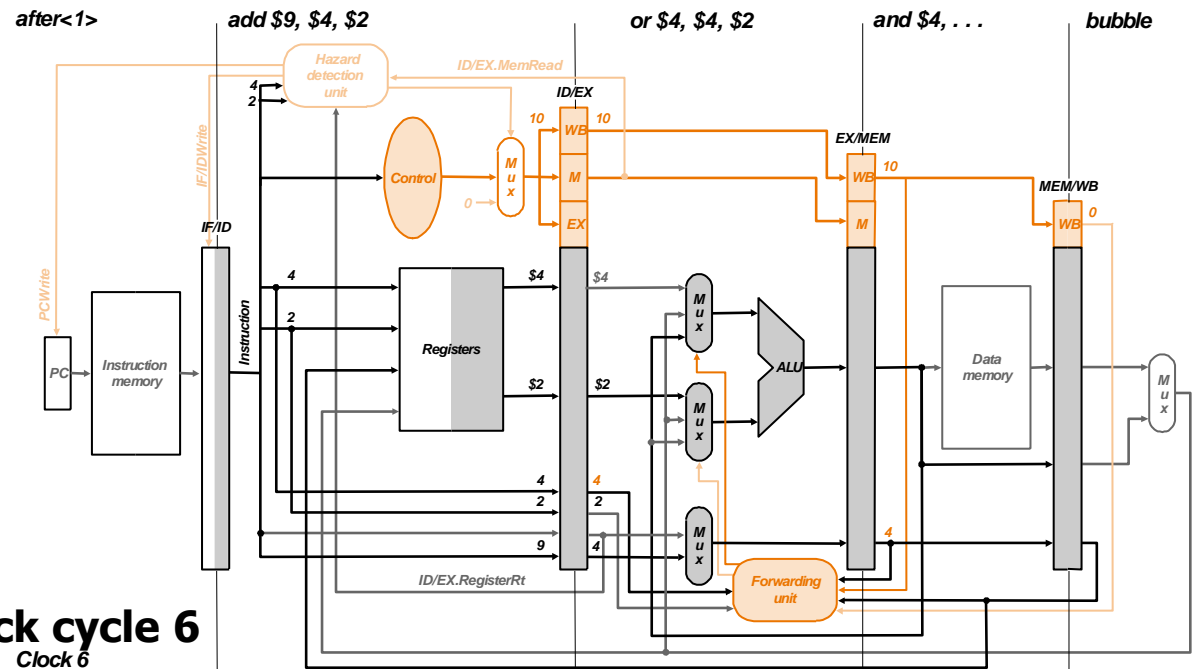

Clock cycle 7
Clock 7

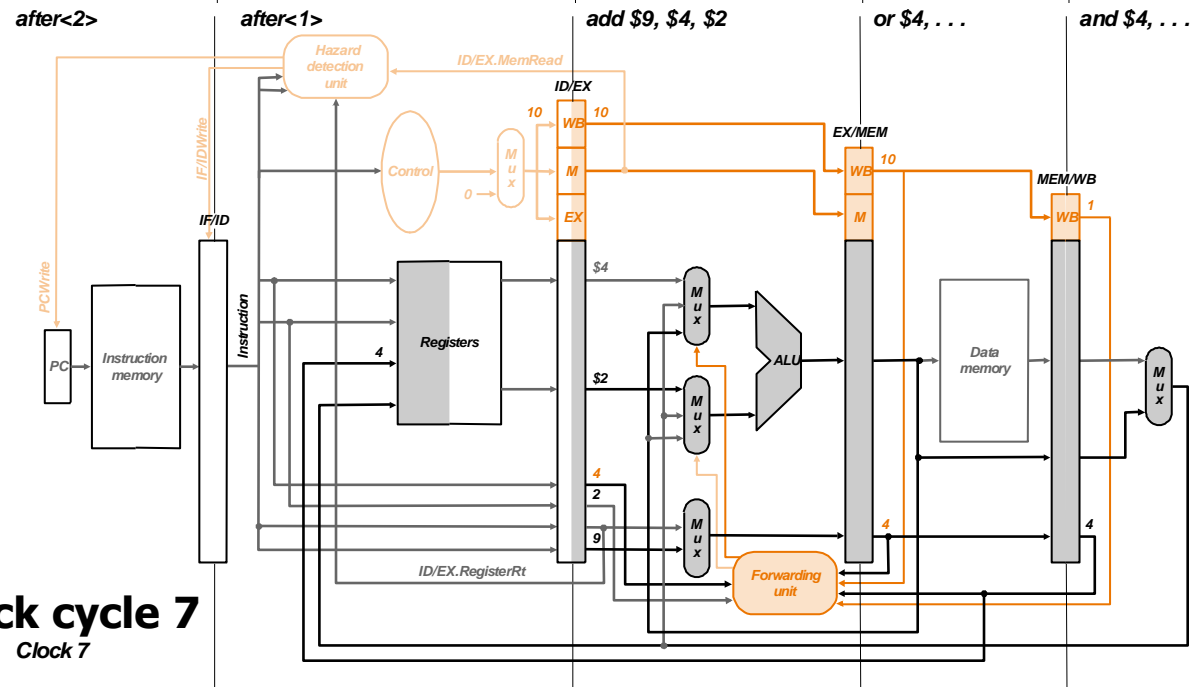


Control Hazards

- ***Need to make a decision based on the result of a previous instruction still executing in pipeline***
- ***Jump and Branch can cause great performance loss***
- ***Jump instruction needs only the jump target address***
- ***Branch instruction needs two things:***
 - ***Branch Result*** ***Taken or Not Taken***
 - ***Branch Target Address***
 - ***PC + 4*** ***If Branch is NOT taken***
 - ***PC + 4 + 4 × immediate*** ***If Branch is Taken***

Control Hazards

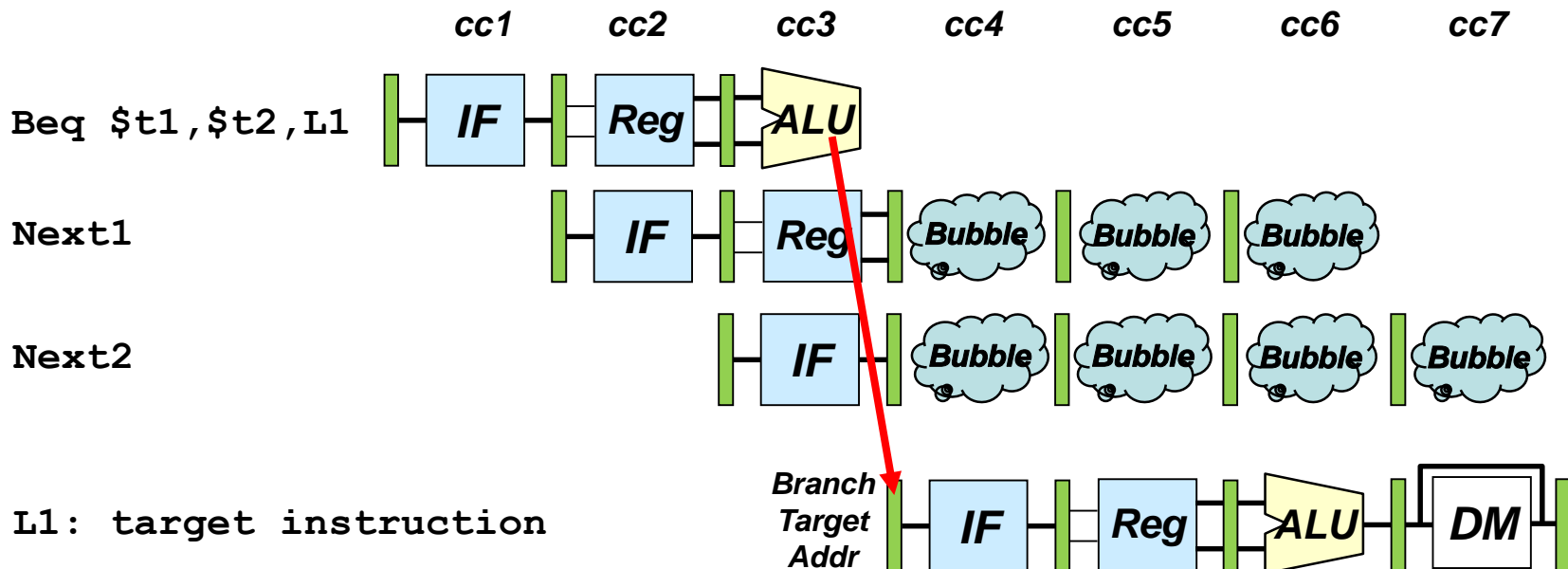- Solution 1 *Stall* the pipeline
- Control logic detects a **Branch** instruction in the 2nd Stage
- ALU computes the **Branch outcome** in the 3rd Stage
- **Next1** and **Next2** instructions will be fetched anyway
- Convert **Next1** and **Next2** into bubbles if branch is taken





- Branch outcome is computed in ID stage with added hardware (later...)

Control Hazards

Solution 2 Predict branch outcome, e.g., predict branch-not-taken

□


No waste of cycles, if success

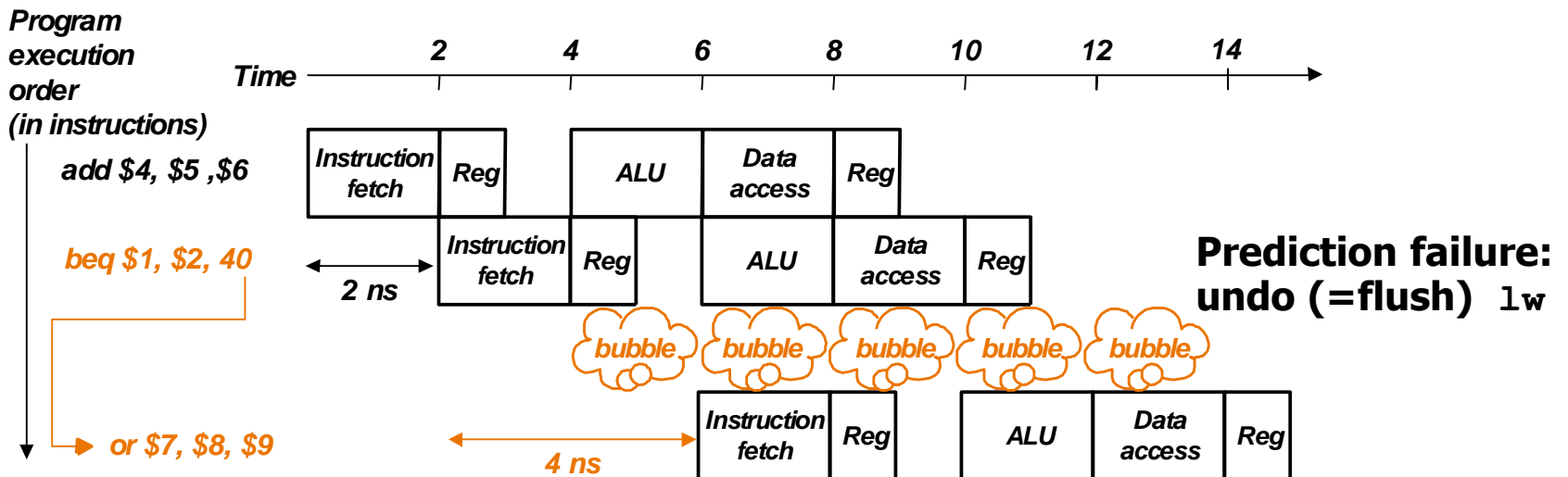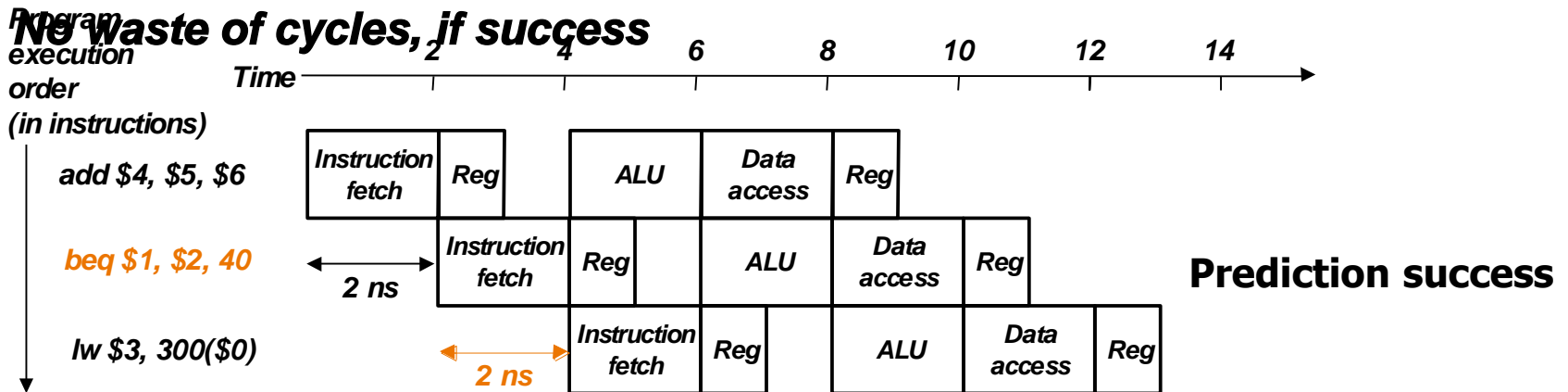

Control Hazards

Solution 3 Delayed branch: always execute the sequentially next statement with the branch executing after one instruction delay

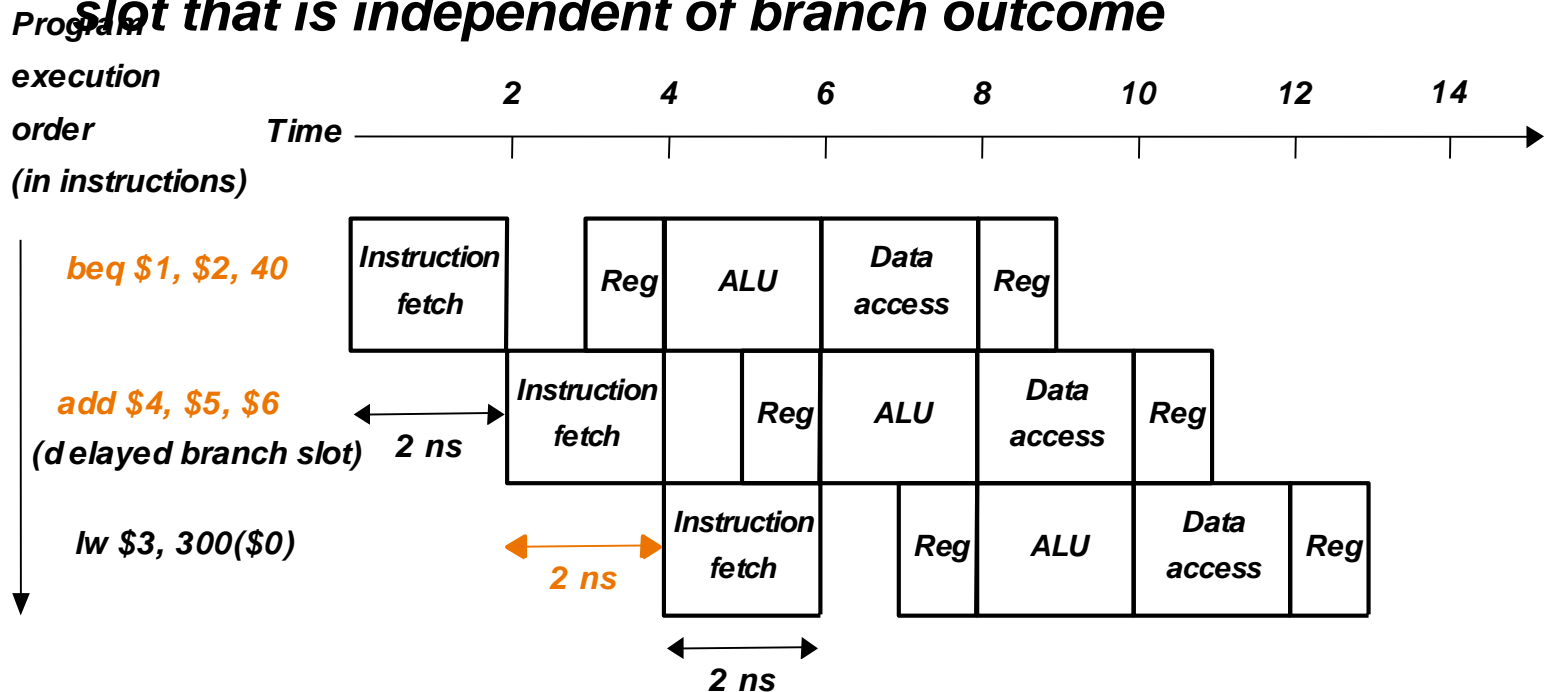- compiler's job to find a statement that can be put in the slot that is independent of branch outcome




Delayed branch *beq* is followed by *add* that is independent of branch outcome

Control (or Branch) Hazards

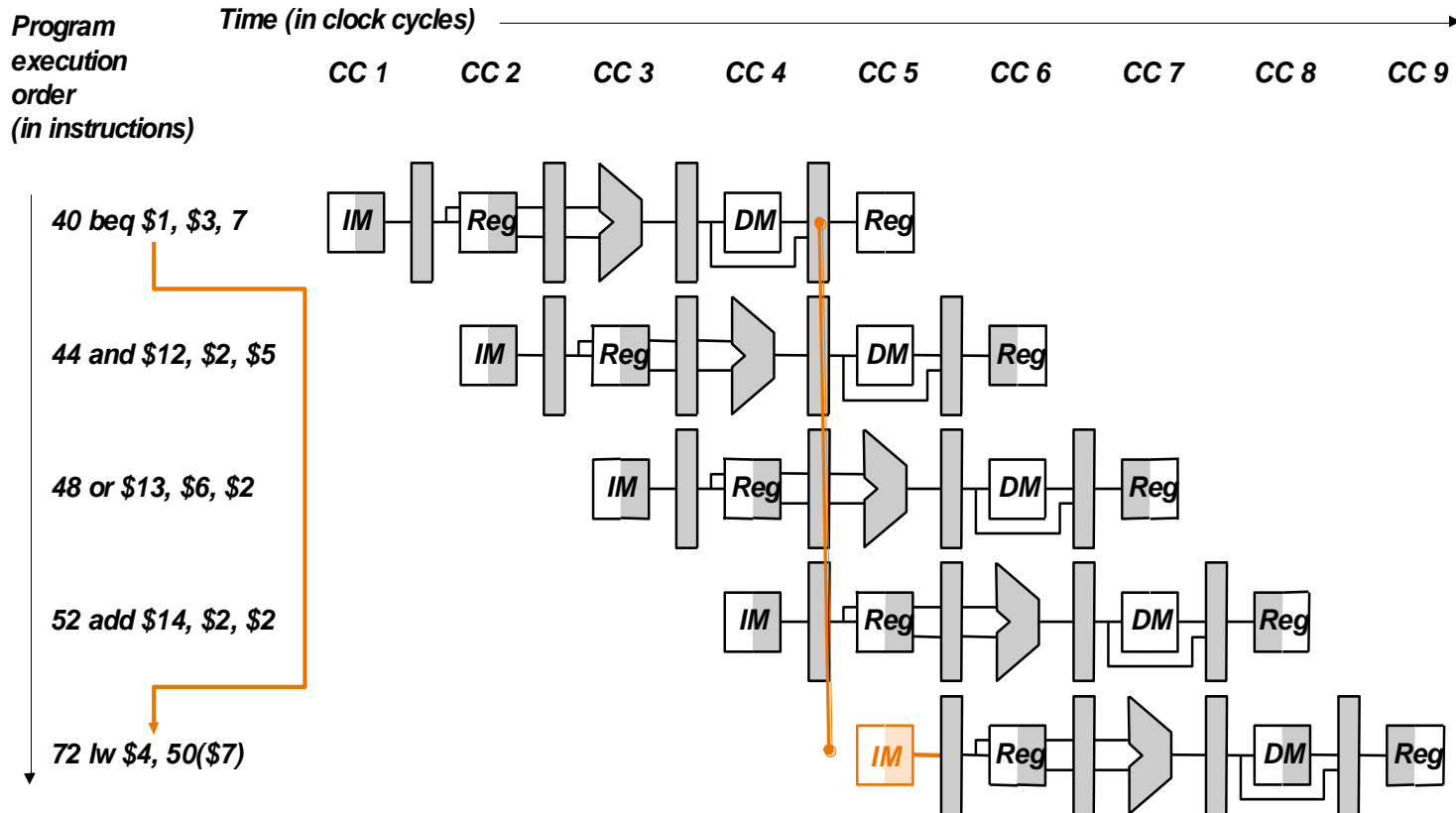- *Problem with branches in the pipeline we have so far is that the branch decision is not made till the MEM stage – so what instructions, if at all, should we insert into the pipeline following the branch instructions?*
- *Possible solution: stall the pipeline till branch decision is known*
 - *not efficient, slow the pipeline significantly!*
- *Another solution: predict the branch outcome*
 - *e.g., always predict branch-not-taken – continue with next sequential instructions*
 - *if the prediction is wrong have to flush the pipeline behind the branch – discard instructions already fetched or decoded – and continue execution at the branch target*
- *Is there any other OPTIMAL solution?*

Predicting Branch-not-taken: Misprediction delay



The outcome of branch taken (prediction wrong) is decided only when beq is in the MEM stage, so the following three sequential instructions already in the pipeline have to be flushed and execution resumes at lw


Optimizing the Pipeline to Reduce Branch Delay

- *Move the branch decision from the MEM stage (as in our current pipeline) earlier to the ID stage*
 - *calculating the branch target address involves moving the branch adder from the MEM stage to the ID stage – inputs to this adder, the PC value and the immediate fields are already available in the IF/ID pipeline register*
 - *calculating the branch decision is efficiently done, e.g., for equality test, by XORing respective bits and then ORing all the results and inverting, rather than using the ALU to subtract and then test for zero (when there is a carry delay)*
 - *with the more efficient equality test we can put it in the ID stage without significantly lengthening this stage – remember an objective of pipeline design is to keep pipeline stages balanced*
 - *we must correspondingly make additions to the forwarding and hazard detection units to forward to or stall the branch at the ID stage in case the branch decision depends on an earlier result*

Flushing on Misprediction

- *Same strategy as for stalling on load-use data hazard...*
- *Zero out all the control values (or the instruction itself) in pipeline registers for the instructions following the branch that are already in the pipeline – effectively turning them into nops – so they are flushed*
 - *in the optimized pipeline, with branch decision made in the ID stage, we have to flush only one instruction in the IF stage – the branch delay penalty is then only one clock cycle*

Optimized Datapath for Branch

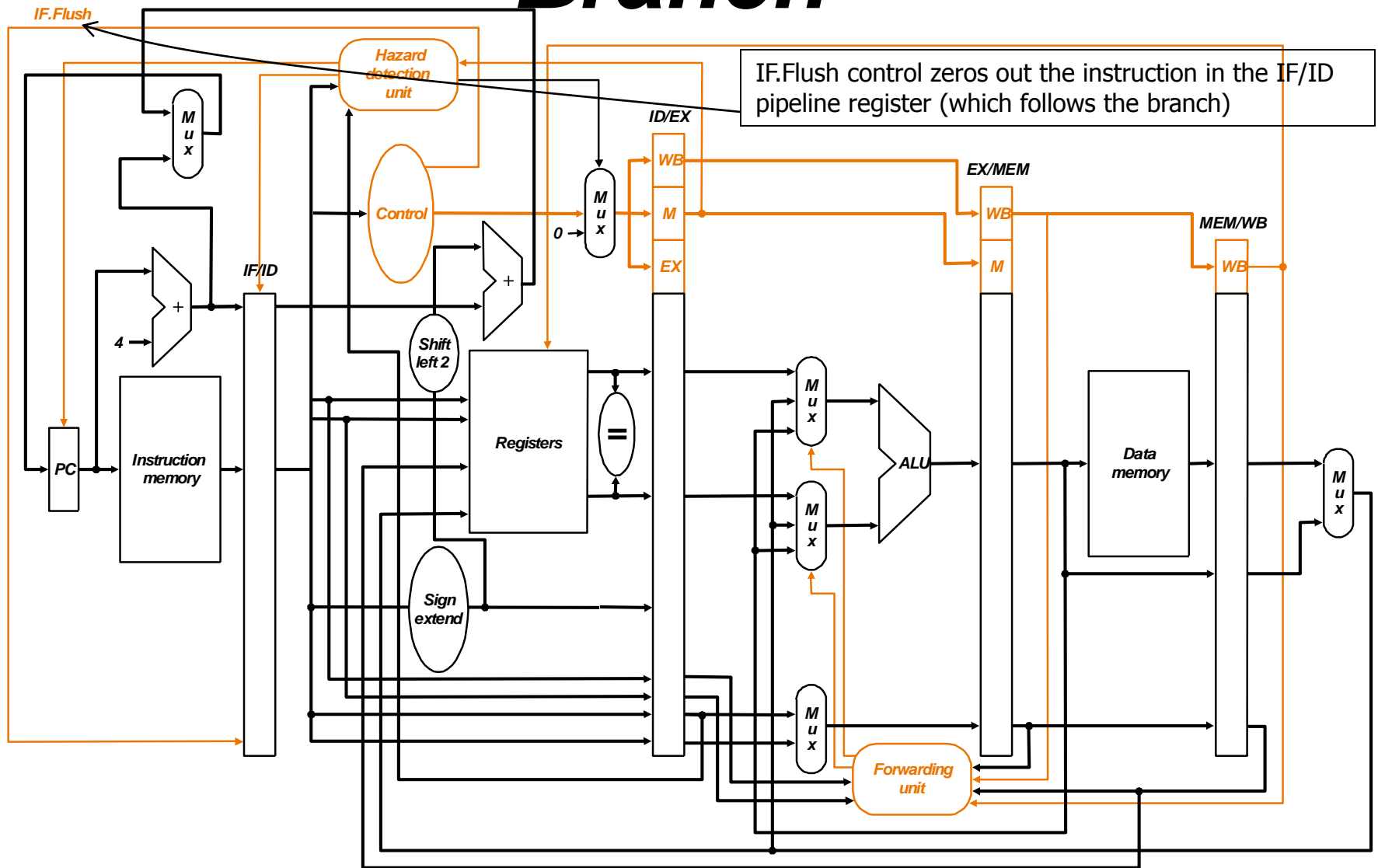

Branch decision is moved from the MEM stage to the ID stage – simplified drawing not showing enhancements to the forwarding and hazard detection units

Pipelined Branch

- Execution example:


```

36 sub $t0, $t4, $t8
40 beq $t1, $t3, 7
44 and $t2, $t2, $t5
48 or $t3, $t2, $t6
52 add $t4, $t4, $t2
56 slt $t5, $t6, $t7
...
72 lw $t4, 50($t7)
  
```

Optimized pipeline with only one bubble as a result of the taken branch

Clock cycle 3

Clock 3

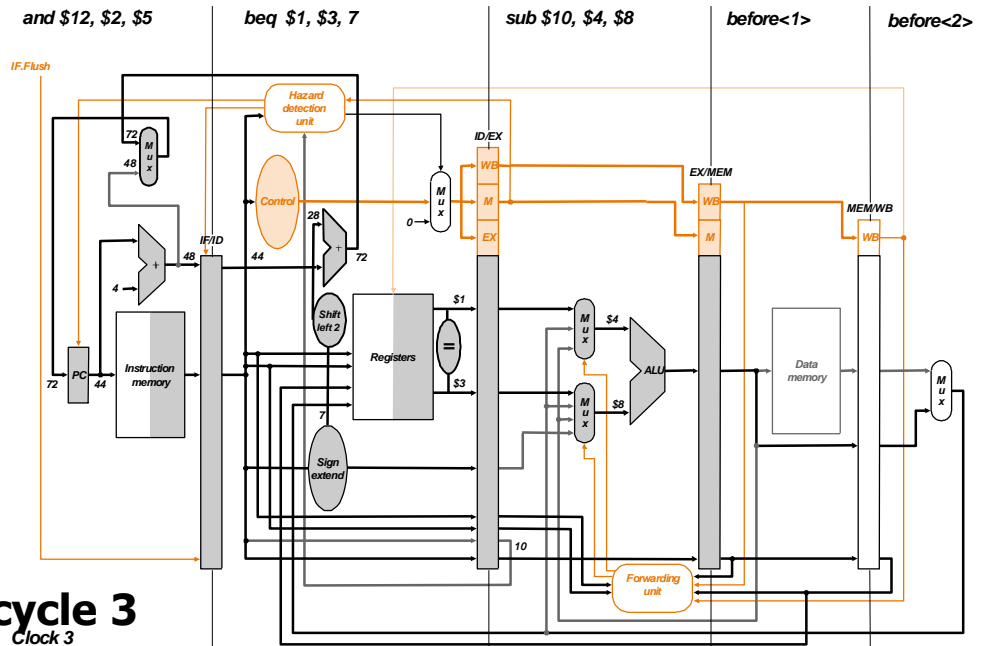

lw \$t4, 50(\$t7)

bubble (nop)


beq \$t1, \$t3, 7

sub \$t0, ...

before<1>

Clock cycle 4

Clock 4

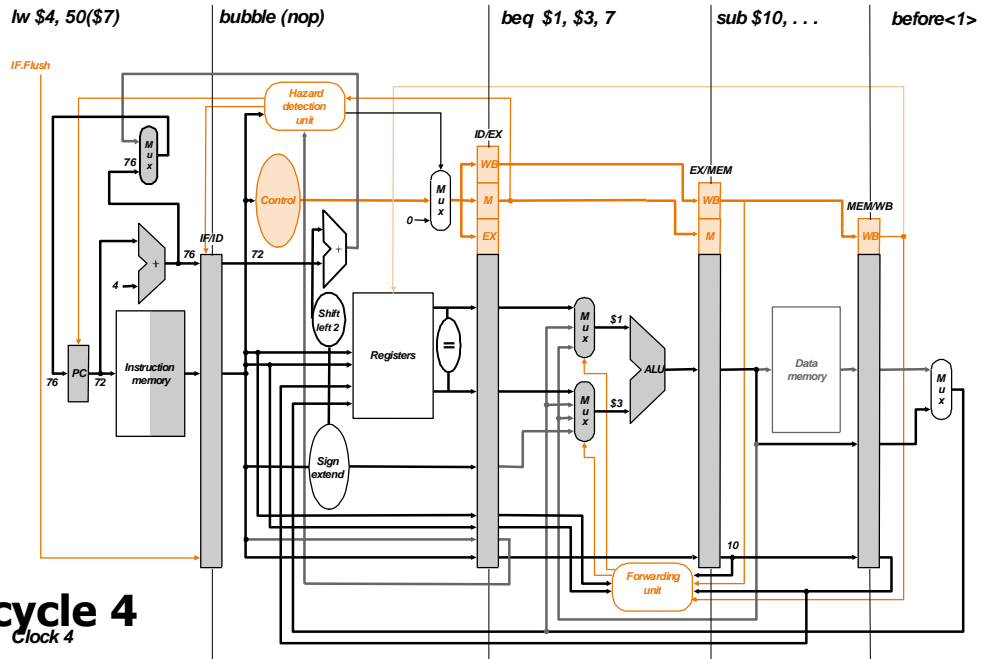

Simple Example: Comparing Performance

- *Compare performance for single-cycle, multicycle, and pipelined datapaths using the gcc instruction mix*
 - ***assume 2 ns for memory access, 2 ns for ALU operation, 1 ns for register read or write***
 - ***assume gcc instruction mix 23% loads, 13% stores, 19% branches, 2% jumps, 43% ALU***
 - ***for pipelined execution assume***
 - ***50% of the loads are followed immediately by an instruction that uses the result of the load***
 - ***25% of branches are mispredicted***
 - ***branch delay on misprediction is 1 clock cycle***
 - ***jumps always incur 1 clock cycle delay so their average time is 2 clock cycles***

Simple Example: Comparing Performance

- ***Single-cycle*** (p. 373): average instruction time 8 ns
- ***Multicycle*** (p. 397): average instruction time 8.04 ns
- ***Pipelined:***
 - loads use 1 cc (clock cycle) when no load-use dependency and 2 cc when there is dependency – given 50% of loads are followed by dependency the average cc per load is 1.5
 - stores use 1 cc each
 - branches use 1 cc when predicted correctly and 2 cc when not – given 25% misprediction average cc per branch is 1.25
 - jumps use 2 cc each
 - ALU instructions use 1 cc each
 - therefore, average CPI is
$$1.5 \times 23\% + 1 \times 13\% + 1.25 \times 19\% + 2 \times 2\% + 1 \times 43\% = 1.18$$
 - therefore, average instruction time is $1.18 \times 2 = 2.36$ ns
 - 50% of the loads are followed immediately by an instruction that uses the result of the load
 - 25% of branches are mispredicted
 - branch delay on misprediction is 1 clock cycle
 - jumps always incur 1 clock cycle delay so their average time is 2 clock cycles

Pipelining Advantages

- ***Higher maximum throughput***
 - ***Higher utilization of CPU resources***
-
- ***But, more hardware needed, perhaps complex control***

Pipelining Exercise

Consider the following MIPS assembly code:

```
add $3, $2, $3  
lw $4, 100($3)  
sub $7, $6, $2  
xor $6, $4, $3
```

Assume there is no forwarding or stalling circuitry in a pipelined processor that uses the standard 5-stages (IF, ID, EX, Mem, WB). Instead, we will require the compiler to add no-ops to the code to ensure correct execution. (Assume that if the processor reads and writes to the same register in a given cycle, the value read out will be the new value that is written in.)

- 1. Rewrite the code to include the no-ops that are needed. Do not change the order of the four statements. Use as few no-ops as possible.***
- 2. Suppose the compiler is allowed to change the order of the four statements, provided it doesn't change the final answer. Is it possible to reduce the number of no-ops needed? Why or why not?***

Tutorial Question

Draw an execution diagram that shows where forwarding and stalling would take place, if any.

add \$6,\$5,\$2

lw \$7,0(\$6)

addi \$7,\$7,10

add \$6,\$4,\$2

sw \$7,0(\$6)

addi \$2,\$2,4

blt \$2,\$3,loop

add \$6,\$5,\$2

Summary-Pipeline Hazards

- ***Structural hazards***

- *Caused by resource contention*
- *Two operations require a single piece of hardware e.g. Memory*
- *Using same resource by two instructions during the same cycle*
- *Structural hazards can be overcome by adding additional hardware*

- ***Data hazards***

- *Instruction from one pipeline stage is “dependant” of data computed in previous pipeline stage*
- *Hardware can detect dependencies between instructions*

- ***Control hazards***


- *Caused by instructions that change control flow (branches/jumps)*
 - *i.e. delays in changing the flow of control*
- *Requiring subsequent instruction fetches to be predicted*
 - *Flushed if prediction does not hold (make sure no state change)*
- *Branch hazards can use dynamic prediction/speculation, branch delay slot*

Refer

***Patterson Chapter 6: Topics 6.1 to
6.6***

End...

Pipelined Datapath with Control II

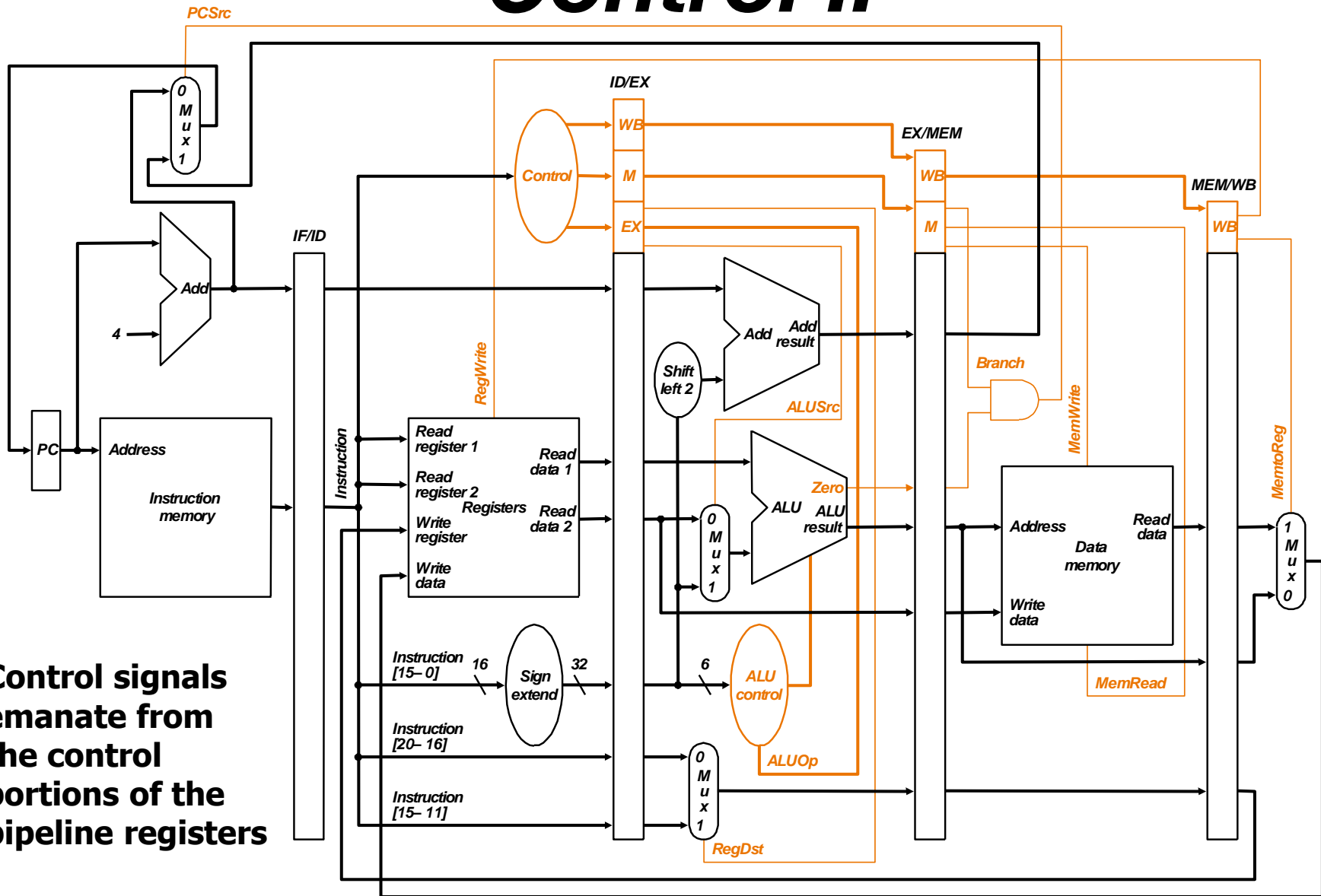

**Control signals
emanate from
the control
portions of the
pipeline registers**

Pipelined Execution and Control

Instruction sequence:


```
lw $t0, 20($t1)
sub $t1, $t2, $t3
and $t2, $t4, $t7
or $t3, $t6, $t7
add $t4, $t8, $t9
```

Label "before<i>" means
ith instruction before
lw

Clock cycle 2
Clock 2

Dark Right Area indicates the Read Operation
Dark Left Area indicates the Write Operation

Clock cycle 1
Clock 1

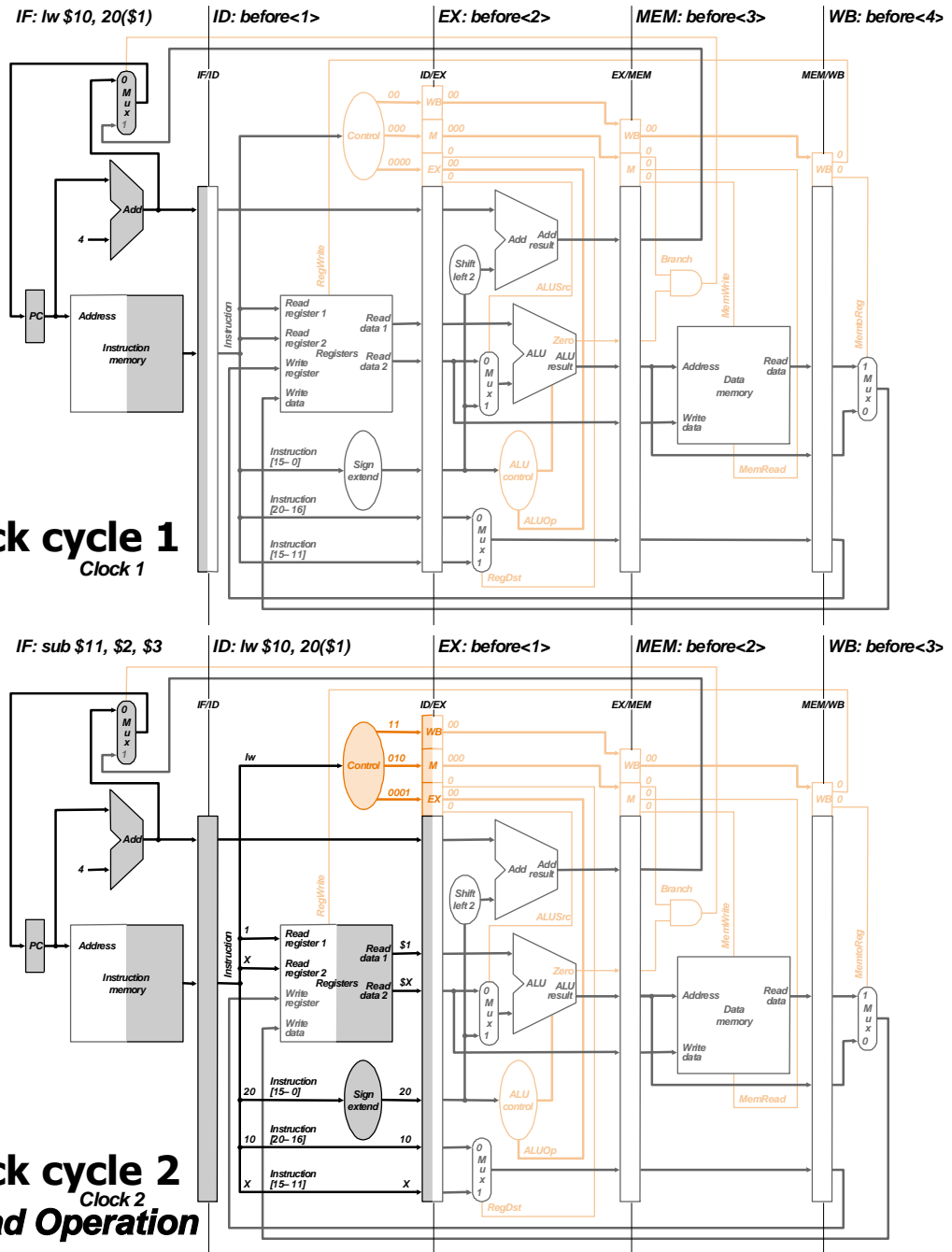


Pipelined Execution and Control


- Instruction sequence:

```
lw $10, 20($1)
sub $11, $2, $3
and $12, $4, $7
or $13, $6, $7
add $14, $8, $9
```

Clock cycle 3
Clock 3

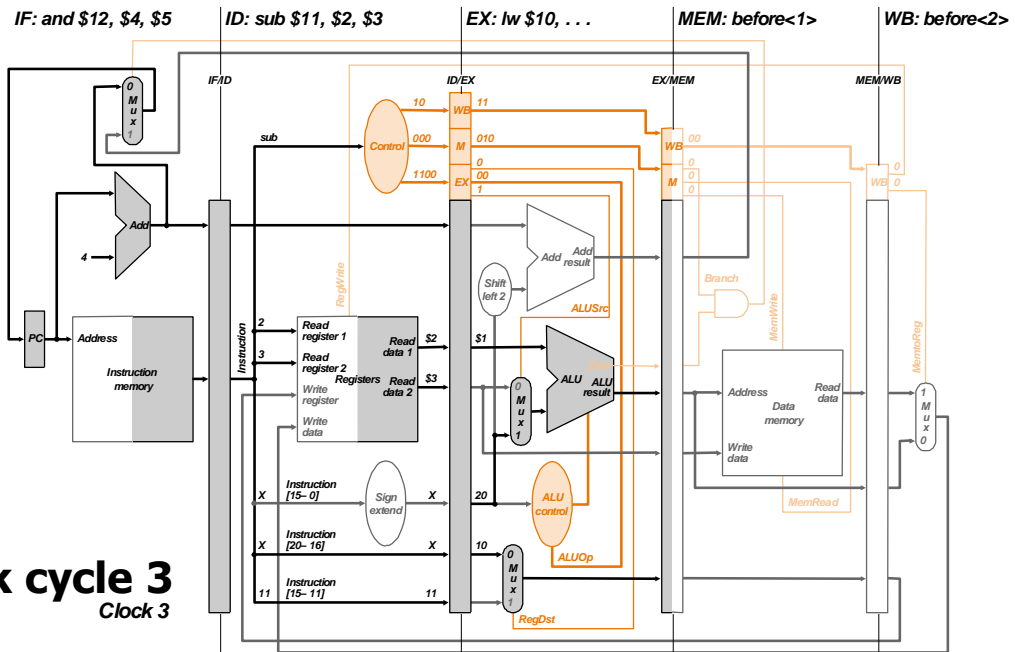

Clock cycle 4
Clock 4

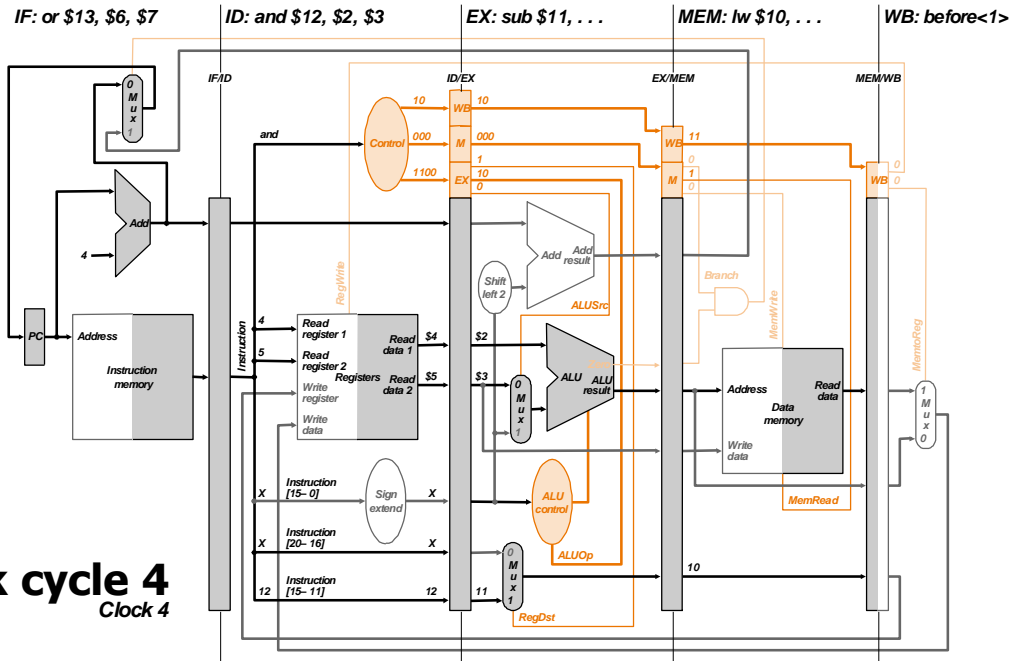


Pipelined Execution and Control

- Instruction sequence:


```
lw    $10, 20($1)
sub   $11, $2, $3
and   $12, $4, $7
or    $13, $6, $7
add   $14, $8, $9
```

Label "after<i>" means
i th instruction after add

Clock cycle 5
Clock 5

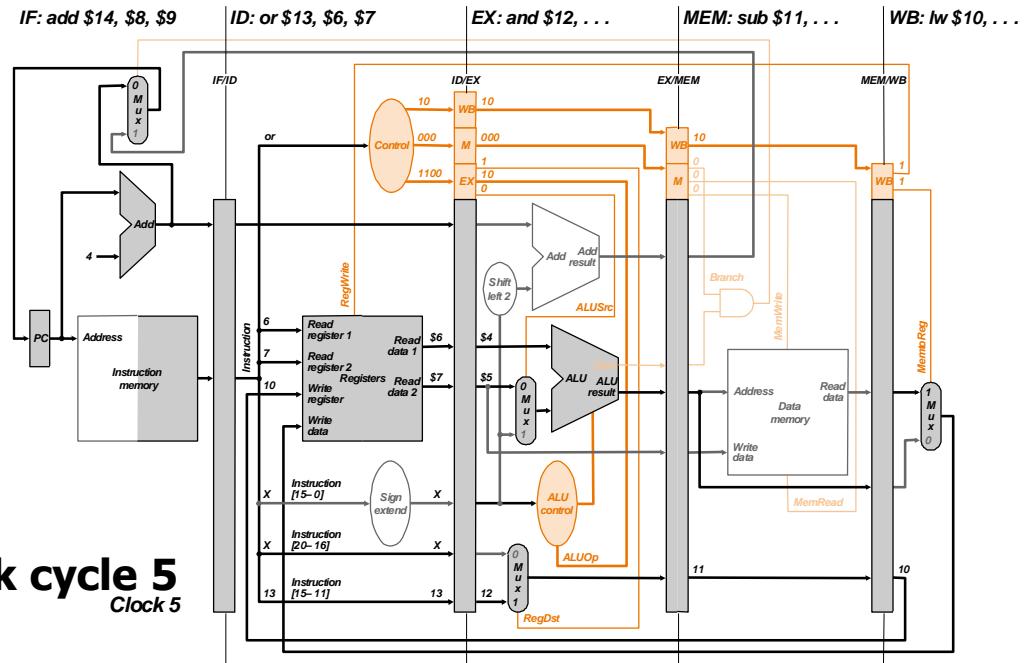

Clock cycle 6
Clock 6

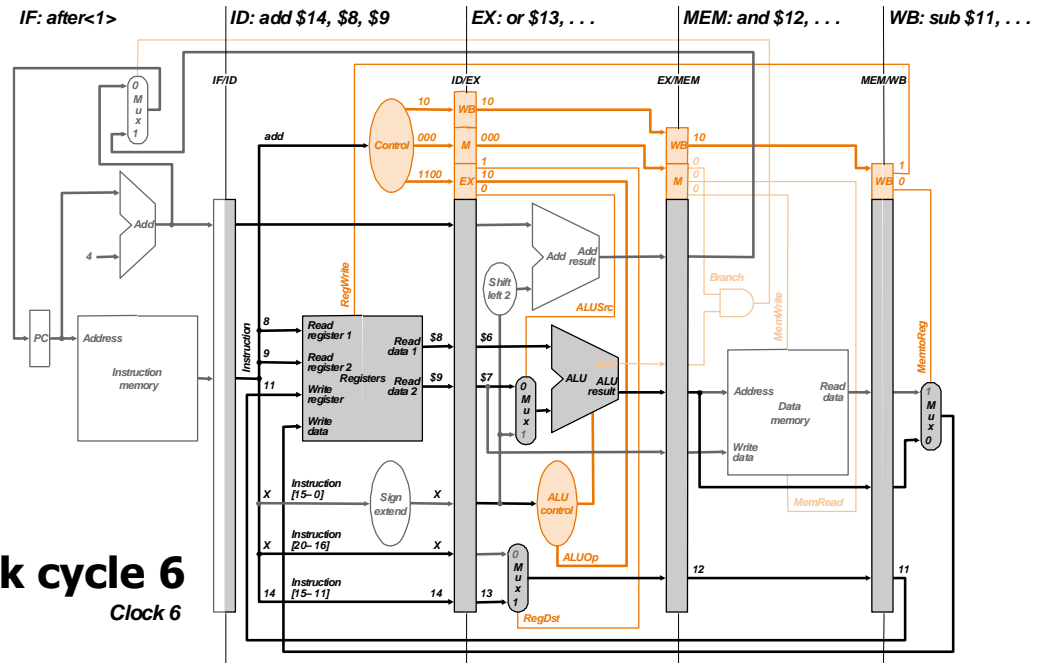


Pipelined Execution and Control


- Instruction sequence:

```
lw    $t0, 20($t1)
sub    $t1, $t2, $t3
and    $t2, $t4, $t7
or     $t3, $t6, $t7
add    $t4, $t8, $t9
```

Clock cycle 7
Clock 7

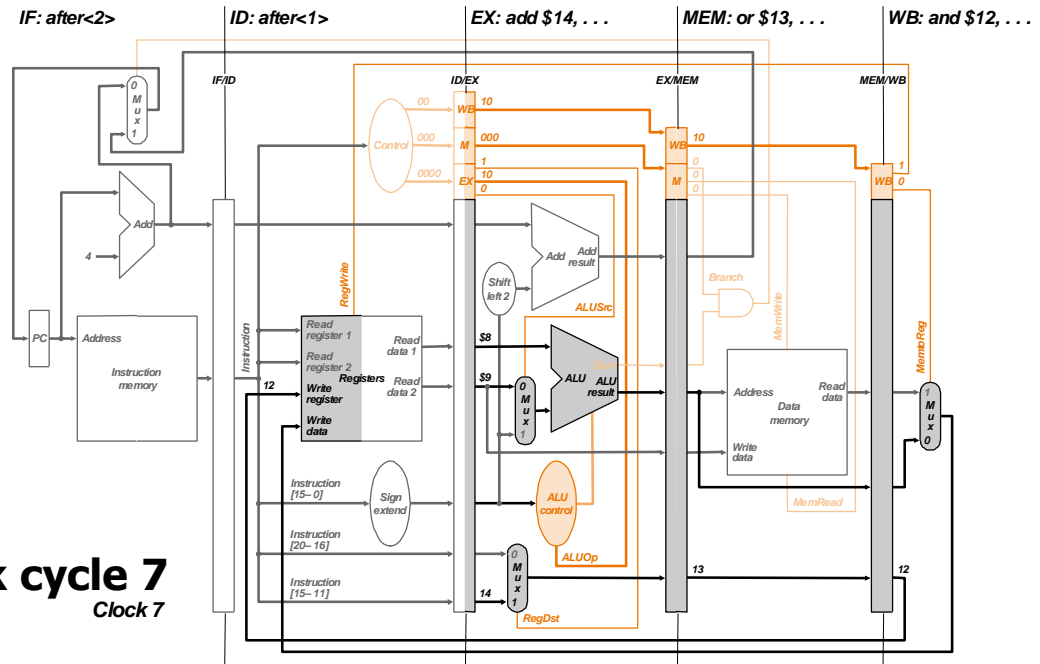

Clock cycle 8
Clock 8

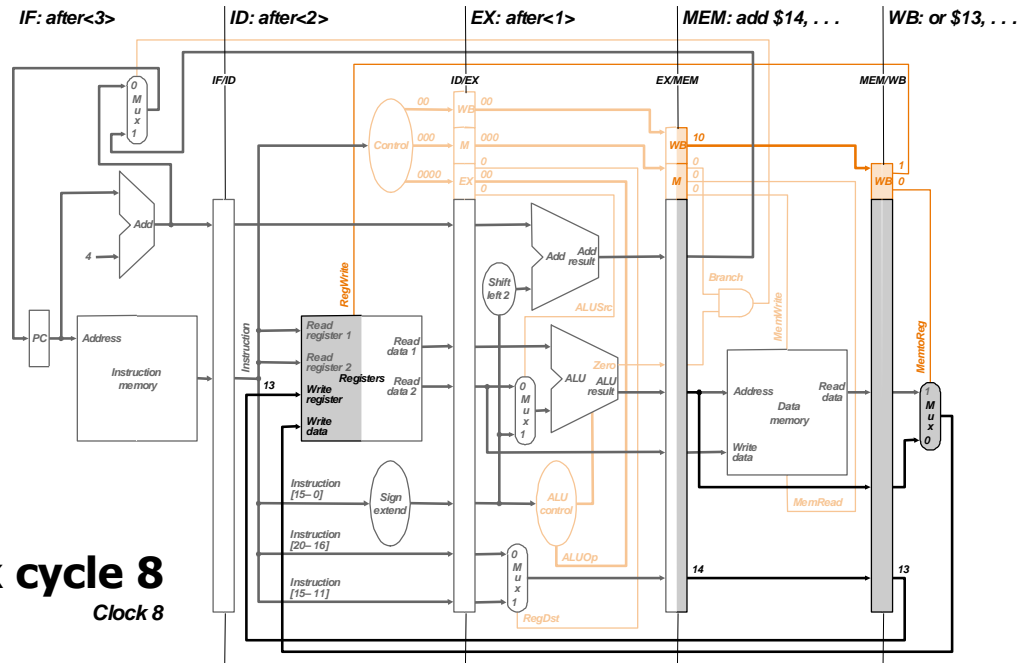

Pipelined Execution and Control

- Instruction sequence:**

```
lw    $t0, 20($t1)
sub    $t1, $t2, $t3
and    $t2, $t4, $t7
or     $t3, $t6, $t7
add    $t4, $t8, $t9
```

